

Seat # 23

أحمد نزار عيسى شعبة (١)

Electrical Machines, 0903373 2nd Exam Second Term 2013/2014.
Student Name (Arabic): ————— Student, ID —————

Problem1: Problem 1: Three single phase transformer have 19052/415 V, 1000 KVA each are supplied from a 33000 V source to form a group of three phase transformer for supplying a load of 500 KVA, 415 V with 0.85 power factor lagging. Sketch the system and determine the line current drawn by the load and supplied from the source



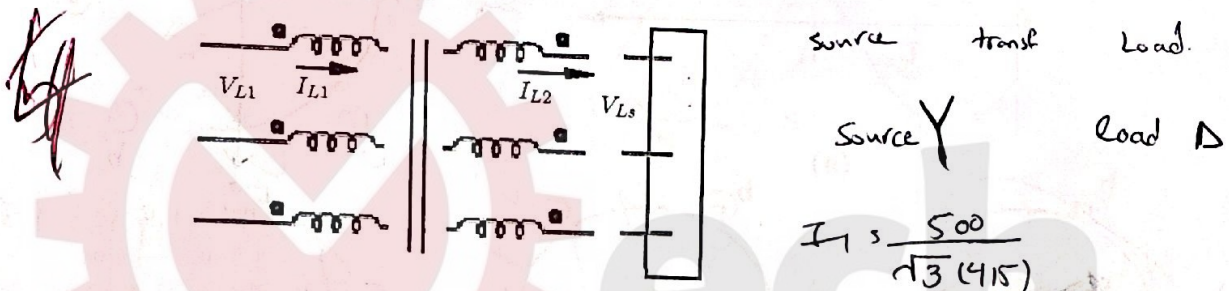
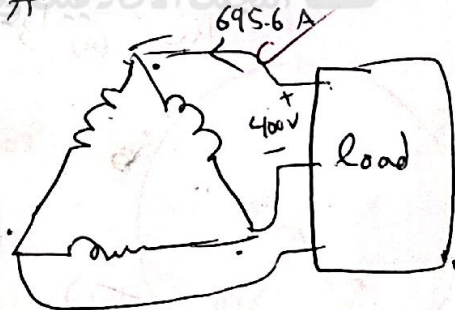
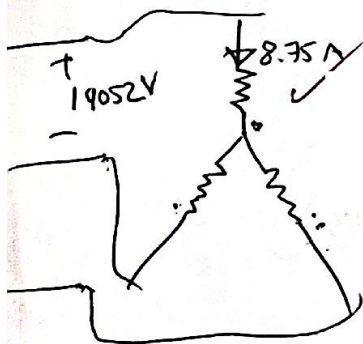


Figure 1:

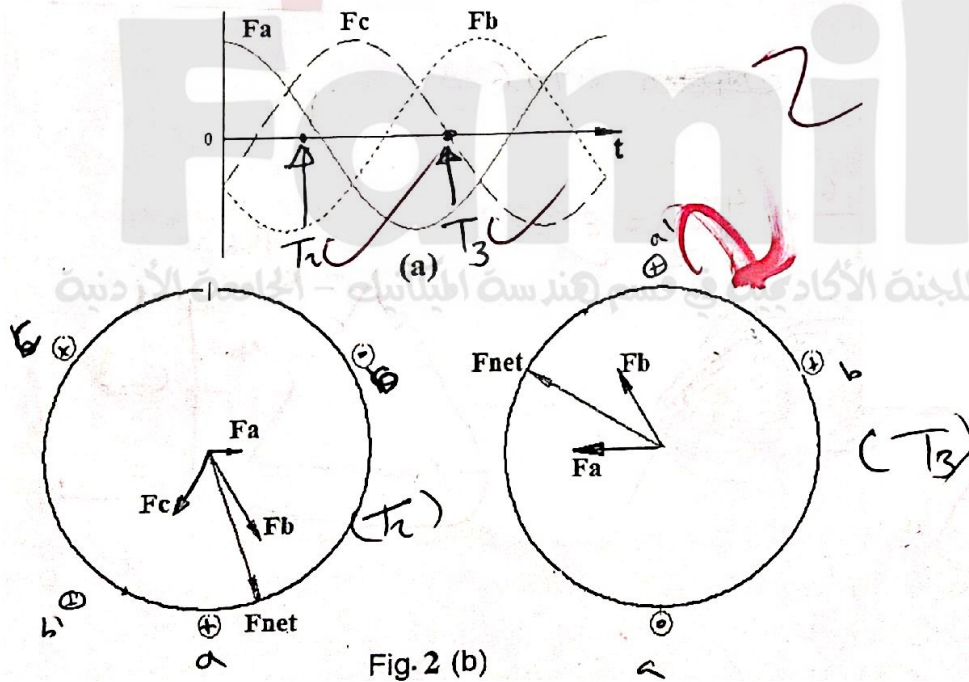1. $V_{L1} = 19052 \text{ V}$
2. $V_{Ls} = 415 \text{ V}$
3. $I_{L2} = \frac{500 \times 10^3}{\sqrt{3} \times 415} = 695.6 \text{ A}$
4. $I_{L1} = \frac{695.6}{\sqrt{3}} \times \frac{415}{19052} = 8.75 \text{ A}$



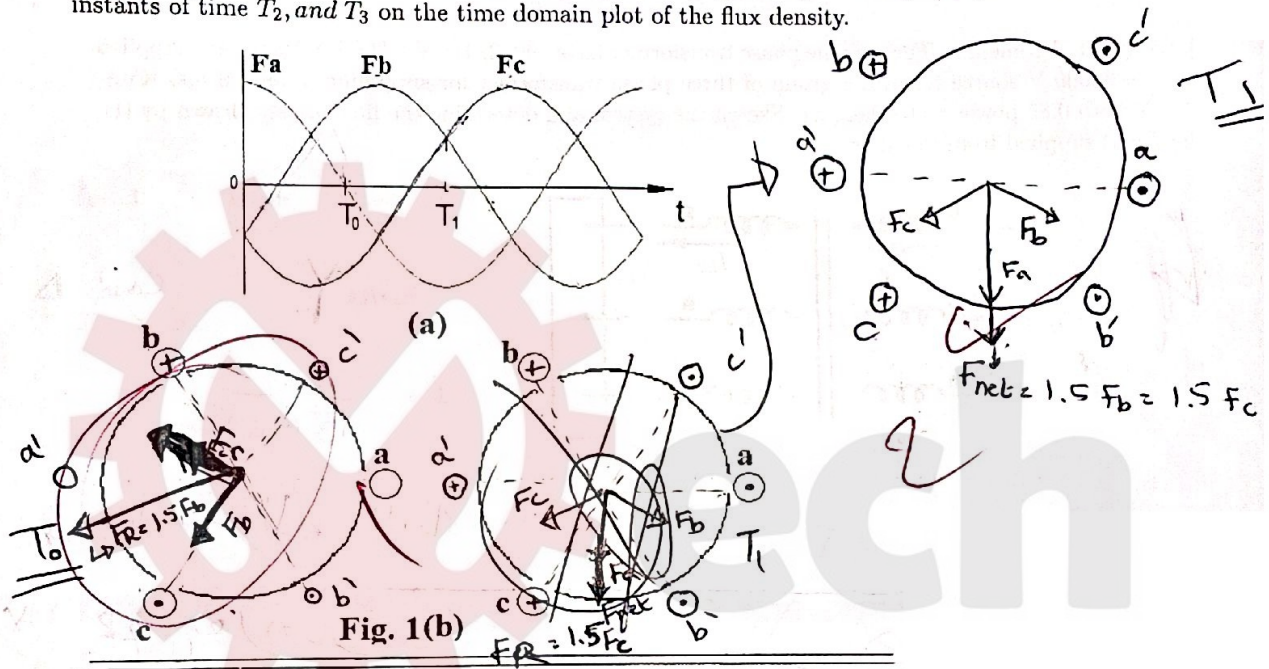Problem2: Use Fig.1(a,b) to explain the concept of rotating magnetic field and show the resultant magnetic force and location of poles at instants of time, T_0 , and T_1 . Use Fig2.(a,b) to determine the instants of time T_2 , and T_3 on the time domain plot of the flux density.



$$s_{max} = \frac{R_2}{\sqrt{R_{th}^2 + (X_2 + X_{th})^2}}$$

Protection

$$P_{out} = P_{conv} - (200)$$

$$P_{conv} = (1-s) [P_{AG}]$$

$$P_{AG} = 3 I_2^2 \frac{R_2}{s}$$

$$P_{AG} = 3 V_{th}^2 R_2$$

$$R_1 \left(\frac{X_m}{X_m + X_1} \right)^2 = 0.2345$$


$$110 \times 180 \frac{2\pi}{60} = P_{AG}$$

$$P_{AG} = 3 I_2^2 \frac{R_2}{s} \rightarrow R_2$$

Problem3: A three-phase 380 V, 60 Hz, 4-pole, Wye connected, induction motor. The developed torque speed curve is given in Figure below. Losses: core=0W, rotational includes friction and windage = 200, losses. It has the following parameters: $R_1 = 0.24\Omega$, $R_2' = ???\Omega$, $X_1 = 0.6$, $X_2 = 1.2\Omega$, $X_m = 51.58\Omega$.

(a) If the motor operates at 0.05 slip and the rotor current is $I_2' = 33.428 \angle -15.79^\circ$, find the value of $R_2' =$

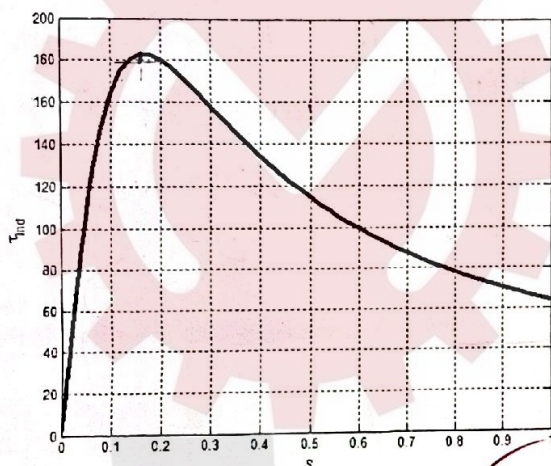(b) For the same characteristics assume that $R_2' = 0.45\Omega$ find the starting torque and speed for new value of $1.5 \times R_2'$.



$$R_1 = 0.24 \Omega, R_2 = ?? \quad X_m = 51.58 \Omega$$

$$X_1 = 0.6 \Omega, X_2 = 1.2 \Omega$$

$$s = 0.05$$

$$I_2 \checkmark$$

$$n_{sync} = \frac{60(60)}{2} = 1800 \text{ rpm}$$

$$n_{motor} = (1 - 0.05)(1800) = 1710 \text{ rpm}$$

$$(a) s_{max} = 0.15$$

$$s_{max} = \frac{R_2}{\sqrt{R_{th}^2 + (X_2 + X_{th})^2}}$$

$$R_{th} = R_1 \left(\frac{X_m}{X_m + X_1} \right)^2 = 0.2345$$

$$R_2 = 0.272 \Omega$$

$$0.15 = \frac{R_2}{\sqrt{0.2345^2 + (1.2 + 0.6)^2}}$$

$$\text{Starting torque; } s=1, T_{ind} = \frac{3 V_{th}^2 R_2 / s}{\omega_{syn} \left[\left(\frac{R_2}{s} + R_{th} \right)^2 + (X_2 + X_{th})^2 \right]}, V_{th} = V_{\phi} \left(\frac{X_m}{X_m + X_1} \right) = 216.87$$

$$T_{starting} = \frac{3 \times 0.675 \times 216.87^2}{188.5 \left[(0.675 + 0.2345)^2 + (0.6 + 1.2)^2 \right]} = 124.23 \text{ N.m.}$$

$$\text{Speed: } n_1 = (1-s)(n_{sync})$$

$$= (1-0.05)(1800) = 1710 \text{ rpm.} \quad \text{Then!}$$

Problem 4: The following test results were obtained when testing a three phase, 400-V, 50-Hz, 4 pole wye-connected, induction motor: No Load test: 400V, 30A, 4 kW, 50Hz
Blocked Rotor: 100V, 100A, 9 kW, 25Hz
DC Test: 3V; 10A

a) Find the No-load rotational losses.

b) Draw the single-phase equivalent circuit and label all its components with values calculated from above tests.

(b)

$$\text{DC test: } R_1 = \frac{1}{2} \left(\frac{3}{10} \right) = 0.15 \Omega$$

$$\text{NL test: } Z_{NL} = \frac{400/\sqrt{3}}{30} = 7.7 \Omega = X_1 + X_m$$

$$\text{BR test: } Z_{BR} = \frac{100}{\frac{\sqrt{3}}{100}} = \frac{1}{\sqrt{3}} = 0.577 \Omega$$

$$\text{PF} = \cos^{-1} \left(\frac{9000}{\sqrt{3}(100)(100)} \right) = \theta = 58.69^\circ$$

$$R_{BR} = \cos(58.69) \times 0.577 = 0.3$$


$$R_2 = 0.3 - 0.15 = 0.15 \Omega$$

$$X_{BR} = \sin(58.69) \times 0.577 = 0.493 \Omega$$

$$X_{BR} = X_1 \left(\frac{50}{25} \right) = 0.987$$

$$X_{BR} = X_1 + X_2 = 2X_1 \Rightarrow X_1 = 0.493 \Omega = X_2$$

$$X_m = 7.7 - 0.493 = 7.2 \Omega$$

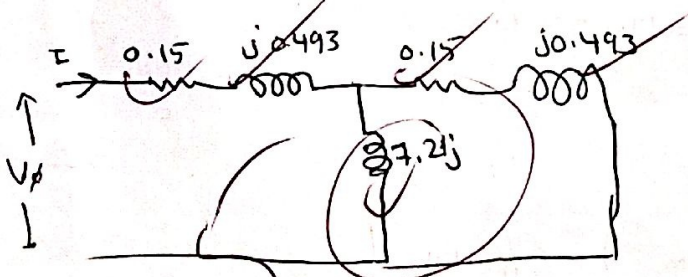

(a)

$$P_{rot} = P_{in} - P_{scL}$$

$$4000 - (3 \times 30^2 \times 0.15) = 3595 \text{ W}$$