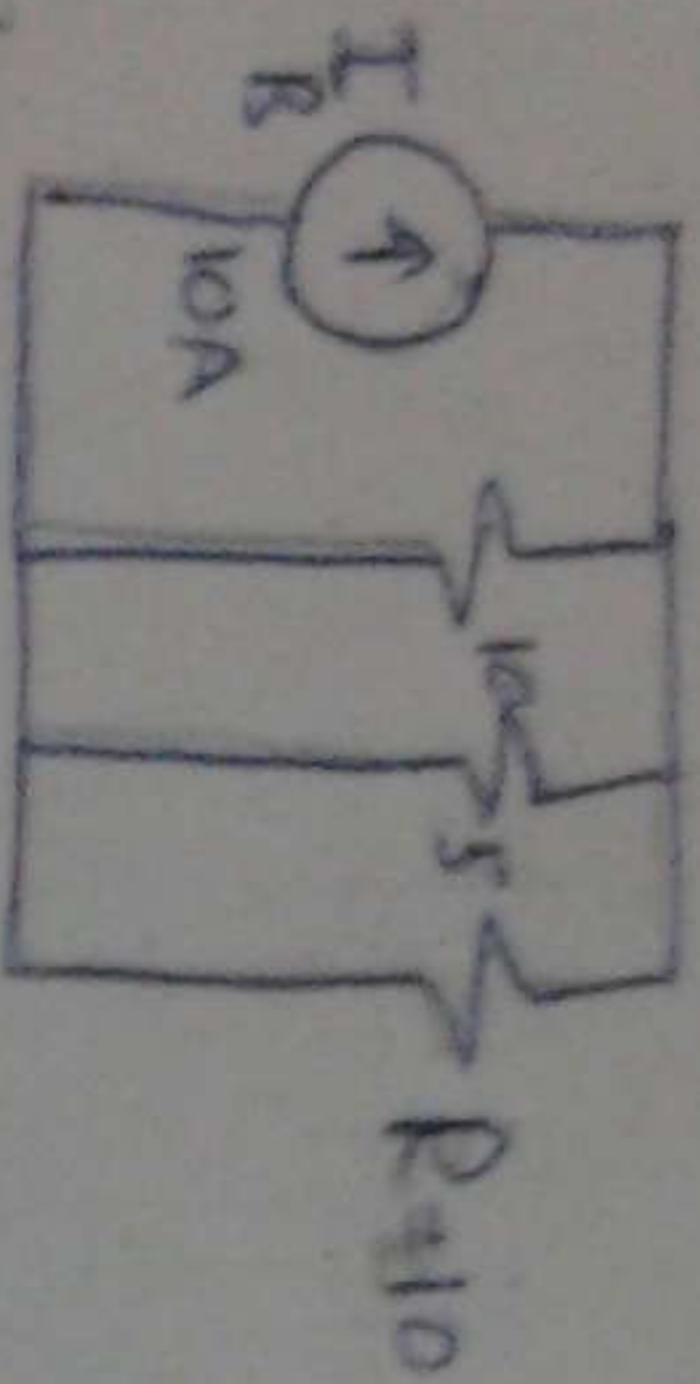



Q1-(7pts) For the circuit shown, where: $I_B = 10A$, $V_G = 12V$, $R_G = 5\Omega$, $R_B = R = 10\Omega$. By using superposition, determine the:

- Voltage across R .
- Power dissipated in R .
- Can be used the superposition method for power calculations, and why?

a)


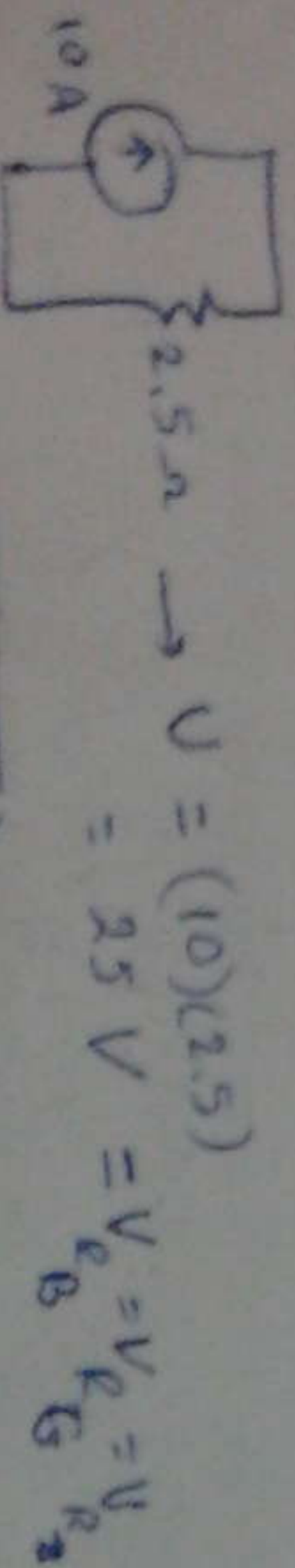
$$\frac{1}{R_{eq}} = \frac{1}{10} + \frac{1}{5} + \frac{1}{10} = \frac{4}{10} \rightarrow R_{eq} = 2.5 \Omega$$




$$V_{R_{short}} = 25 V$$

I_B open $\rightarrow$



$\Rightarrow$

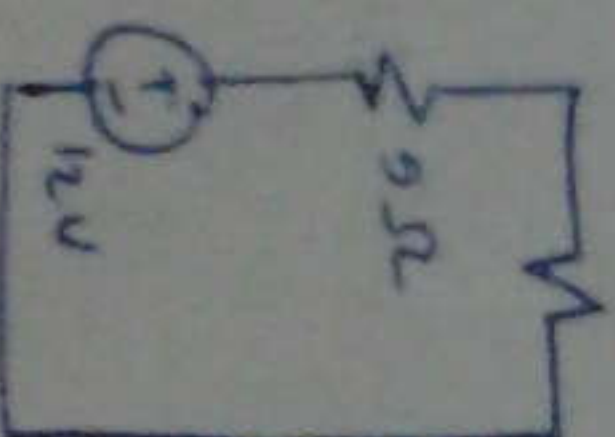


$$V_{eq} = \frac{12}{10} + \frac{12}{10} = 2.4 V$$

Voltage divider

$$V'_{R_{open}} = V_G \frac{R_{eq}}{R_G + R_{eq}} = 12 \left(\frac{2.5}{10 + 2.5} \right) = 2.4 V$$

$$V = 2.4 + 2.4 = 4.8 V$$
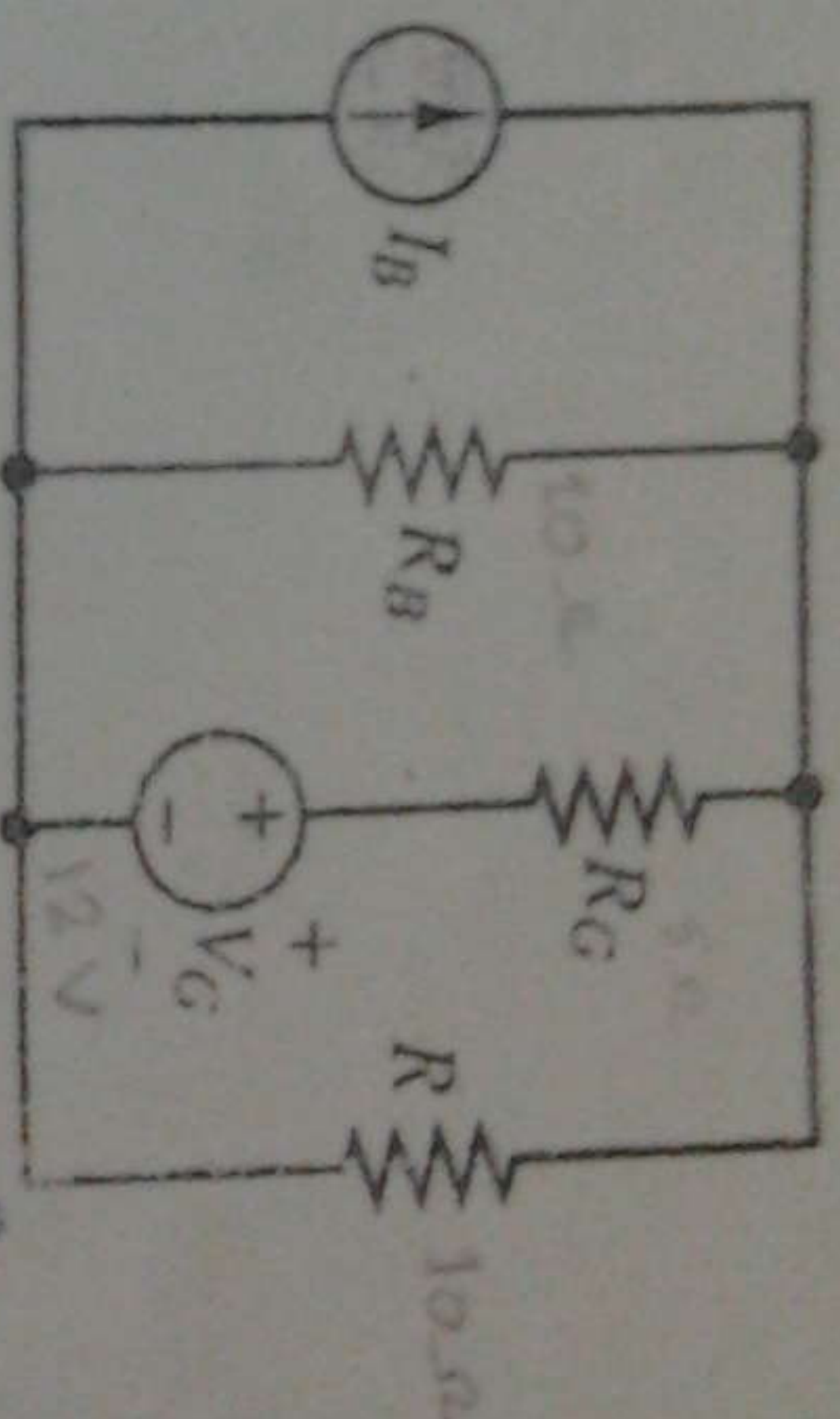
$$b) P = \frac{V^2}{R} = \frac{(4.8)^2}{10} = 2.304 W$$






a- $3.1 V$

b- $1.09 W$

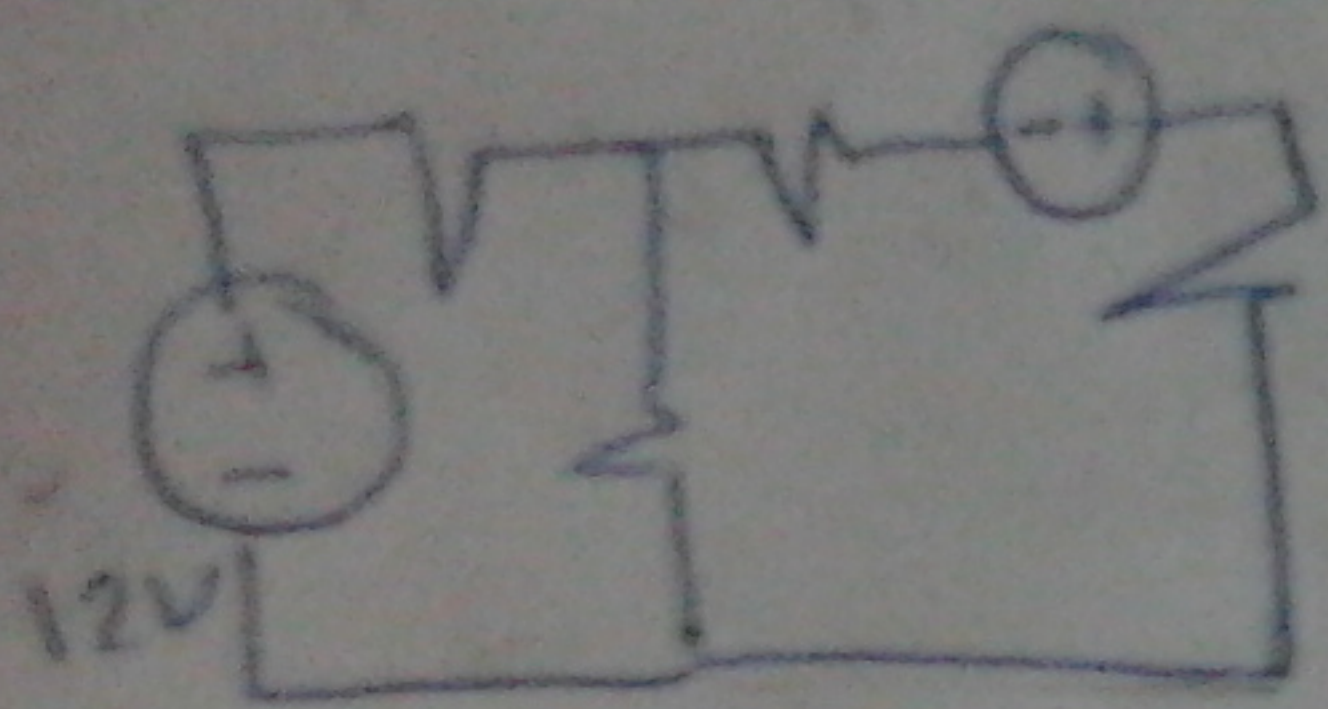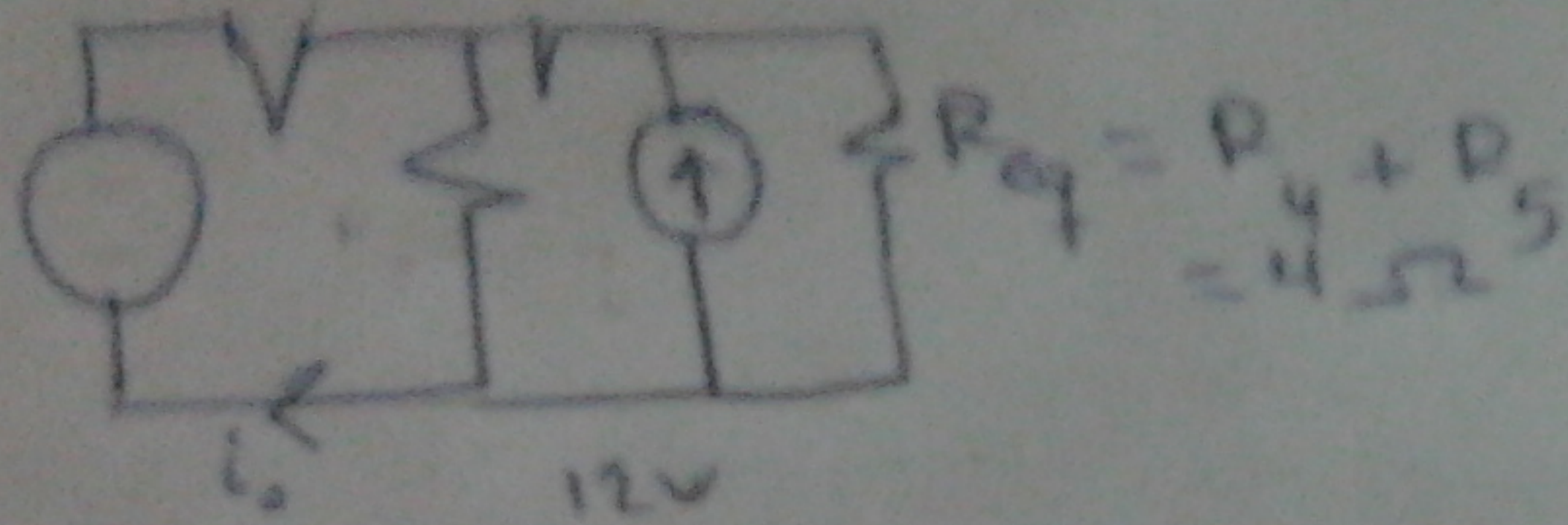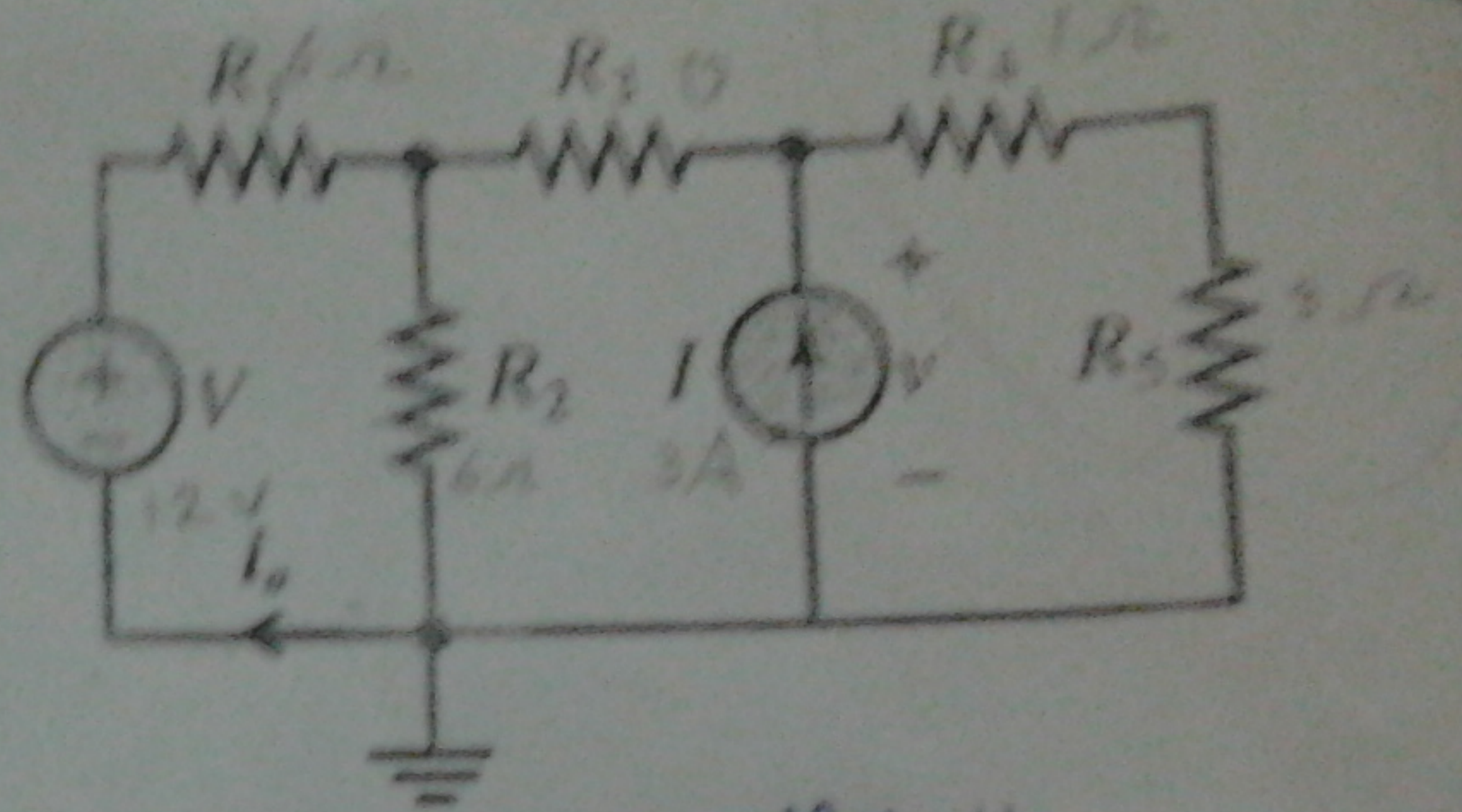Q3- (6Pts) For the circuit shown, where: $V = 12V$, $I = 3A$,
 $R_1 = 6\Omega$, $R_2 = 6\Omega$, $R_3 = 6\Omega$, $R_4 = 1\Omega$, $R_5 = 3\Omega$.
 By using proper Source Transformation
 technique, determine the:


- a- Current i_o b- Voltage V across the I source.



$$V_1 = I R_{eq}$$

$$= (3)(4) = 12V \Rightarrow$$

$$R_{eq} = 0 + 4 = 4\Omega$$

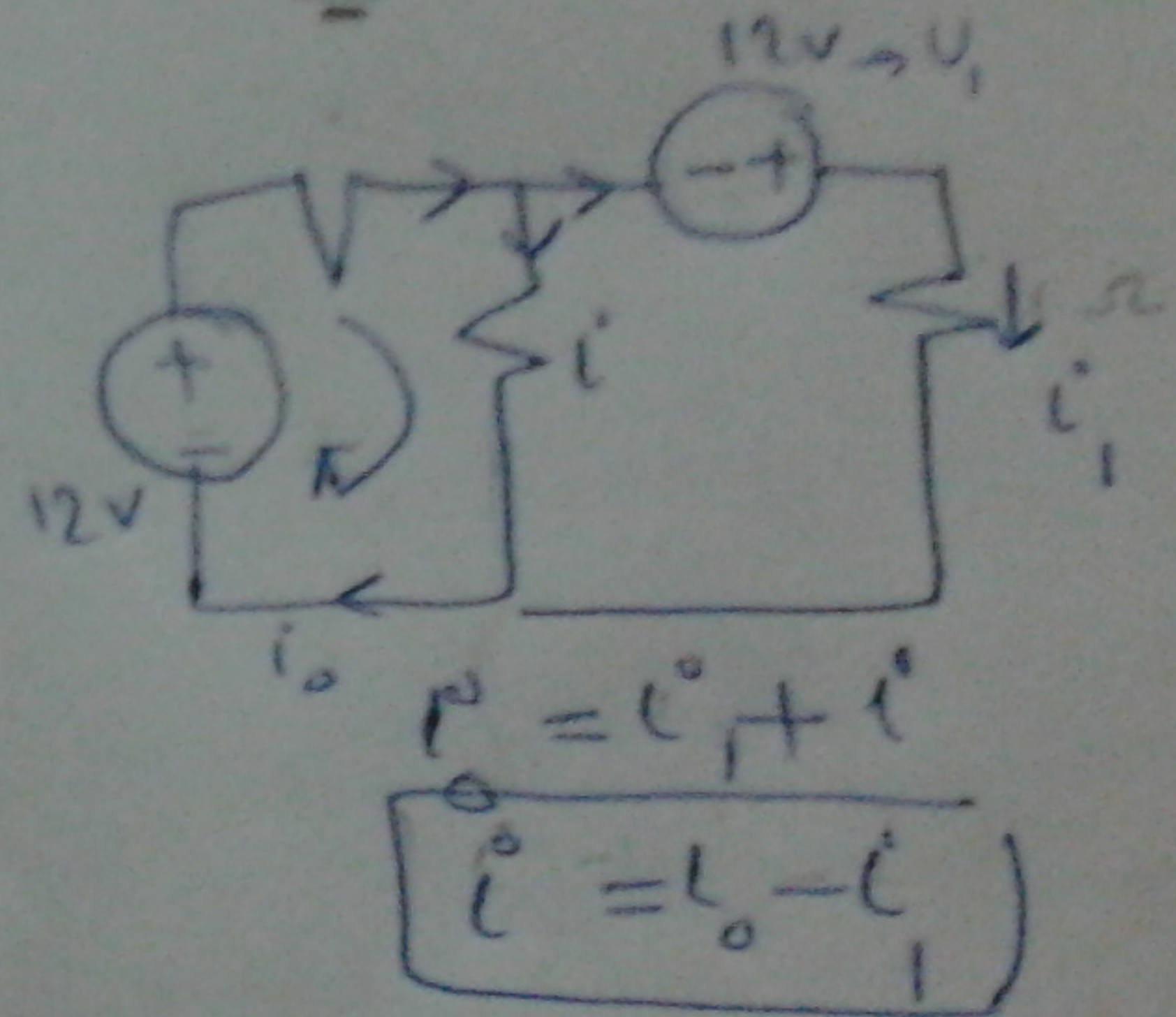

Use mesh method

$$-12 + i_o(6) - 12 + 4(i_o) = 0 \rightarrow 6i_o + 4i_o = 24$$

$$-12 + 6i_o + 6(i_o - i_1) = 0 \rightarrow 12i_o - 6i_1 = 12$$

$$i_o = 2.29 A$$

أو يمكن أن نحول الكلي على Transformative بتحويل
 12V 7.2V
 V₁ I V₁

a- 2.3 A

b- 12 V


Q3- (6Pts) For the circuit shown, where: $v_s(t) = 311 \cos(\omega t)$ V.

$i_L(t)$

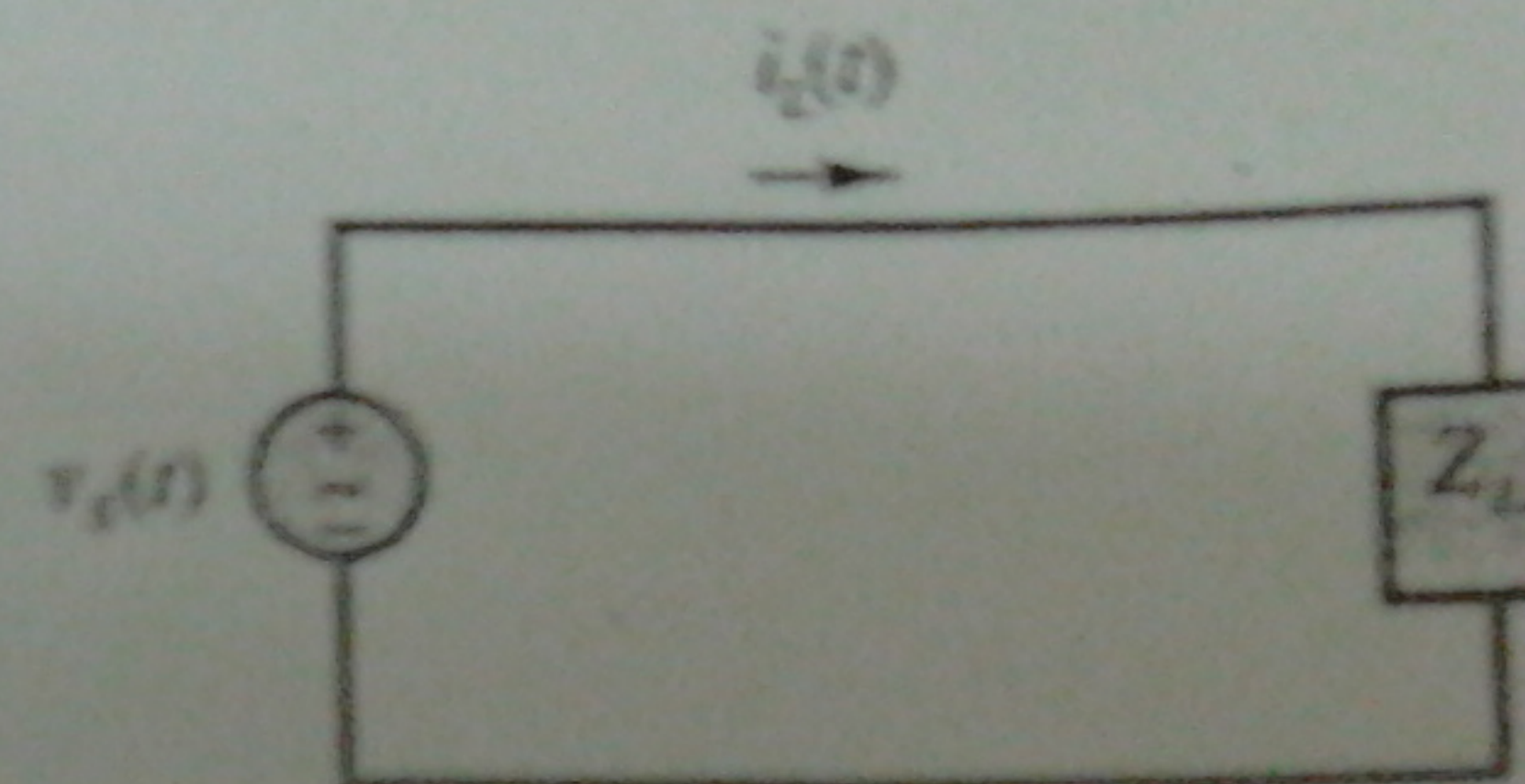Q3- (6P) For the circuit shown, where: $v_s(t) = 311 \cos(\omega t)$ V.

$i_L(t) = 2.83 \sin(\omega t + 55^\circ)$ A. Determine the:

- a- rms phasor voltage.
- b- rms phasor current.
- c- Phasor load impedance.
- d- Load power factor.
- e- Power factor it's leading or lagging.
- f- Load is Resistive, Capacitive or Inductive.



$$i_L(t) = 2.83 \cos(\omega t - 35^\circ)$$

$$V_{s\text{rms}} = \frac{311}{\sqrt{2}} = 219.9 \text{ V}$$

$$I_{\text{rms}} = \frac{2.83}{\sqrt{2}} = 2 \text{ A}$$

$$Z_L = \frac{V_s}{I_s} = \frac{311 \angle 0^\circ}{2.83 \angle -35^\circ} = 109.95 \angle 35^\circ$$

$$\text{PF} = \cos(\theta_v - \theta_i) = \cos(+35^\circ) = 0.82$$

$\theta_Z \rightarrow \text{positive} \rightarrow \text{lagging} \rightarrow \text{Inductive}$

a- 219.9 V

b- 2 A


c- $109.95 \angle 35^\circ$

d- 0.82

e- lagging

f- Inductive

balanced three-phase (a-b-c), 50 Hz, $Z_Y = (4 + j3) \Omega$.
 $R_{line} = 0.1 \Omega$, $R_{neutral} = 10 \Omega$. Determine the:
 a- rms $I_{aa'}$ phasor current. b- rms $I_{aa'}$ phasor current.
 c- Total generated real power. d- Power factor.
 e- Total generated complex (apparent) power.
 f- Total generated reactive power.
 g- Total Power losses in the lines.
 h- Sketch and label the power triangle phasor diagram.

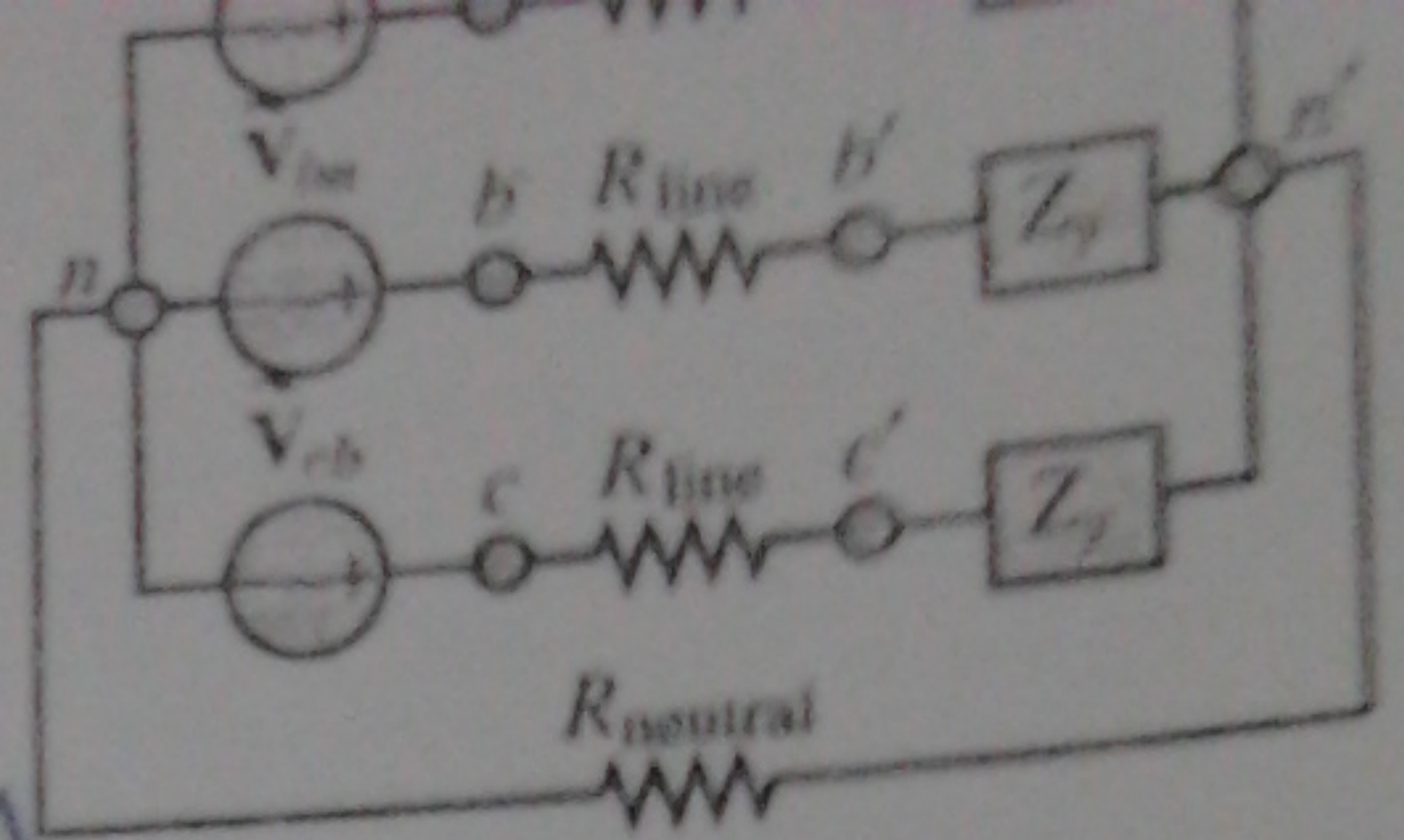

$$I_{aa'} = I_L = \tilde{I}_3 = \frac{\tilde{V}_{an}}{R_{line} + Z_Y} = 43.3 \angle -36.2^\circ \text{ A}$$

b- Zero.

$$Z_Y = 4 + j3 = 5 \angle 36.9^\circ \Omega$$

$$P_{av} = \sqrt{3} \tilde{I}_{LL} \tilde{V}_{LL} \cos \theta_z$$

$$\sqrt{3} (43.3) (375) \cos(36.9^\circ)$$

$$= 22.5 \text{ kW}$$

$$V_{p-L} = 220 \angle 0 \frac{4 + j3}{(4 + j3) + 0.1} = 2$$

$$V_{LL} = V_{aa'} = \sqrt{3} V_{L-P} = 375 \text{ V}$$

$$Q = \sqrt{3} I_{aa'} V_{aa'} \sin \theta_z$$

$$= 16.9 \text{ KVAR}$$


$$g- P_L = 3 I_{aa' \text{ line}}^2 R$$

$$= 562.5 \text{ W}$$

$$S_{total} = \sqrt{3} \tilde{V}_{aa'} \tilde{I}_{aa'}^*$$

$$= (\sqrt{3}) (375 \angle 0.67^\circ) (43.3 \angle +36.2^\circ)$$


$$= 28.1 \text{ KVA}$$

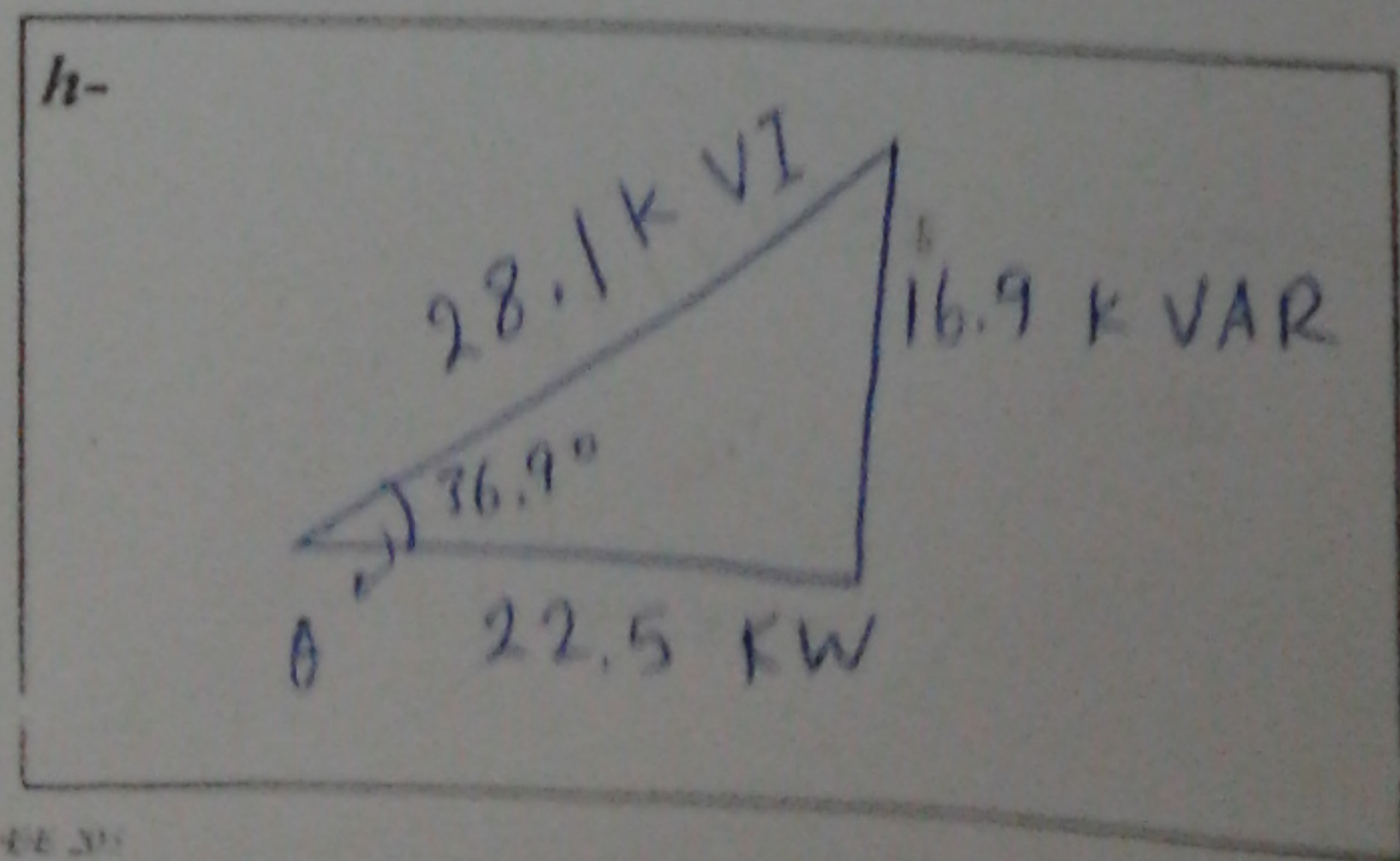

- a- 43.3 A
- b- Zero
- c- 22.5 kW
- d- 0.8
- e- 16.9 KVAR
- f- 28.1 KVA
- g- 562.5 W


Q11-(3Pts) For the shown BJTs, Determine the operating region and whether the BE and BC junctions are forward or reverse biased.

BJT	BE junction	BC junction	Operating Region
(a)	-0.5	-0.7	Cutoff
(b)	+0.7	+0.4	Saturated

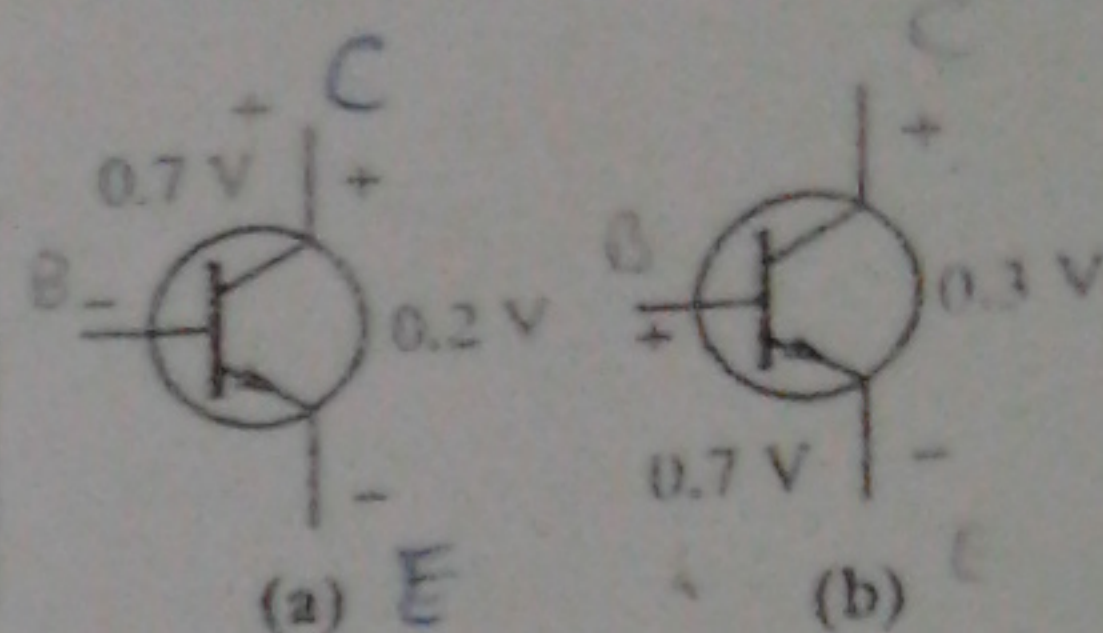

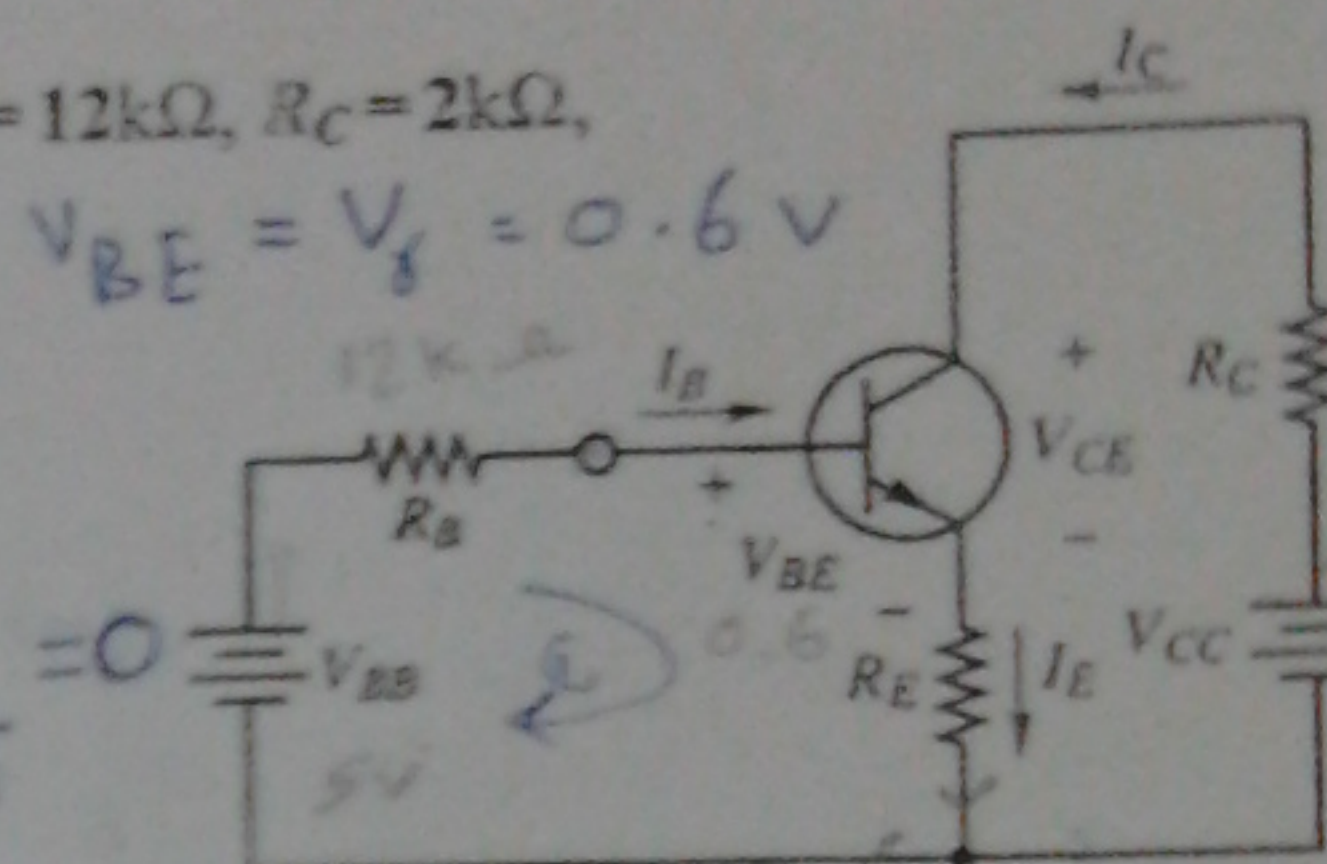Q12-(10Pts) For the circuit shown, where: $V_{BB} = 5V$, $V_{CC} = 15V$, $R_B = 12k\Omega$, $R_C = 2k\Omega$, $R_E = 1k\Omega$, $V_{\gamma} = 0.6V$, $\beta = 100$. Determine the:

- Base Current I_B .
- Collector Current I_C .
- Emitter voltage V_E .
- V_{CE} voltage.
- Operating region.



Q11

a) $BC = -0.7$ reverse

$$V_{CE} = V_{CB} + V_{BE}$$

$$0.2 = 0.7 + V_{BE}$$

$$V_{BE} = -0.5 \text{ V reverse}$$

b) $V_{BC} = ?$

$$V_{CE} = V_{CB} + V_{BE}$$

$$0.3 = V_{CB} + 0.7$$

$$V_{CB} = -0.4 \rightarrow V_{BC} = 0.4$$

$$-5 + I_B R_B + V_{BE} + I_E R_E = 0$$

$$I_E = I_B + I_C \quad \text{plug}$$

$$\rightarrow 10^3 I_C + 13 \times 10^3 I_B = 4.4$$

$$\text{but } I_C = I_B \beta = 100 I_B \quad \text{plug} \quad [a]$$

$$\text{we have } I_B = 0.04 \text{ mA} \quad [b]$$

$$I_C = (100)(0.04 \times 10^{-3}) = 4 \text{ mA}$$

$$\text{outer loop } -5 + R_B I_B + V_{BC} - R_C I_C + V_{CC} = 0$$

$$-5 + (12 \times 10^3)(0.04 \times 10^{-3}) + V_{BC} - (2 \times 10^3)(4 \times 10^{-3}) + 15 = 0$$

$$V_{BC} = -2.5 \text{ V (reverse)}$$

$$V_{BE} = +0.6 \text{ (forward)}$$

(e) Active Region

$$\begin{aligned} V_{CE} &= V_{CB} + V_{BE} \\ &= 2.5 + 0.6 \\ &= 3.1 \text{ V} \end{aligned}$$

$$\begin{aligned} V_E &= I_E R_E \\ &= (I_B + I_C) R_E \\ &= 4 \text{ V} \end{aligned}$$

a- 0.04 mA

b- 4 mA

c- 4 V

d- 3.1 V

e- active

Q14-(4Pts) a- Fill in the blank cells in the table by a proper result depends on the rules of Boolean algebra.

Boolean Algebra	Result	Boolean Algebra	Result
$0 + X$	X	$X \cdot \bar{X}$	1
$1 + X$	1	$X + X \cdot Z$	X
$X + X$	X	$X \cdot (X + Y)$	X
$X \cdot \bar{X}$	0	$X + \bar{X} \cdot Y$	$X + Y$

b- Use Truth table to prove that $= AB + \bar{A}B$.

$$= B(A + \bar{A})$$

$$= B$$

$AB + \bar{A}B$


A	B	$\bar{A}$	AB	$\bar{A}B$	$AB + \bar{A}B$
0	0	1	0	0	0
0	1	1	0	1	1
1	0	0	0	0	0
1	1	0	1	0	1

Q15-(3Pts) For the logic circuit shown. a- Determine the Boolean function describing the operation of the output F.

b- Build a truth table of this logic circuit, function by X, Y, Z.

a- $F = (\bar{A} \cdot \bar{B}) \cdot (\bar{C} \cdot D) \cdot (\bar{E})$

b-

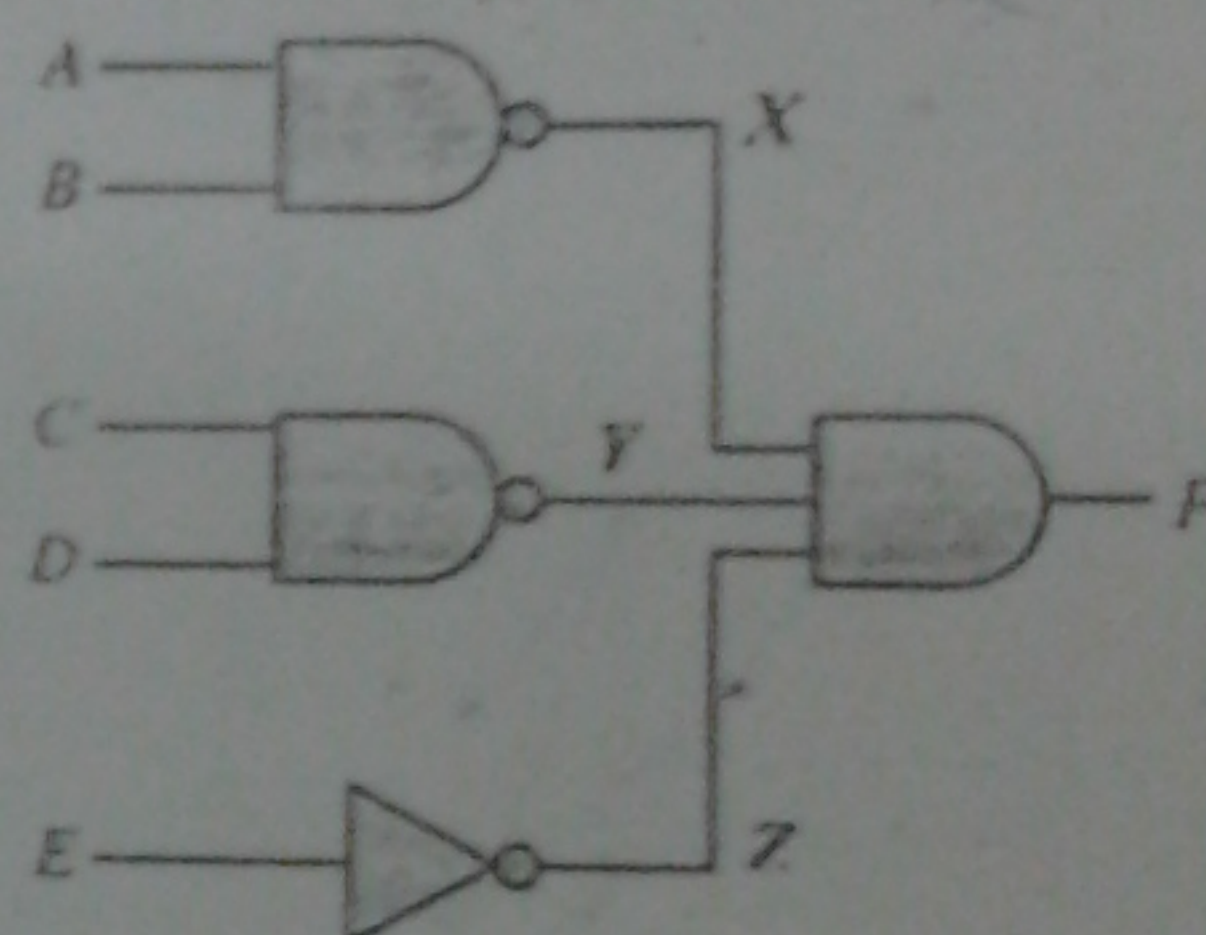

Q16-(4Pts) For the logic circuit shown.


a- Determine the Boolean function describing the operation of the outputs S and C.

b- Build a truth table of this logic circuit.

c- Name the acts of this logic circuit.

a) $S = A \oplus B$

$C = A \cdot B$

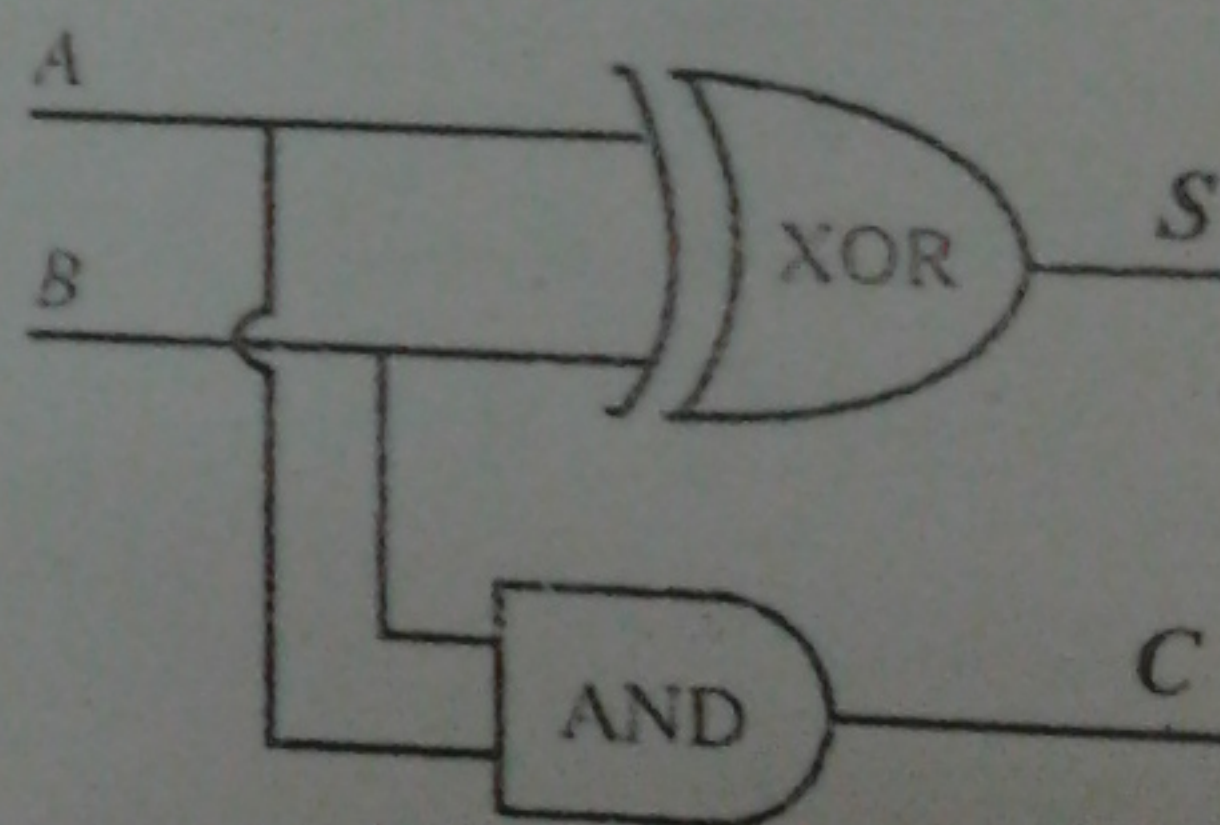

a- $S = A \oplus B$
 $C = A \cdot B$

c- half-adder

b-

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1