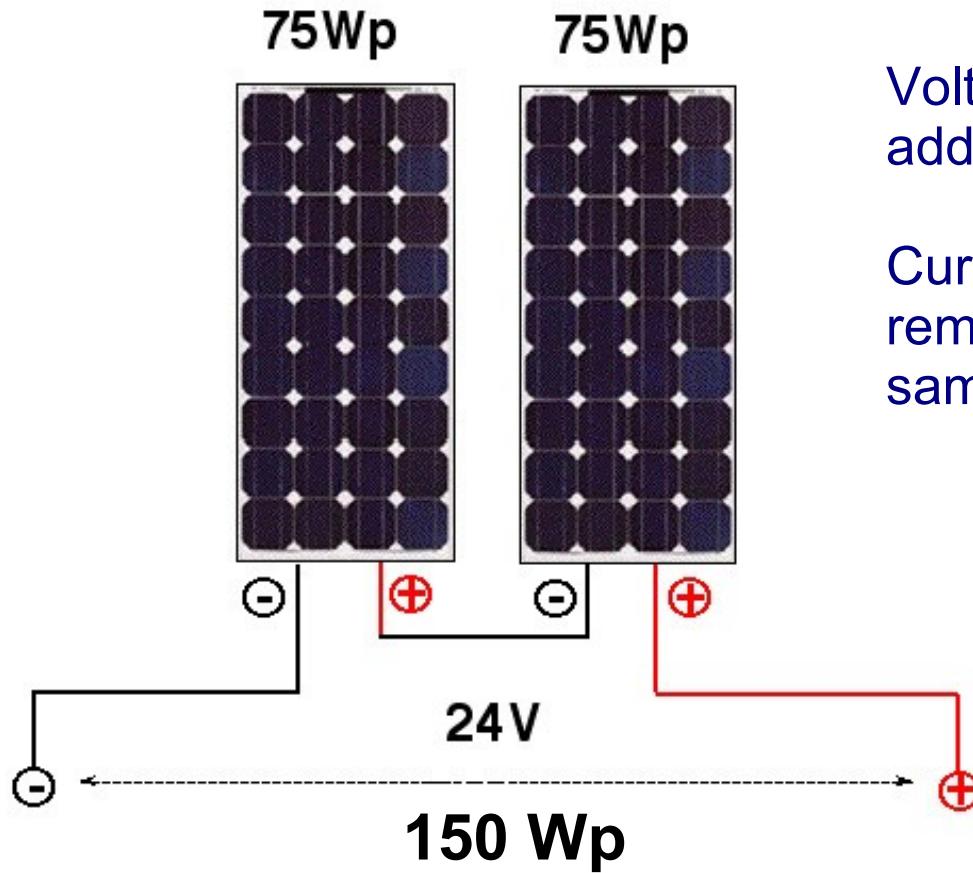


SOLAR MODULES

- WIRING CONFIGURATIONS

Two solar modules connected in series

Modules wattages are added together




Voltages are added together

Current remains the same

Two solar modules connected in parallel

Modules wattages are added together


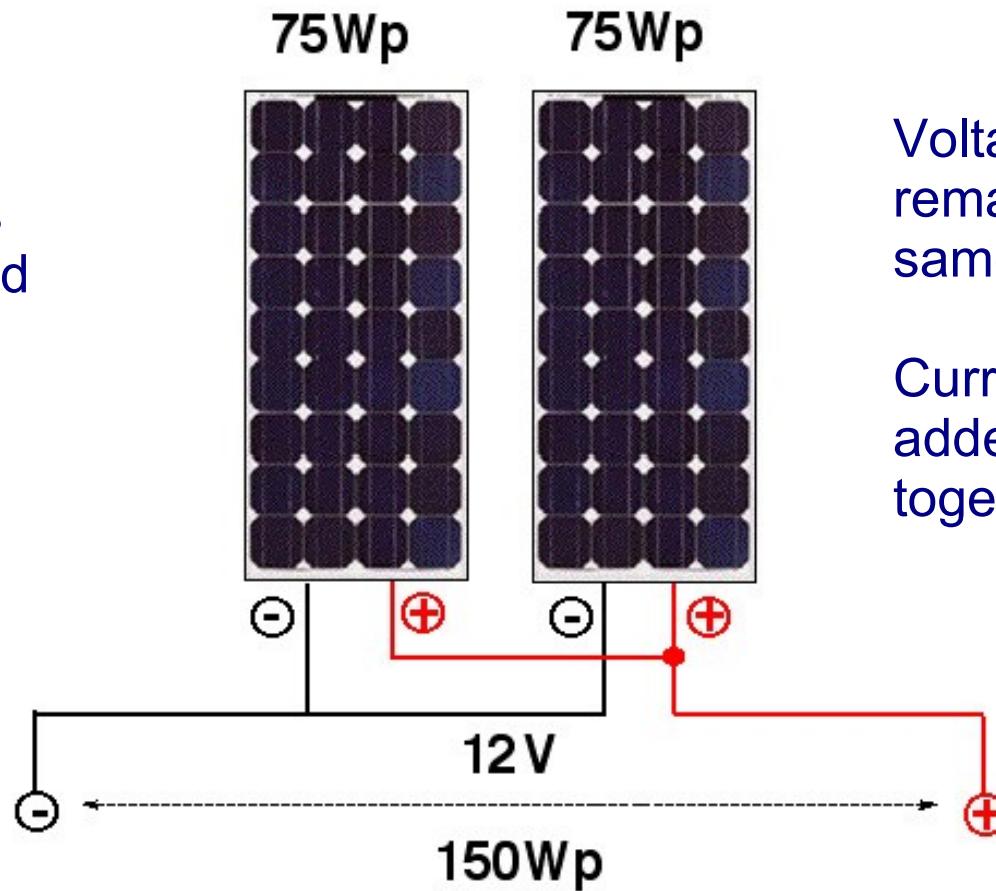


Voltage remains the same


Currents are added together

Four solar modules connected in series

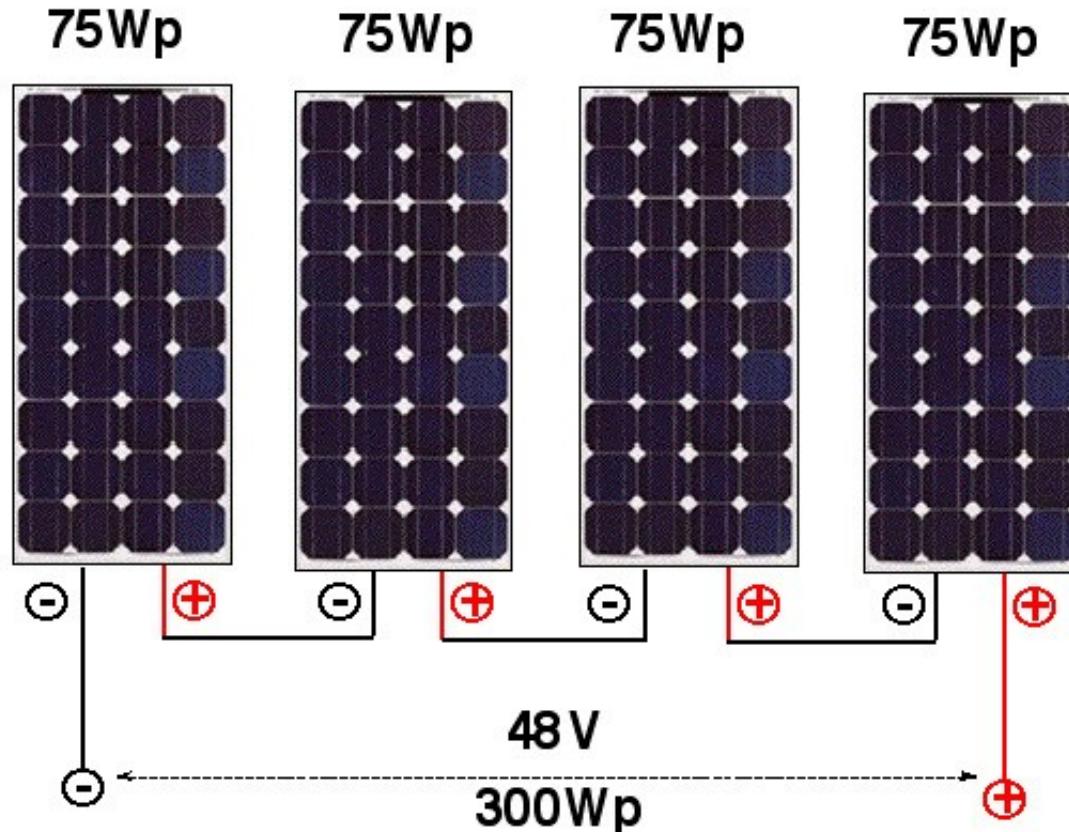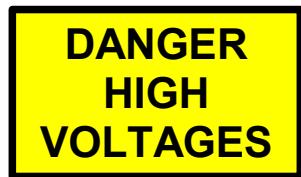Modules wattages are added together
Volts are added together
Current remains the same





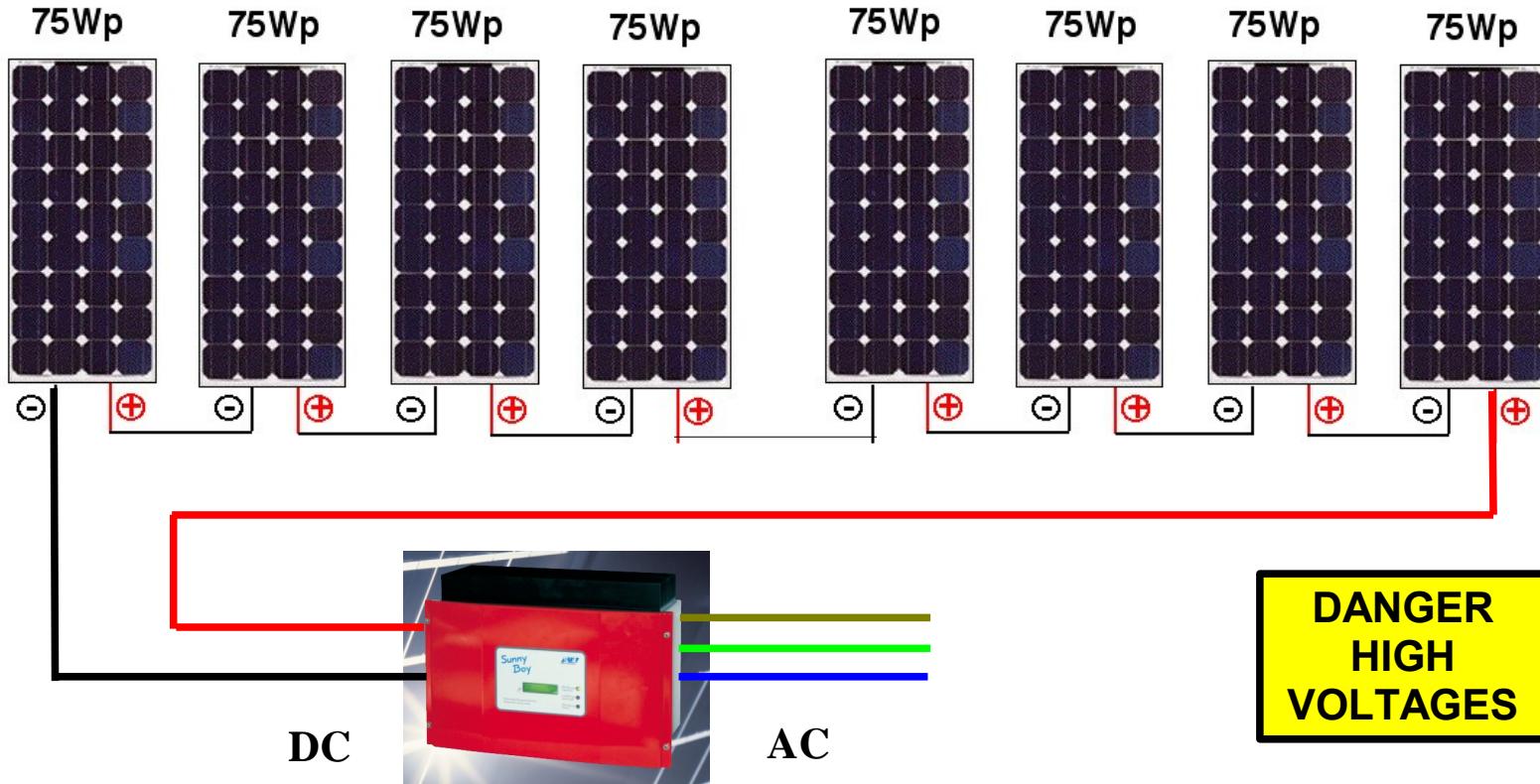Grid-tied PV - wiring of modules in strings




Solar modules of *different sizes* connected in series

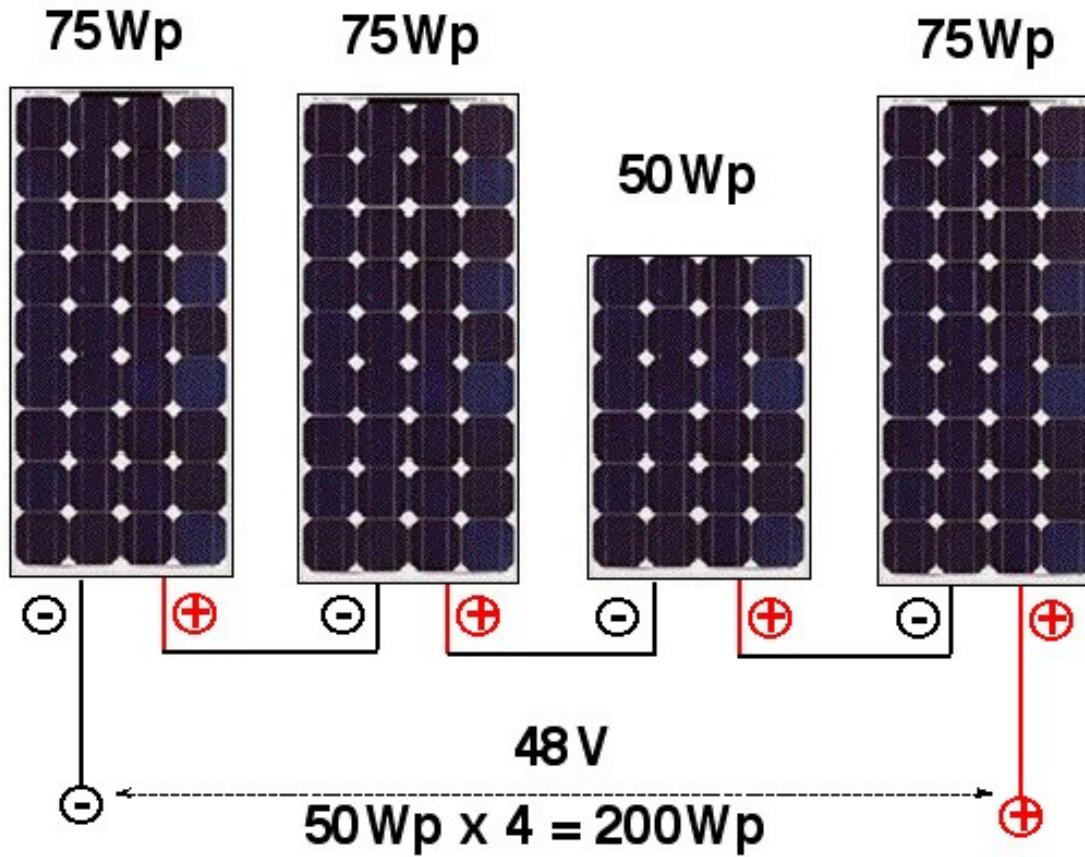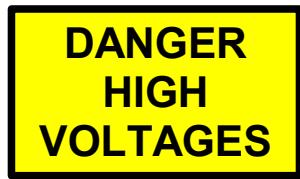Voltages
are added
together
Current will
be that of
the
smallest
module




Four solar modules connected in parallel

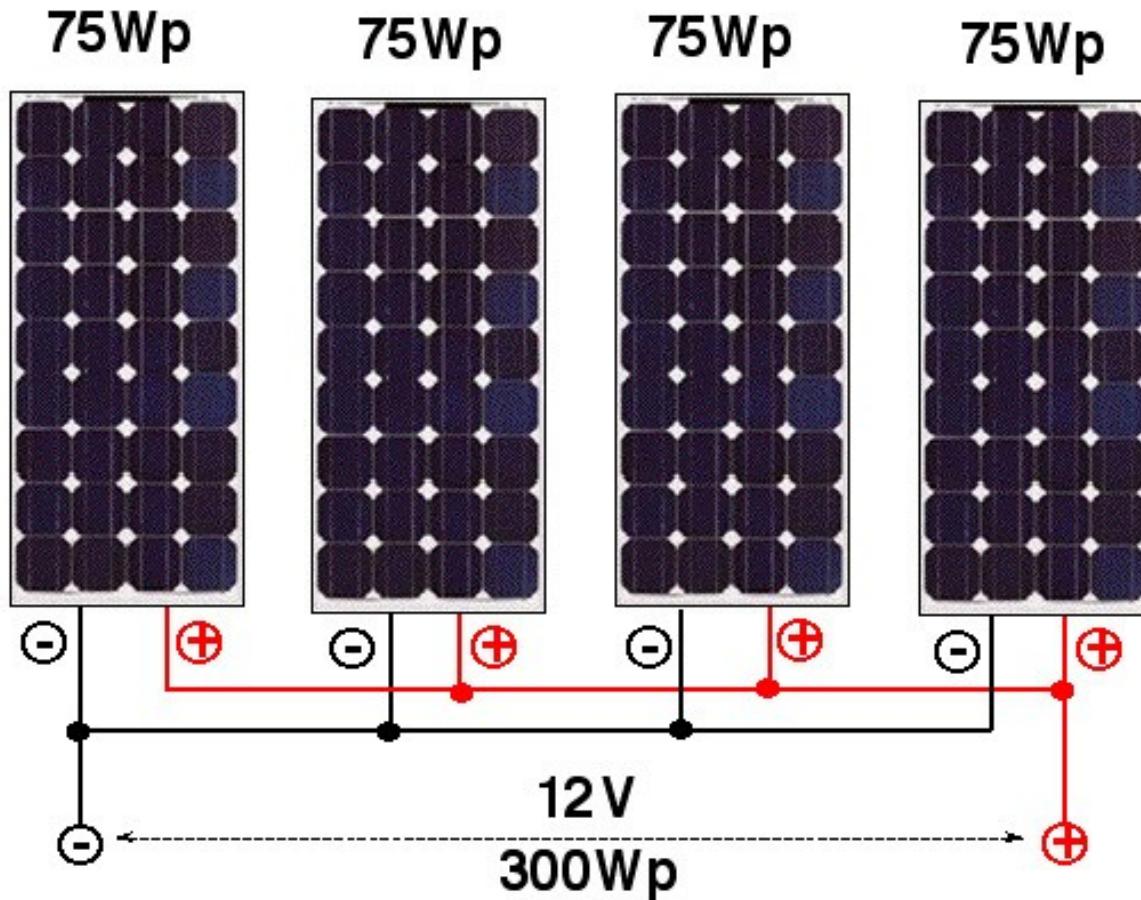Module wattages are added together
Voltage remains the same
Currents are added together



Solar modules of *different sizes* connected in parallel

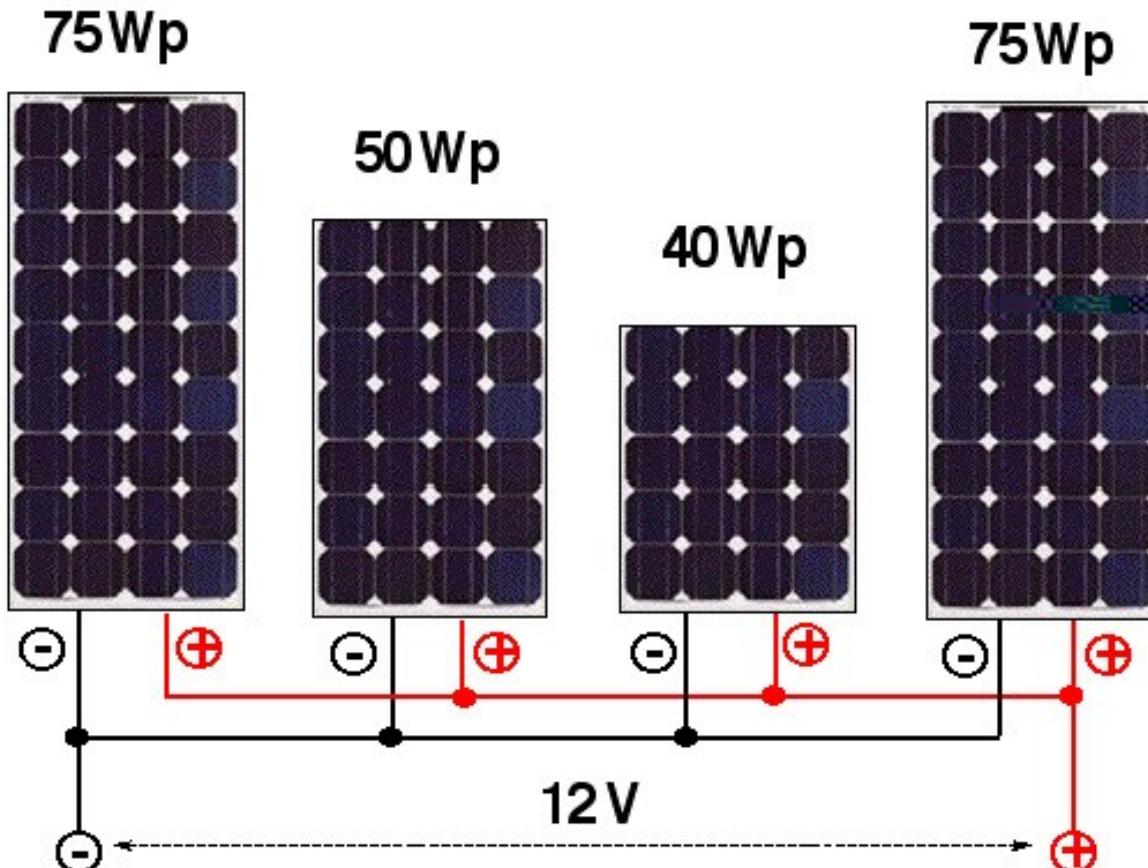Module wattages are added together
Voltage remains the same
Currents are added together



$$75Wp + 50Wp + 40Wp + 75Wp = 240Wp$$

Solar modules connected in series-parallel

Wattages
are added
together




Current of
strings are
added
together

Solar modules connected in series-parallel

Wattages
are added
together


Current of
strings are
added
together

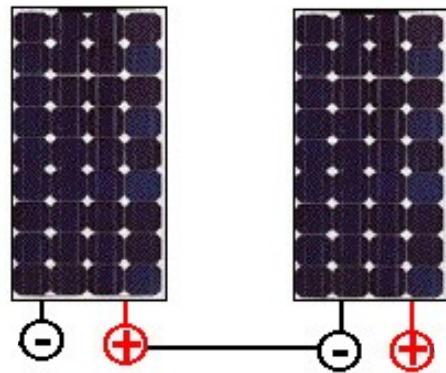

Solar modules connected in series-parallel

Wattages
are added
together

Current of
strings are
added
together

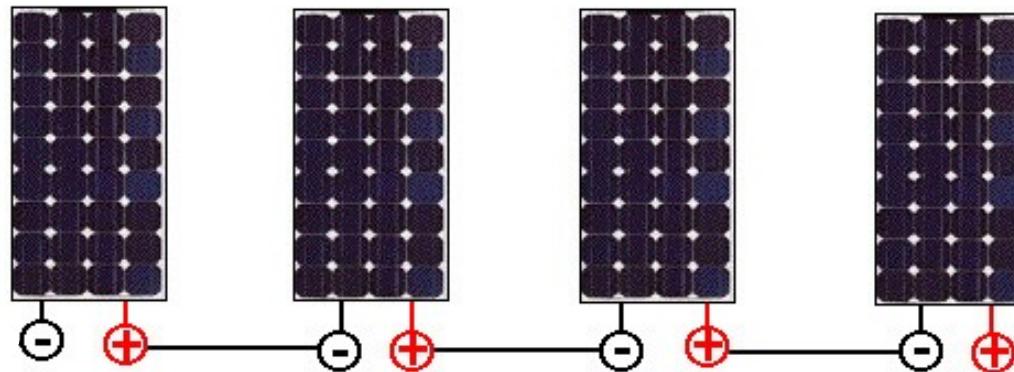

**DANGER
HIGH
VOLTAGES**

Solar modules connected in series-parallel

Wattages
are added
together

Current of
strings are
added
together

**DANGER
HIGH
VOLTAGES**

