
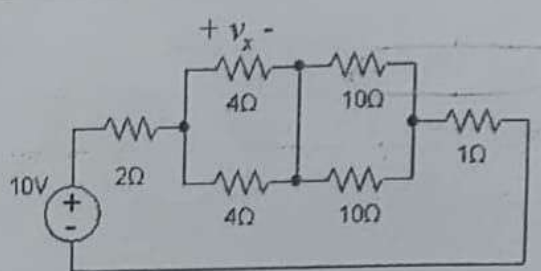
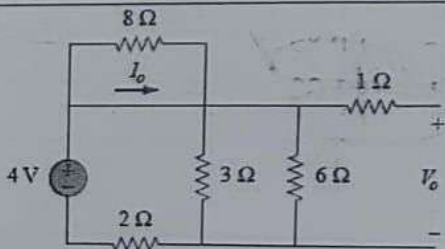
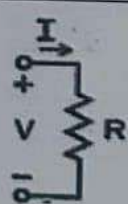


Q4	For the circuit shown, the voltage v_x is:	
a.	2.86 V	
b.	1 V	
c.	2.5 V	
d.	0 V	
e.	2 V	


Q5	For the circuit shown, I_o is:	
a.	1.5 A	
b.	0.5 A	
c.	1 A	
d.	0 A	
e.	0.33 A	

Q6	If the voltage across a resistor is 0.6V, and $R=20\text{ K}\Omega$, the current flowing through the resistor is	
a.	30 μA	
b.	30 mA	
c.	0.3 pA	
d.	30 pA	
e.	0.3 μA	
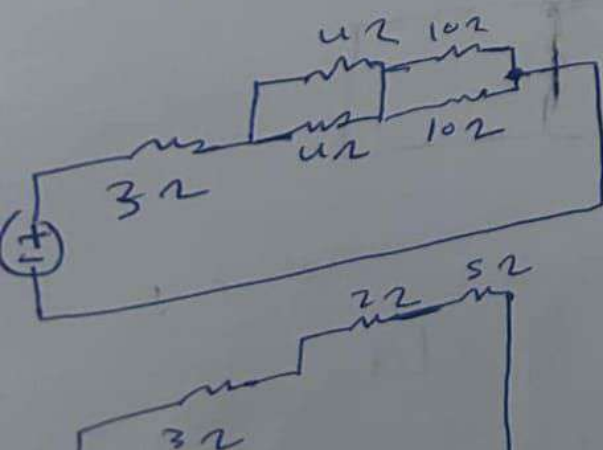
$$I = \frac{V}{R} = \frac{0.6}{20 \times 10^3} = \frac{6 \times 10^{-1}}{20 \times 10^3}$$



→

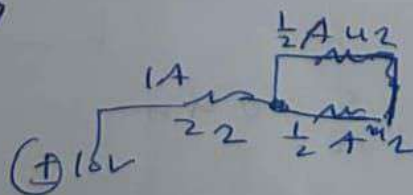

$$v_x = \frac{1}{2} (4) = 2V$$

0.3

3×10^{-5}


1.8


1.6


$$R_A = \frac{12 \times 18}{12 + 18} = 6$$

$$R_B = \frac{12 \times 6}{12 + 6 + 18} = 2$$

$$R_C = \frac{18 \times 6}{18 + 6 + 12} = 2$$

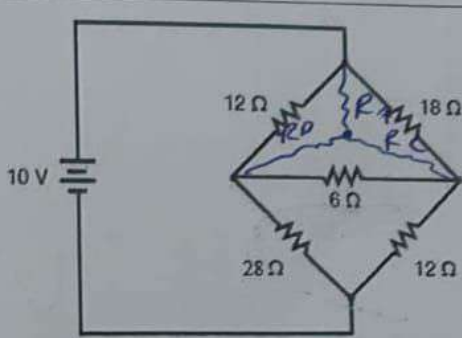Q7	Use Δ -Y transformation to find the equivalent resistance seen by the 10V source for the circuit shown.	
a.	14.62 Ω	
b.	21.6 Ω	
c.	16 Ω	
d.	76 Ω	
e.	8 Ω	

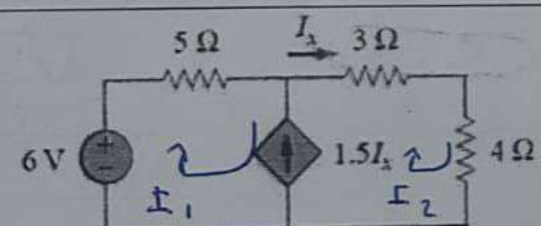Q8	For the circuit shown, the current I_x is:	
a.	0.857 A	
b.	1.33 A	
c.	0	
d.	0.5 A	
e.	1 A	

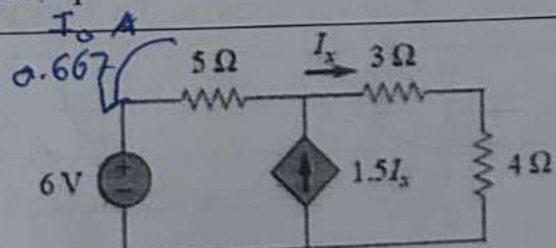Q9	For the circuit shown, the absorbed or generated power of the 6V source is:	
a.	8 W, generated	
b.	8 W, absorbed	
c.	4 W, absorbed	
d.	4 W, generated	
e.	None of these	



$$12 + 5$$

$$I_x = I_2$$

$$\frac{I}{2} = I_1 \times$$

$$-6 + 5I_1 + 7I_2 =$$

$$5I_1 + 7I_2 = 6$$

$$-I_1 + I_2 = 1.5I_x$$

$$\frac{I}{2} - I_1 = 1.5$$


$$Q. 8$$

$$I_2 = I_x$$

$$R/K/2$$

$$I_1 + I_2 = 1.5I_x$$

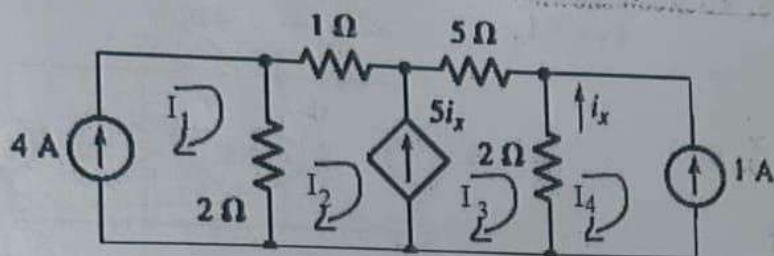** For the circuit shown, use Mesh Analysis to answer questions (13-16)



$$\frac{1}{u} = -1A$$

$$I_1 = 4A$$

$$3 \frac{I_1}{2} + \frac{I_1}{2} + \frac{I_1}{3} + \frac{I_1}{3}$$

$$2 \frac{I_2}{2} + \frac{I_2}{2} + 5 \frac{I_3}{3} + 2 \frac{I_3}{3} - \frac{I_1}{4}$$

$$2 \frac{I_2}{2} + \frac{I_2}{2} + 5 \frac{I_3}{3} + 2 \frac{I_3}{3} - 2 \frac{I_1}{4} - 2 \frac{I_1}{1} = 0$$

$$3 \frac{I_2}{2} + 7 \frac{I_3}{3} - 2(-1) - 8 = 0$$

$$3 \frac{I_2}{2} + 7 \frac{I_3}{3} + 2 - 8 = 0$$

$$\frac{I_2}{u} - I_3 = I_1$$

$$-1 - I_3 = I_1$$

$$(1) 3 \frac{I_2}{2} + 7 \frac{I_3}{3} = 6$$

$$(2) \frac{I_2}{3} - I_3 = 5i_x$$

$$I_2 - I_3 - 5i_x = 0$$

$$(3) \frac{I_2}{3} - \frac{I_1}{u} = -I_x$$

$$\frac{I_2}{3} + 1 = -I_x$$

$$(3) I_2 + I_x = -1$$

$$I_2 = 2.8$$

$$I_3 = -0.36$$

$$I_x = -0.64$$

Q13	The current I_2 is:
a.	2.17 A
b.	1.4 A
c.	6.6 A
d.	2.8 A
e.	None of these

Q14	The current I_3 is:
a.	-0.72 A
b.	-0.36 A
c.	0.36 A
d.	0.72 A
e.	None of these

Q15	The current I_4 is:
a.	-4 A
b.	1 A
c.	-1 A
d.	4 A
e.	0 A


Q16	The current i_x is:
a.	-3.2 A
b.	-0.64 A
c.	3.2 A
d.	6.4 A
e.	-6.4 A

Q1	If you replace R_x in the following circuit by a short circuit , the driven current by the source is:	
a.	0 A	
b.	0.4 A	
c.	0.1 A	
d.	0.133 A	
e.	None of these	

Q2	For the circuit shown, V_o is:	
a.	0 V	
b.	2 V	
c.	3 V	
d.	1 V	
e.	4 V	

Q3	For the circuit shown, the current through the 6- Ω resistor I is:	
a.	9 A	
b.	6 A	
c.	1.5 A	
d.	5.14 A	
e.	3 A	

$$\frac{I}{6} = \frac{9(12)}{12+6} = 6$$

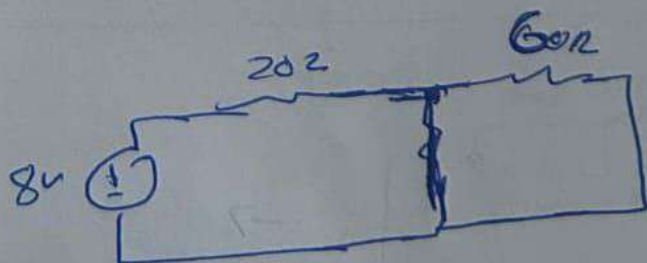

$$I = \frac{8}{20} = 0.4 \text{ A}$$

$$I = \frac{4}{4} = 1 \text{ A}$$



apply k.v.L

$$2(5I_x) + V_2 = 4$$

$$V_1 = 5I_x$$


** For the circuit shown, use Nodal Analysis to answer questions (17-20)

$$I_x = \frac{V_1}{5}$$

$$I_x = \frac{V_1}{5}$$

$$V_2 - V_1 = 0.2I_x$$

$$V_2 - 5I_x = 0.2I_x$$

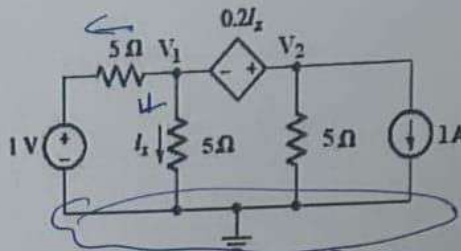

rcf

$$V_2 - V_1 = 0.2I_x$$

$$V_2 - V_1 = 0.2\left(\frac{V_1}{5}\right)$$

$$\frac{V_1 - 1}{5} + \frac{V_1}{5} = 0$$

$I_{outside}$ I_{inside}

$$\frac{V_1 - 1}{5} + \frac{V_1}{5} + \frac{V_2}{5} = 1$$

Q17	The nodal voltage V_2 is:
a.	-1.37 V
b.	1 V
c.	0.3 V
d.	-4.22 V
e.	6.75 V

Q18	The voltage at the reference point is:
a.	-1 V
b.	5 V
c.	-5 V
d.	1 V
e.	0 V

Q19	The nodal voltage V_1 is:
a.	-2.632 V
b.	2.632 V
c.	0.2 V
d.	-1.316 V
e.	1 V

Q20	The current I_x is:
a.	-3.375 A
b.	1.37 A
c.	3.375 A
d.	-0.2632 A
e.	-0.844 A

$$0.2V_1 - 0.2 + 0.2V_1 + 0.2V_2 = 1$$

$$0.2V_1 + 0.2V_1 + 0.2V_2 = 1.2$$

$$0.4V_1 + 0.2V_2 = 1.2$$

$$V_2 - V_1 = 0.2\left(\frac{V_1}{5}\right)$$

$$V_2 - V_1 = 0.04V_1$$

$$V_2 - V_1 = 0.04V_1$$

$$-1.04V_1 + V_2 = 0$$

$$I_x = \frac{V_1}{5}$$

$$V_1 - 1 + V_1 + V_2 = 5$$

$$2V_1 + V_2 = 6$$

$$V_2 - V_1 = 0.2\left(\frac{V_1}{5}\right)$$

$$V_1 = 5I_x$$

$$0.2V_2 - 0.2V_1 = \frac{V_1}{5}$$

$$10I_x + V_2 = 4$$

$$5.2I_x - 0.2V_1 = 0.2V_1$$

$$\frac{V_1 - 1}{5} + \frac{V_1}{5} + \frac{V_2}{5} = 1$$

$$V_1 + 1 + V_1 + V_2 = 5$$

$$2V_1 + V_2 = 4$$

$$2V_1 + V_2 = 4$$

Q10	For the circuit shown, the absorbed power in the 3k ohm resistor	
a.	3.333 μ W	
b.	33.3 mW	
c.	900 W	
d.	300 W	
e.	30 W	

Q11	If you replace R_x in the following circuit by an open circuit, the driven current by the source is:	
a.	0 A	
b.	0.1 A	
c.	8 A	
d.	0.133 A	
e.	0.4 A	

Q12	For the circuit shown, the voltage across the 6 Ω resistor is:	
a.	-6 V	
b.	6 V	
c.	10 V	
d.	4 V	
e.	-4 V	

$$\sum I_{in} = \sum I_{out} \text{ at node 2}$$

$$q_{10}$$

$$P = I^2 R$$

$$I = \frac{10}{10} = 1$$

$$V = IR = 1/6$$

$$= 3 \times 10^3 \times 6.11^2$$

$$= 30W$$

$$V_2 = 1/2 \times 10 = 5$$

$$V_2 = 30 = 0$$