


Question 4

(4 Marks)

For the circuit shown in Figure 6, use mesh current analysis to find

3

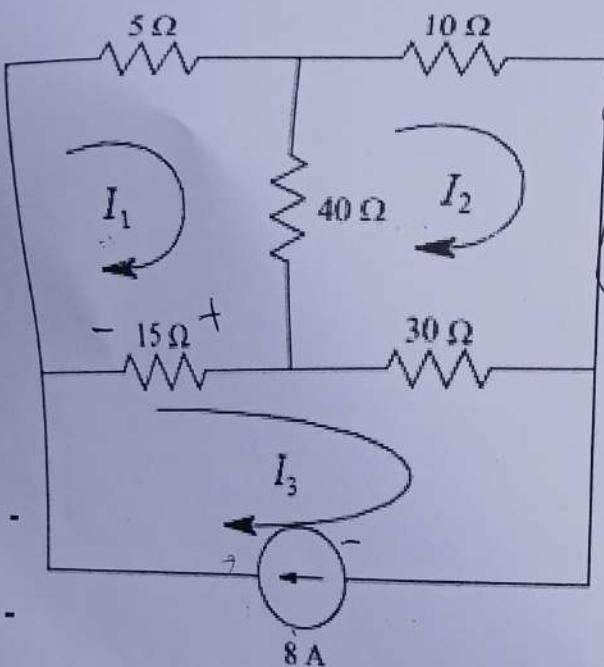a- The mesh currents I_1 , I_2 , and I_3
 b- The current through the $30\ \Omega$ resistor.
 c- The power dissipated by the $15\ \Omega$ resistor.



at mesh ①

$$60I_1 + 40I_1 + 15I_1 + 5I_1 - 40I_2 - 15I_3 = 0$$

$$60I_1 - 40I_2 - 15I_3 = 0$$

at mesh ②

$$10I_2 + 30I_2 + 40I_2 - 40I_1 - 30I_3 = 0$$

~~$$80I_2 - 40I_1 = 0$$~~

at mesh ③ =
I₃ = 8

~~$$60I_1 - 40I_2 = 120$$~~

~~$$80I_2 - 40I_1 = 240$$~~

~~$$I_3 = 8$$~~

~~$$I_1 = 6\ A$$~~

~~$$I_2 = 6\ A$$~~

~~$$I_3 = 8\ A$$~~

$$\begin{aligned} P_{(15\ \Omega)} &= I V \\ &= I (I R) \\ &= (6)(6 \cdot 15) \end{aligned}$$

~~$$\textcircled{a} \quad P_{(30\ \Omega)} = 8 \cdot 30 \text{ W}$$~~

$$I_{(30\ \Omega)} = I_3 - I_2$$

$$8 - 6$$

~~$$I_{(30\ \Omega)} = 2\ A$$~~

b- In Figure. 4, Find I_o/I_s


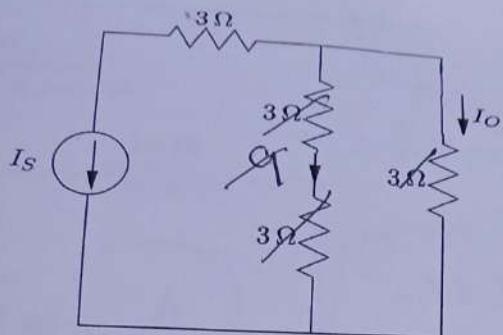


Figure 4:

$$I_s \Rightarrow I_o \times \frac{1}{3}$$
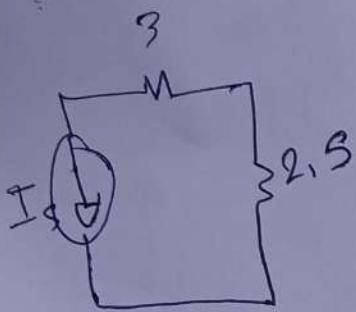
$$\frac{1}{2\sqrt{3}} + \frac{1}{6} + \frac{1}{2\sqrt{3}}$$



$$I = I_o$$

$$I_s = I_o \times \frac{1}{3} = I_s = I_o \times \frac{1}{3}$$

~~$$I_s = \frac{I_o}{3}$$~~

~~$$0.5$$~~

~~$$\frac{5}{6}$$~~

~~$$I_s = \frac{6 I_o \times \frac{1}{3}}{5}$$~~

~~$$I_s = \frac{6 I_o}{5}$$~~

~~$$I_s = \frac{6 I_o}{5}$$~~

~~$$I_s = \frac{6 I_o}{5}$$~~

c- In the circuit shown in Figure. 5. Find V_o

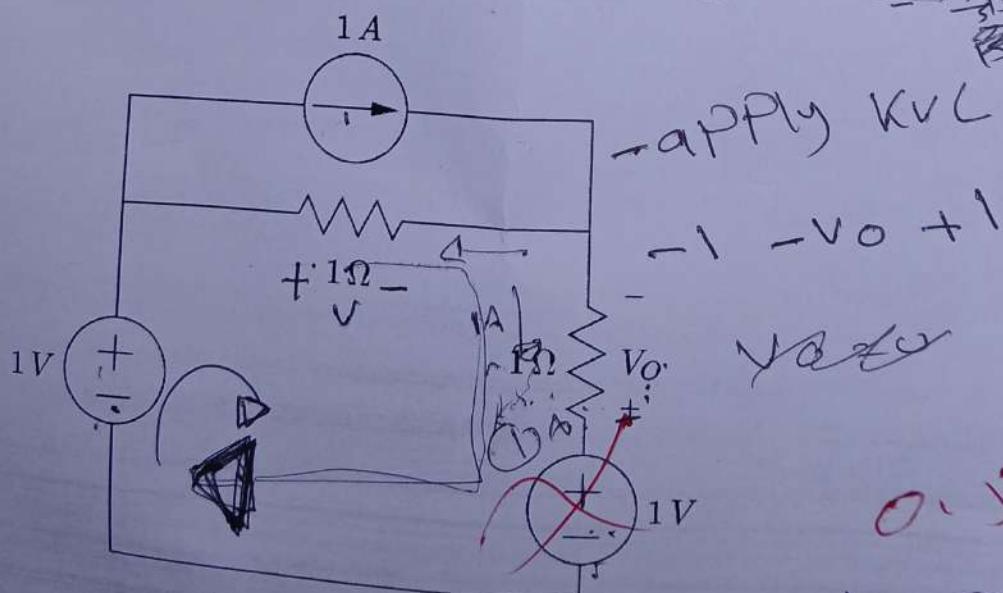


Figure 5:

$$I = \frac{V}{R} = \frac{1}{1} = 1$$


Question: 3

(6 Marks)

This question consist of 3 parts (2 marks each)


a- The equivalent resistance at the terminals a-b for the circuits shown in Figure. 3 is equal to

3

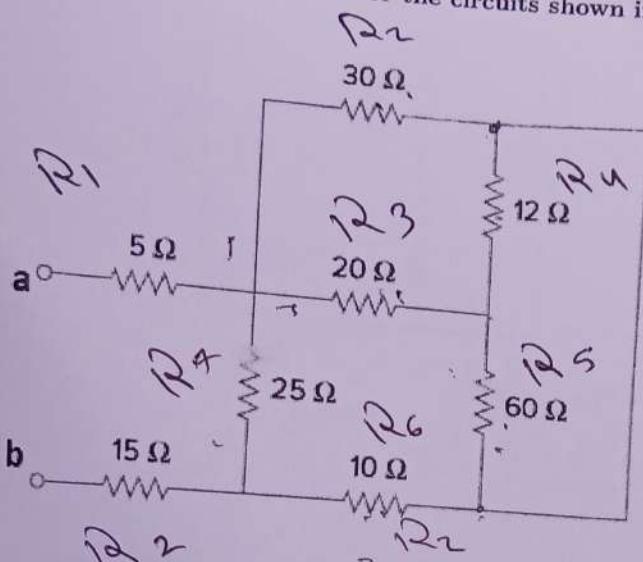


* $R_4 | R_5$ ~~Series~~ Parallel

$$R_{45} = \frac{12 \times 60}{72} =$$

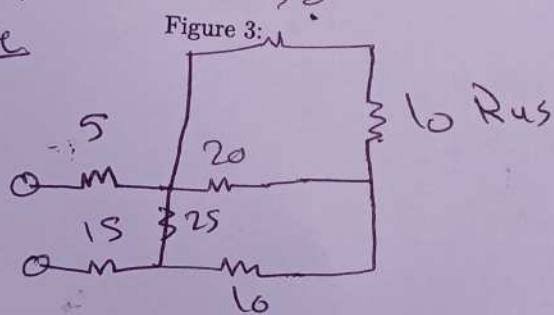

* R_{45}, R_2 series




$$80 + 10 = 90$$

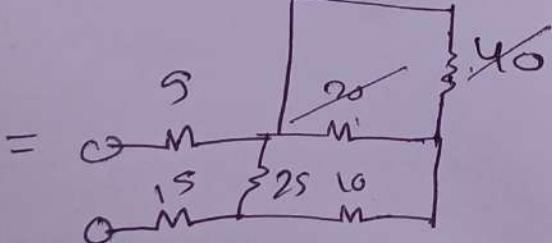

2

* R_{452}, R_3 ~~Series~~

$$\frac{90 \times 20}{60} = 13.33$$

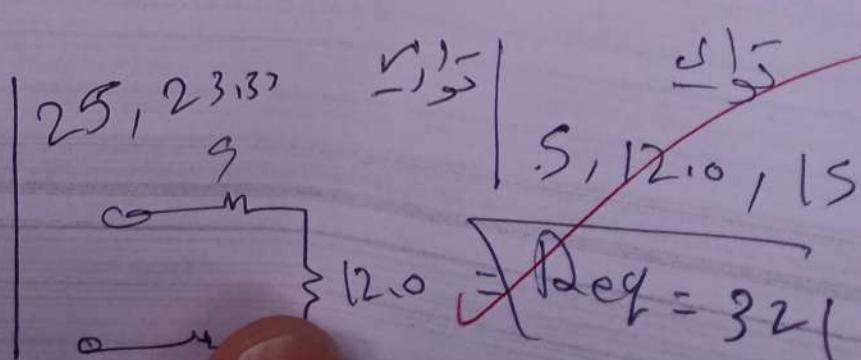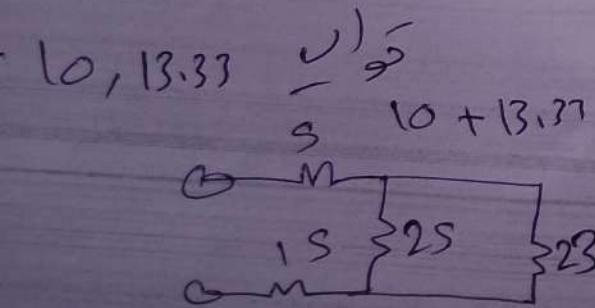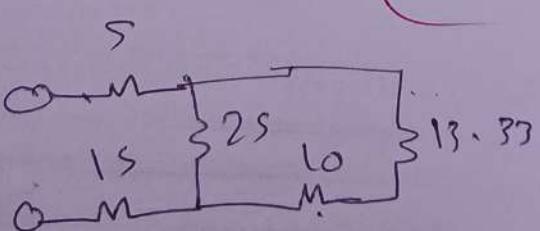


~~$R_{eq} = 32$~~

Question 2:

For the circuit shown in figure 2, Use the Nodal analysis method to find
 a-The nodal voltages, V_1 and V_2 .
 b-The current i_3 .
 c-The power absorbed/ supplied by the current source.

(6 marks)

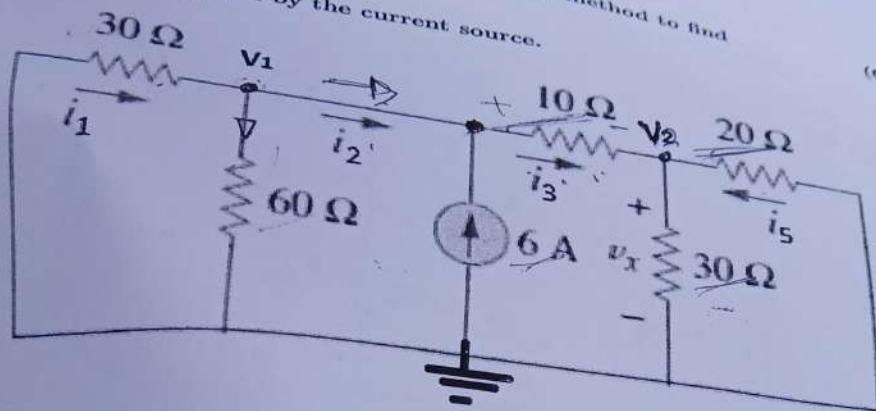

at Node V_1 : $\Sigma I_{in} = \Sigma I_{out}$ Figure 2:

$$\frac{V_1}{30} = \frac{V_0}{60} + \frac{V_1 - V_2}{10} = \frac{V_1}{60} + \frac{6 \times V_1 - 6 \times V_2}{6 \times 10} - \frac{2 \times V_1}{2 \times 30} = \frac{V_1}{60} + \frac{6V_1 - 6V_2 - 2V_1}{60}$$

$$\text{at Node } V_2 = \frac{V_1 - V_2}{10} + \frac{V_2}{20} = \frac{V_2}{20} \quad \Rightarrow \quad \frac{5V_1 - 6V_2}{60} =$$

$$= \frac{6V_1 - V_2}{6 \times 10} + \frac{3V_2}{3 \times 20} - \frac{2V_2}{2 \times 30} = 0$$

$$\frac{6V_1 - 6V_2 + 3V_2 - 2V_2}{60} = \frac{6V_1 - 5V_2}{60}$$

$$2 = 2V + I_2$$

Question: 1

(4 Marks)

For the circuit shown in Figure 1 Find,

a- The mesh currents, I_1 and I_2

b- The voltage V across the current source


$$I = \frac{V}{2\Omega}$$

$$I_1 = \frac{20}{2 + 1/3}$$

$$I_1 = 2A$$

$$I_2 = -2A$$
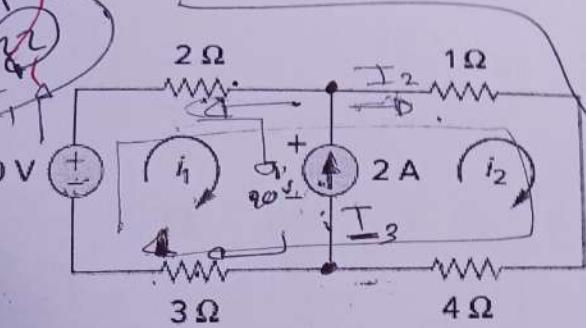
$$b) \text{ Voltage } V = V_0 = \frac{4 \times 3}{3} = 20 = V_0$$




Mesh(1):

$$-20 + I_2 + 2 + 3I_1 - 2 = 2I_1 + 3I_2 =$$


$$\text{Mesh(2)} = 2 + I_2 + 4I_2 - 2$$

$$\text{Supermesh} = 20 + 2I_1$$

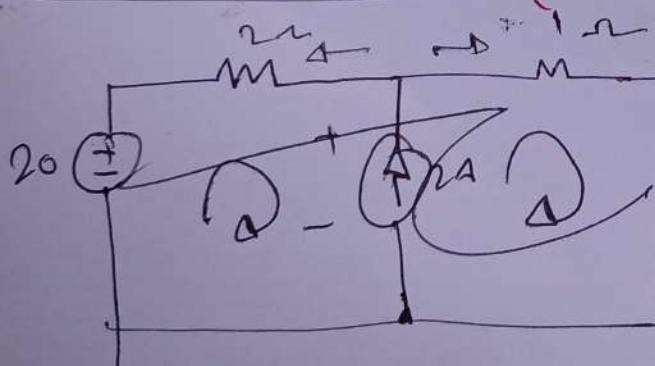

$$\text{at mesh(1)} \\ -20 + 2I_1 - 2 + 3I_1 - 2 =$$
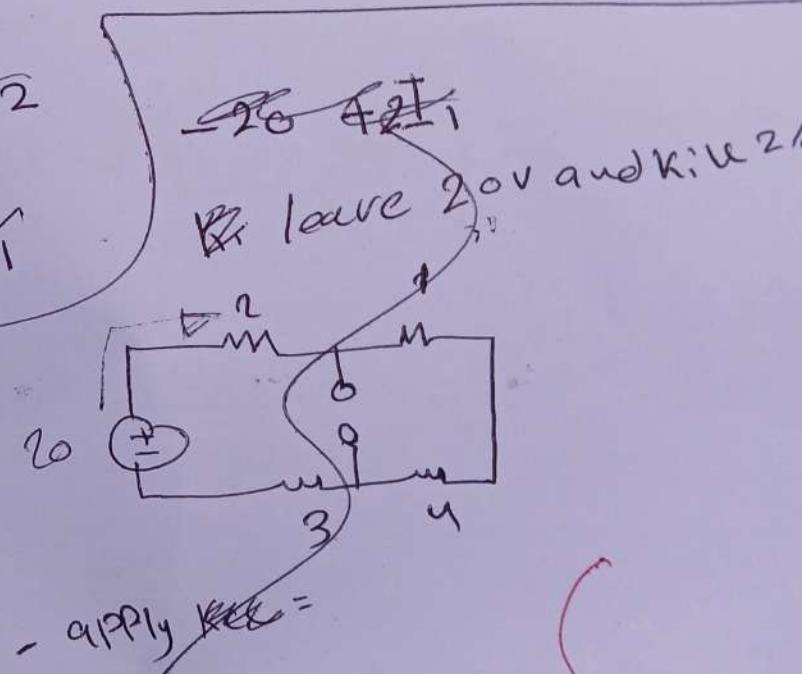
$$\text{at mesh(2)} \\ + 2 + I_2 + I_2 =$$



$$- \text{apply KCL} = \\ V = IR \\ = IER$$

$$2 = I(2 + 1 + 3 + 4)$$

$$2/10 = I/10 \\ I = 0.2$$

$$I = 0.2$$