

EE373-Electrical Machines

Topic 2: Transformers



Topic 2: Transformer

LEARNING GOALS

Introduction

Construction and Principle of Operation

1. Basic Component

1. Two winding theory
2. Ideal transformer
3. Impedance Transfer

Practical Transformer

1. Equivalent Circuit
2. Referred & Approximate Equivalent Circuit
3. Analysis of Transformer

Equivalent Circuit Parameters

1. Open-Circuit Test
2. Short-Circuit Test

Multi-secondary windings

Autotransformer

Voltage Regulation


Efficiency

Introduction

A transformer is an electrical device that transfers energy from one electrical circuit to another by magnetic coupling but without any moving parts.

- Its action is based on the laws of electromagnetic induction.
- There is no electrical connection between primary and secondary.
- There is no change in frequency.
- The ac power is transferred from primary to secondary through magnetic flux.
- Transformer has no moving parts.
- Rugged and durable in construction.
- High efficiency as well as 99%.
- Transformers alone cannot do the following:
 1. Convert DC to AC or vice versa
 2. Change the voltage or current of DC
 3. Change the frequency (the "cycles") of AC.

Introduction

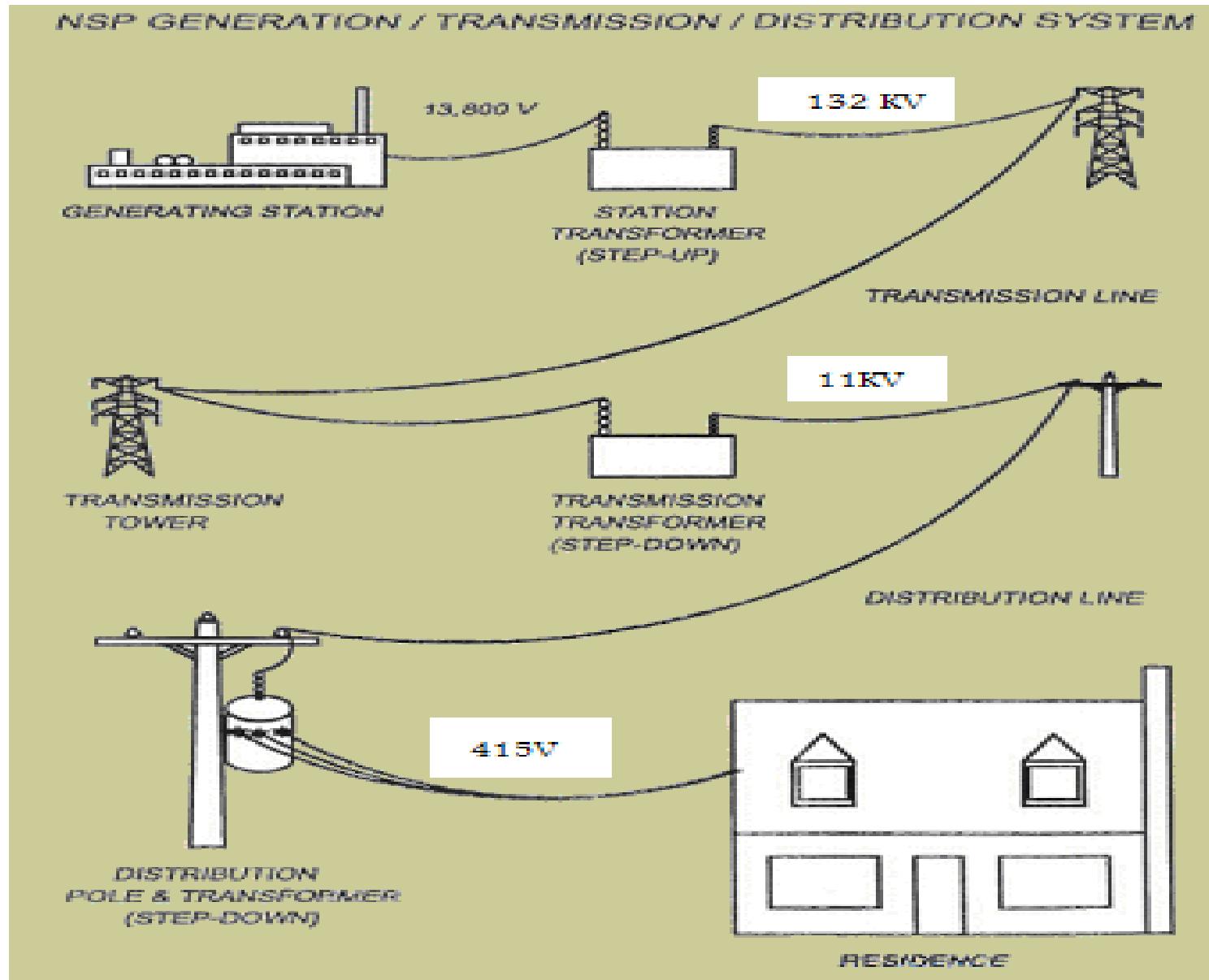

Transmission Transformer



220 KV – 1MV

161 kV Primary Delta-13.8 kV Secondary WYE, (47MVA), Transformer at the SNS site, Oak Ridge, Tennessee, USA.

Distribution Transformer





5 KV – 220 KV

Service Transformer




11 KV – 415V

Circuit Transformer

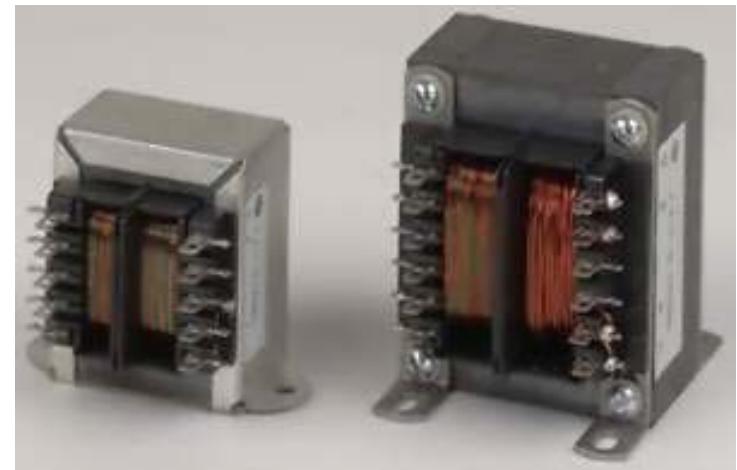
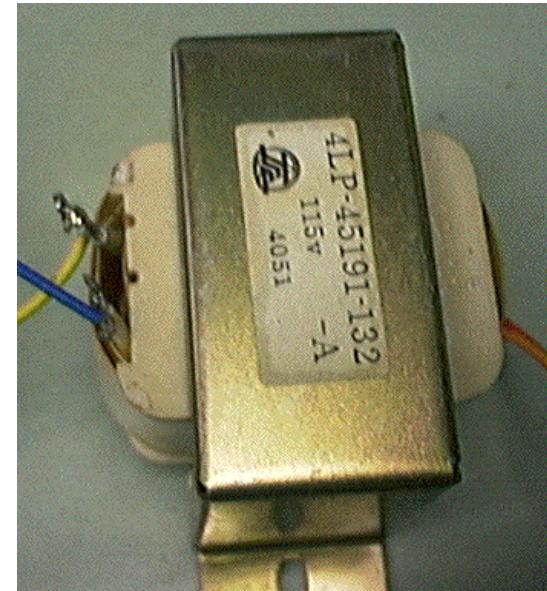


Basic Components

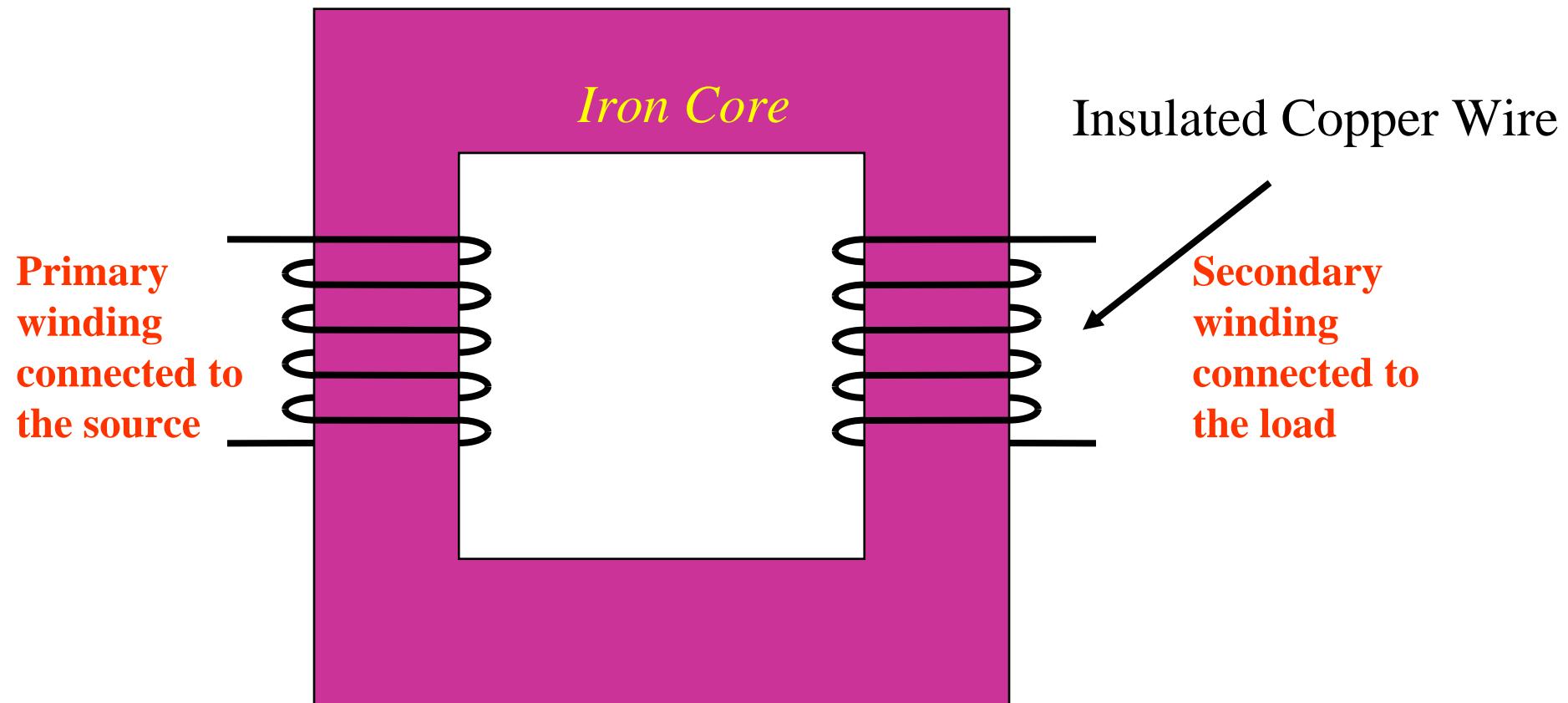


Both coils are electrically separated but magnetically linked through a low reluctance path (Iron Core)

Basic Components

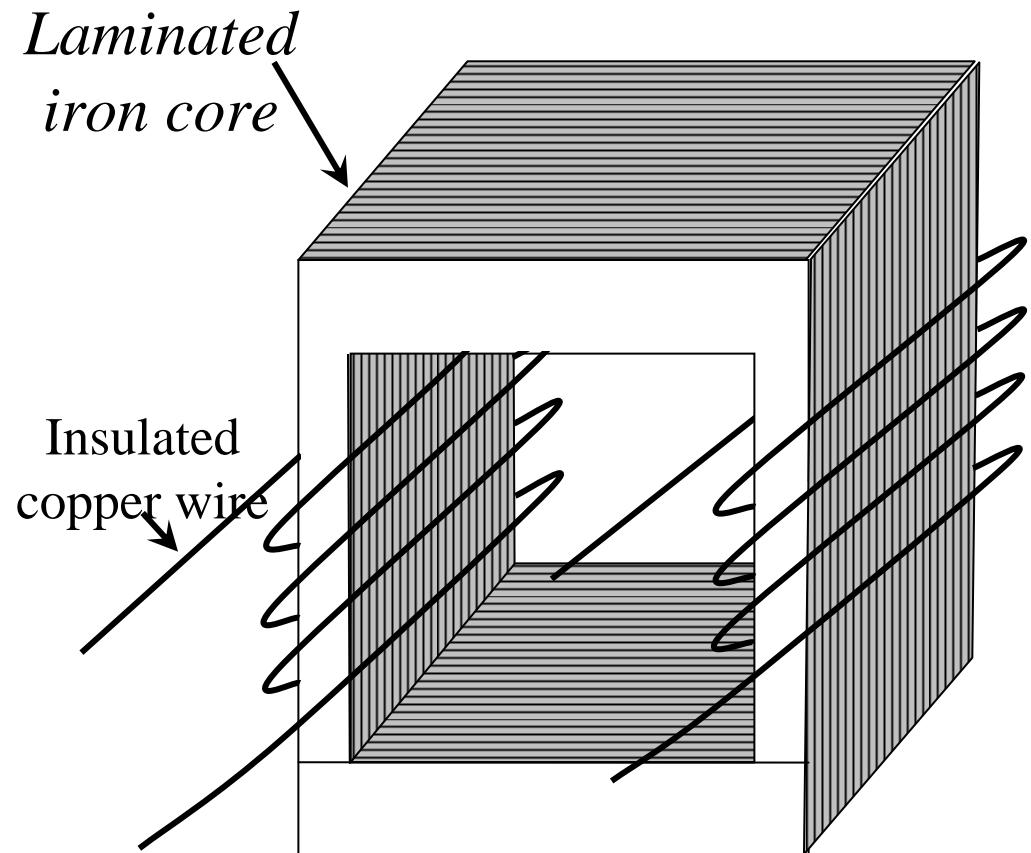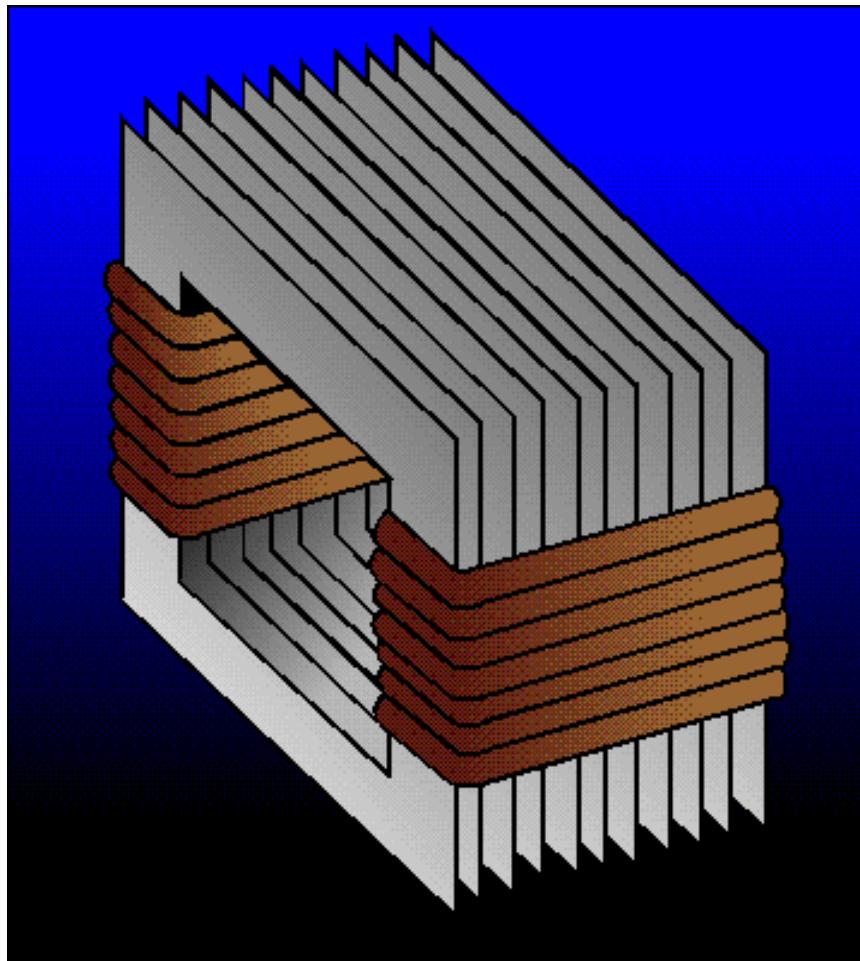

The Two-Winding Theory

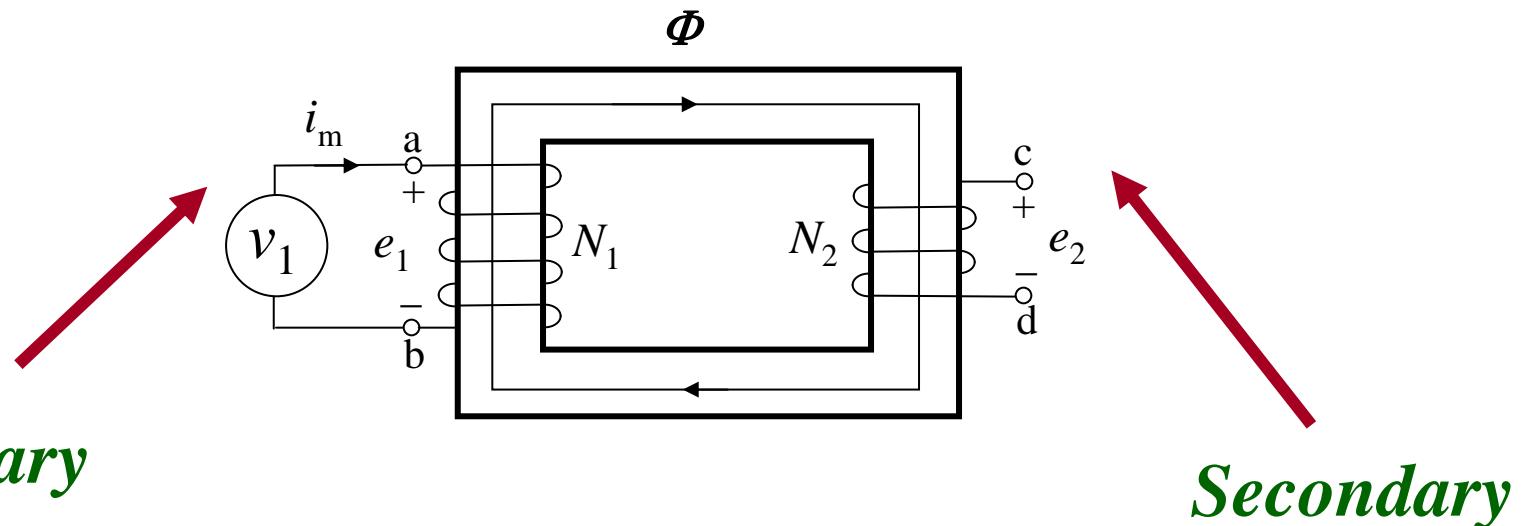

Primary

Secondary

$$e_1 = N_1 \frac{d\phi}{dt}$$

$$e_2 = N_2 \frac{d\phi}{dt}$$

If the flux varies sinusoidally, $\phi = \Phi_m \sin \omega t$ then,


$$e_1 = \omega N_1 \Phi_m \cos \omega t = \sqrt{2} E_1 \cos \omega t$$

E_1 is the root-mean-square value

The Two-Winding Theory (cont.)

$$E_1 = \frac{N_1 \Phi_m \omega}{\sqrt{2}} = \frac{2\pi f}{\sqrt{2}} \Phi_m N_1 = 4.44 f \Phi_m N_1$$

$$E_2 = 4.44 f \Phi_m N_2$$

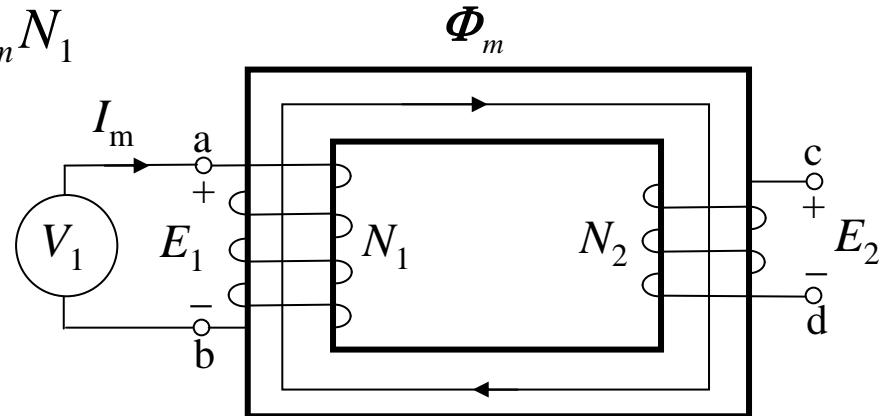

E_1 and E_2 are root-mean-square values


$$\frac{E_1}{E_2} = \frac{N_1}{N_2} = a = \text{turns ratio}$$

- *Voltages are in phase (no phase shift)*
- *Voltage magnitudes vary with turns ratio.*

Ideal Transformer at No-Load

Ideal Transformer

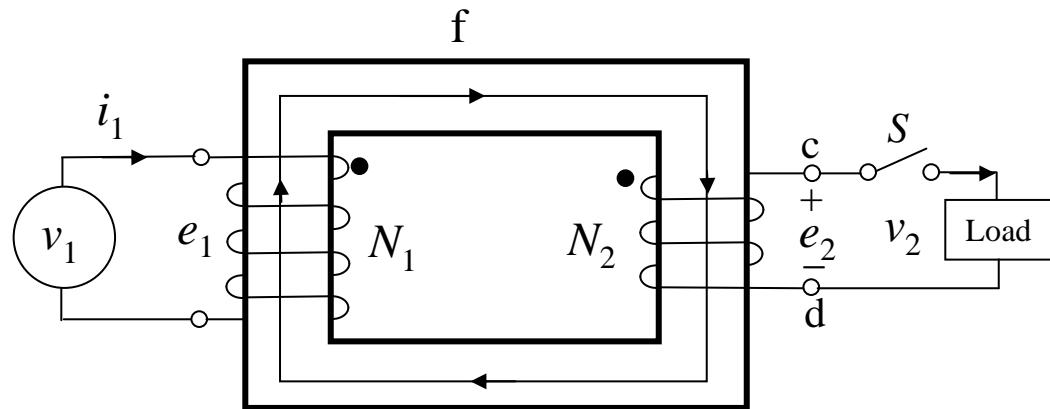- $r_1 \approx r_2 \approx 0$
- No leakage flux \Rightarrow core losses are negligible
- $\mu \approx \infty$ (high permeability)
 \Rightarrow exciting current = 0



$$v_1 = e_1 = N_1 \frac{d\phi}{dt}$$


$$v_2 = e_2 = N_2 \frac{d\phi}{dt}$$

$$\frac{v_1}{v_2} = \frac{e_1}{e_2} = \frac{N_1}{N_2} = a \text{ (turns ratio or transformer ratio)}$$

Ideal Transformer Under Load

$$S_1 = S_2$$
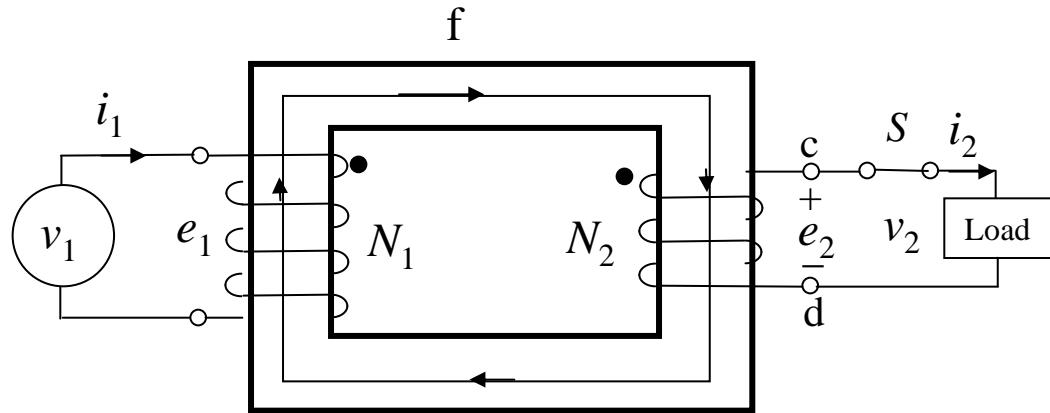
$$\bar{E}_1 \bar{I}_1^* = \bar{E}_2 \bar{I}_2^*$$




$$\frac{\bar{I}_1^*}{\bar{I}_2^*} = \frac{\bar{E}_2}{\bar{E}_1} \rightarrow \boxed{\frac{I_1}{I_2} = \frac{E_2}{E_1} = \frac{N_2}{N_1}} \rightarrow N_1 I_1 = N_2 I_2$$

- *Currents are in phase.*
- *Current ratio is opposite to the voltage ratio*

Impedance Transfer

$$\text{Secondary impedance} = Z_2 = \frac{V_2}{I_2}$$
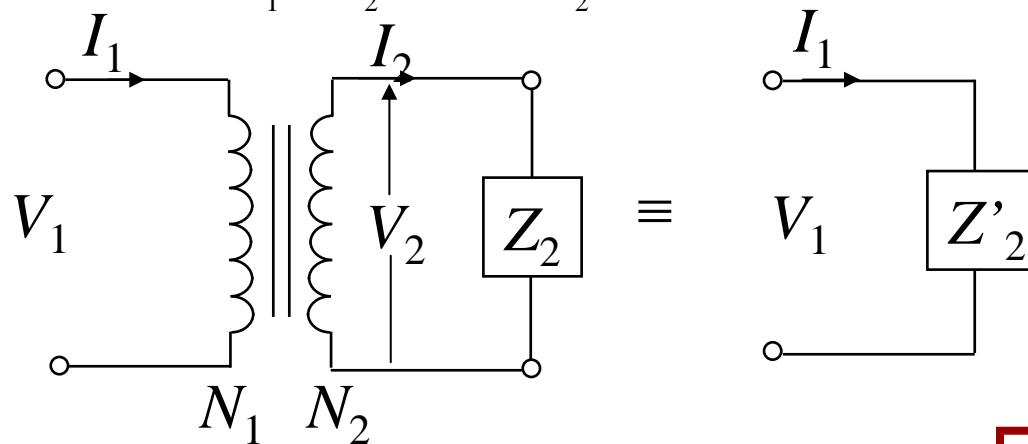
$$\text{Primary impedance} = Z_1 = \frac{V_1}{I_1} = \frac{aV_2}{I_2/a} = a^2 \frac{V_2}{I_2} = a^2 Z_2 \quad \text{where } a = \frac{N_1}{N_2}$$



Secondary impedance is transferred to the primary side


$$\rightarrow Z'_2 = Z_1 = a^2 Z_2$$

Primary impedance is transferred to the secondary side

$$\rightarrow Z'_1 = Z_2 = \frac{1}{a^2} Z_1$$

This impedance transfer is very useful because it eliminates a coupled circuit in an electrical circuit and thereby simplifies the circuit.

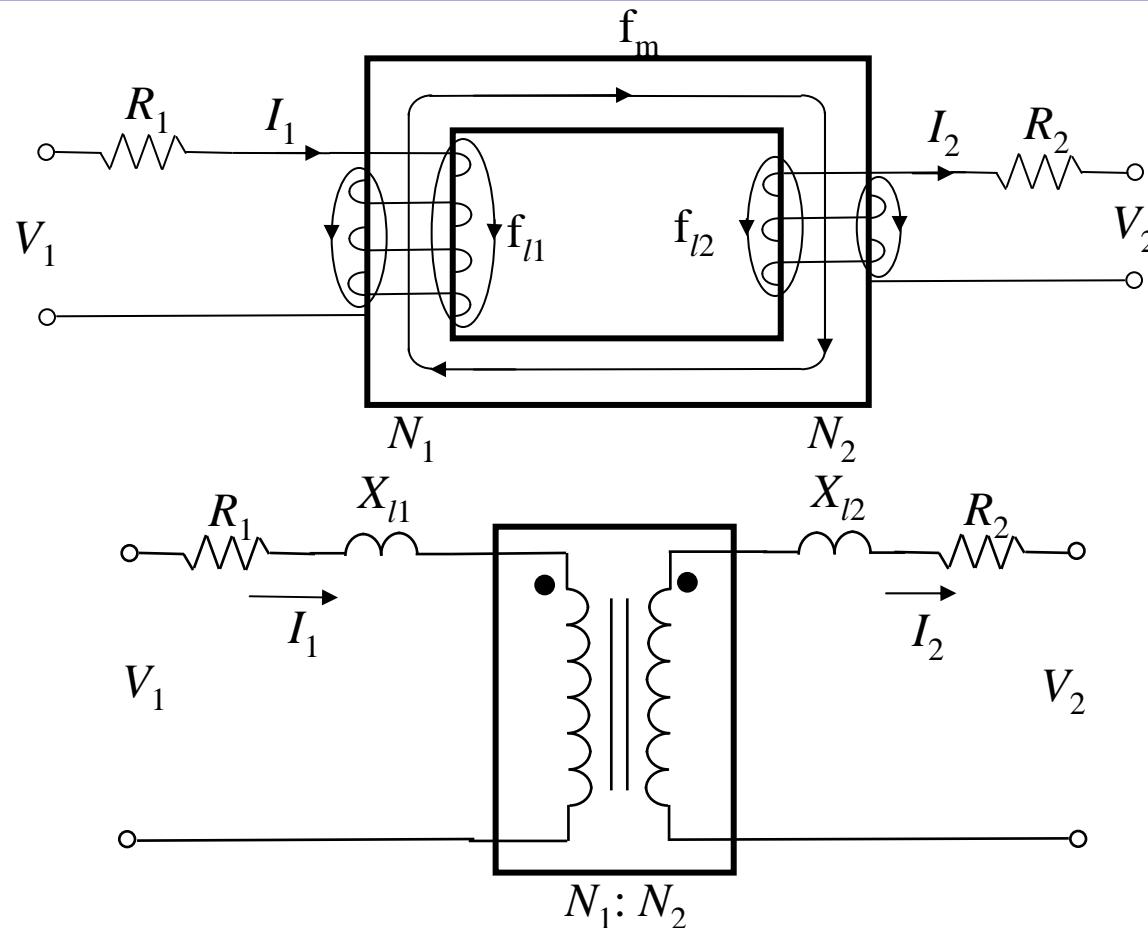Equivalent Circuit: Practical Transformer




R_1 & R_2 : the resistance of the primary and secondary winding

$$X_{l1} = 2\pi f L_{l1} = \text{leakage reactance of winding 1} \Rightarrow L_{l1} = \frac{N_1 \Phi_{l1}}{I_1} = \text{leakage inductance of winding 1}$$

$$X_{l2} = 2\pi f L_{l2} = \text{leakage reactance of winding 2} \Rightarrow L_{l2} = \frac{N_2 \Phi_{l2}}{I_2} = \text{leakage inductance of winding 2}$$


Equivalent Circuit: Practical Transformer

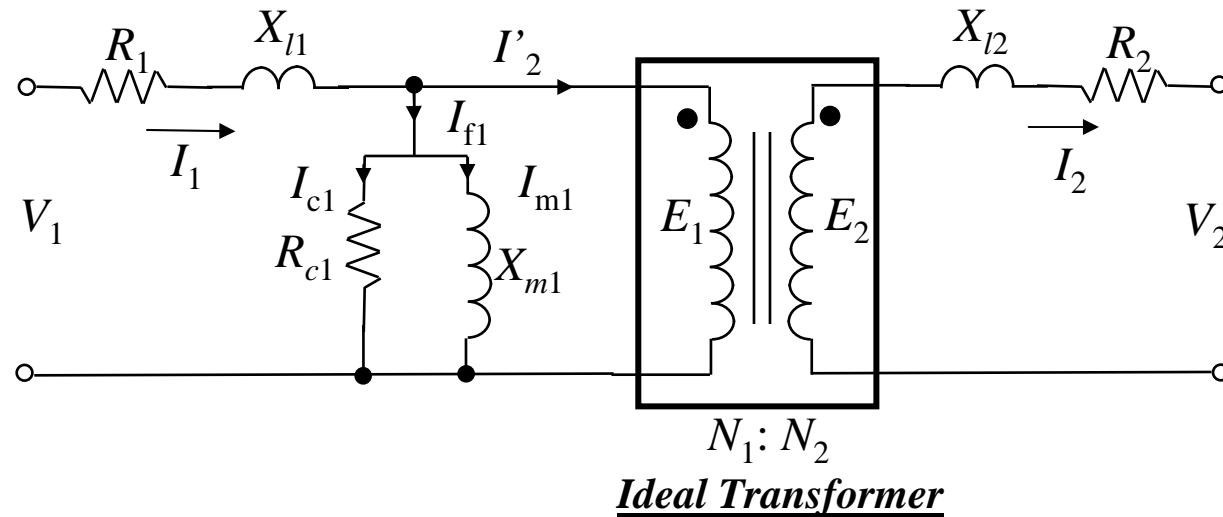- ❖ In practice I_m is required to establish flux f_m in the core.
=> This effect can be represented by a magnetizing inductance L_m .
- ❖ The core loss can be represented by a resistance R_c .



A practical transformer is equivalent to an ideal transformer + external impedances that represent imperfections of an actual transformer.

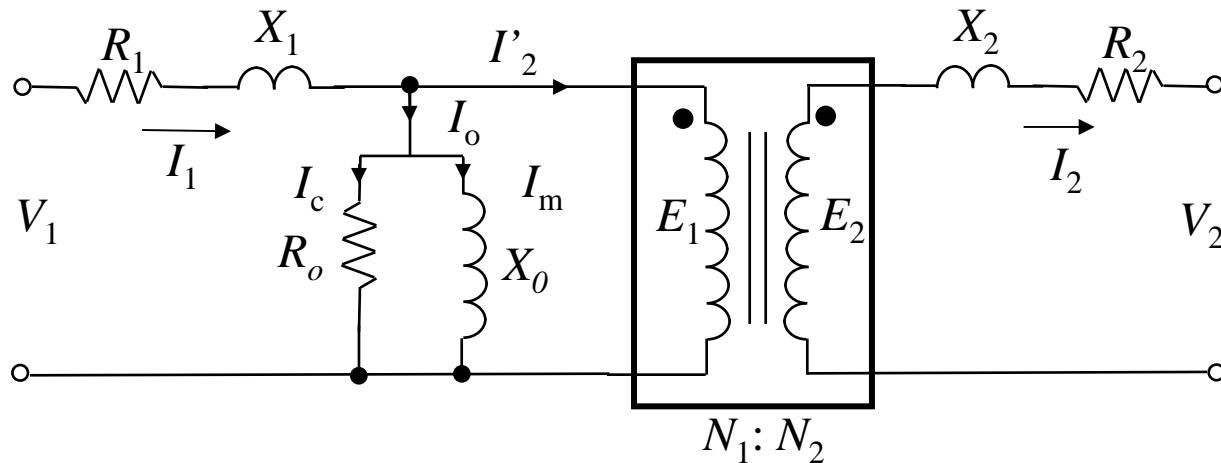Equivalent Circuit: Practical Transformer



$$\bar{V}_1 = \bar{E}_1 + \bar{I}_1 (R_1 + jX_1)$$

$$\bar{E}_2 = [\bar{V}_2 + \bar{I}_2 (R_2 + jX_2)]$$

$$\bar{V}_1 = \bar{E}_2 \frac{N_1}{N_2} + \bar{I}_1 (R_1 + jX_1)$$

$$\bar{V}_1 = [\bar{V}_2 + \bar{I}_2 (R_2 + jX_2)] \frac{N_1}{N_2} + \bar{I}_1 (R_1 + jX_1)$$

$$but \quad I_2 = I'_2 \left(\frac{N_1}{N_2} \right)$$

$$\bar{V}_1 = \left[\bar{V}_2 \frac{N_1}{N_2} + I'_2 \left(\frac{N_1}{N_2} \right)^2 (R_2 + jX_2) \right] + \bar{I}_1 (R_1 + jX_1)$$


$$\bar{V}_1 = \left[\bar{V}_2' + I'_2 (R'_2 + jX'_2) \right] + \bar{I}_1 (R_1 + jX_1)$$

$$R'_2 = R_2 \left(\frac{N_1}{N_2} \right)^2$$


$$X'_2 = X_2 \left(\frac{N_1}{N_2} \right)^2$$

$$V'_2 = V_2 \left(\frac{N_1}{N_2} \right)$$

Referred Equivalent Circuit

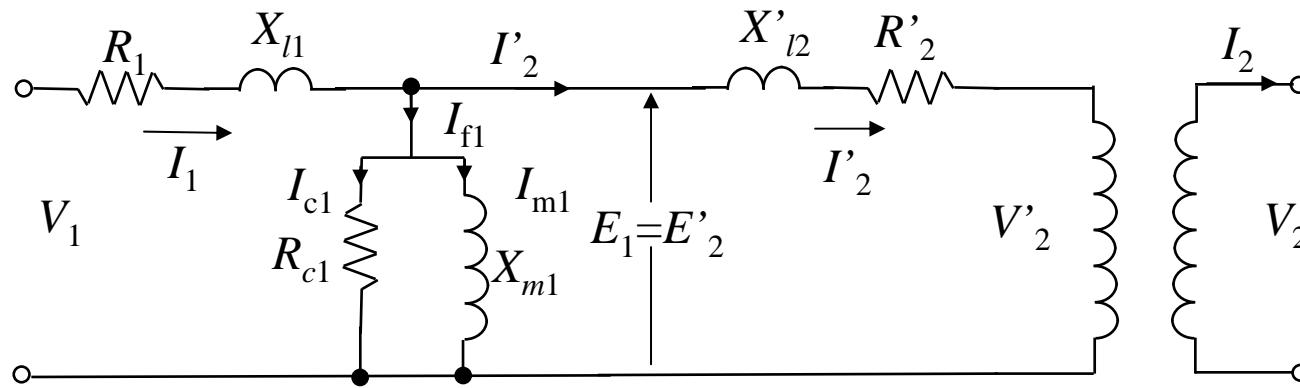

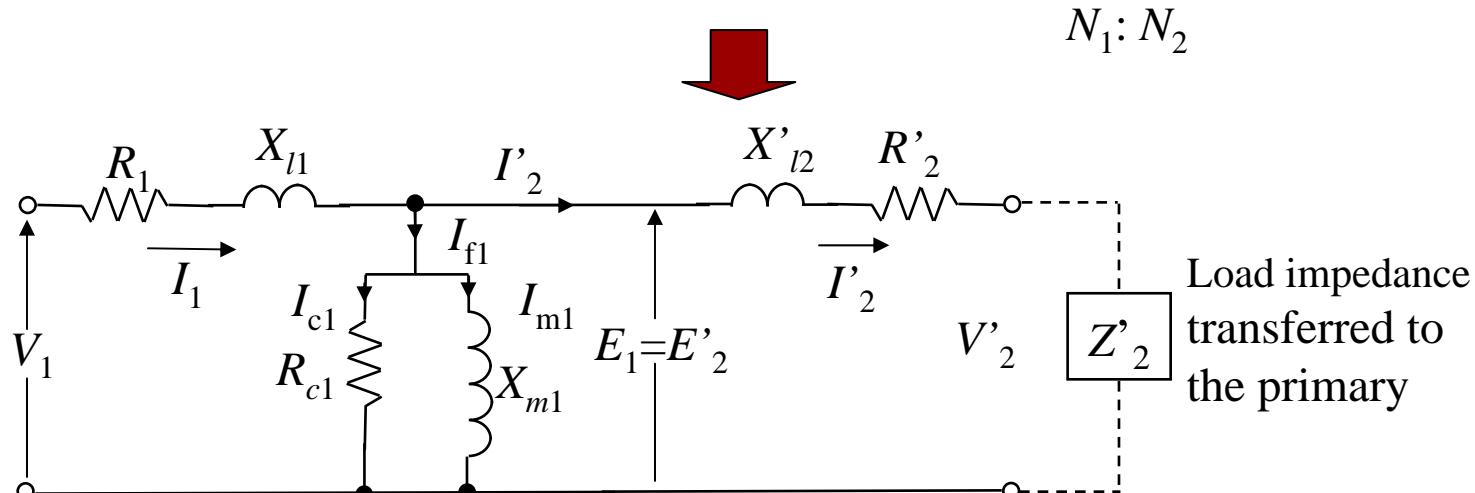
$$\begin{aligned}E_1 &= E_2 = aE_2 \\V_2 &= aV_2 \\I_2 &= I_2 / a \\X_{l2} &= a^2 X_{l2} \\R_2 &= a^2 R_2\end{aligned}$$




Transformer Equivalent Circuit

Approximate Equivalent Circuit


$I_1 R_1$ and $I_1 X_{l1}$ are very small compared to $V_1 \Rightarrow |E_1| \approx |V_1|$

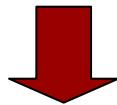

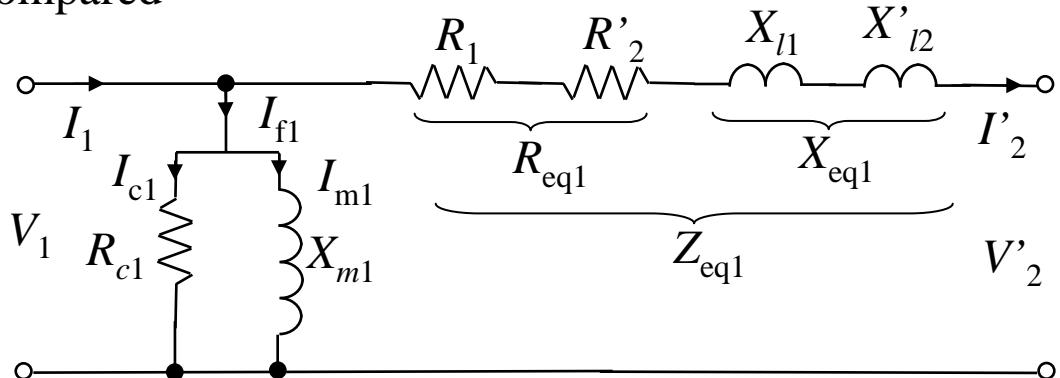Shunt branch can be moved to the supply terminal



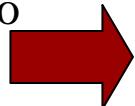
$I_{\phi 1}$ is also very small compared to I_1
 $I_{\phi 1} \leq 5\% \times I_1 \Rightarrow$ it's possible to remove the shunt branch.




$$R_{eq2} = \frac{R_{eq1}}{a^2} = R_2 + R'_1$$

$$X_{eq2} = \frac{X_{eq1}}{a^2} = X_{l2} + X'_{l1}$$
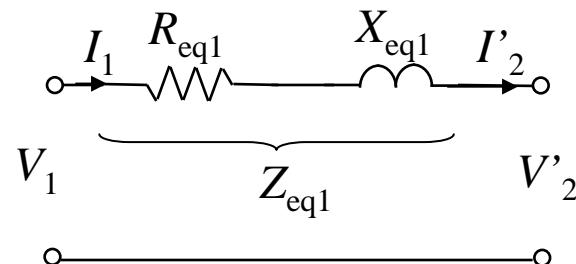
$$V'_1 = \frac{V_1}{a} \quad , \quad I'_1 = I_2 = aI_1$$



Referred to Primary


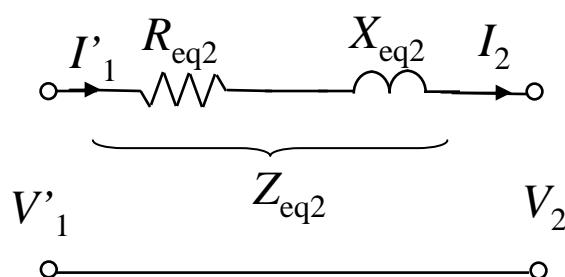


Referred to Secondary

The magnetization current in a real transformer


Even when no load is connected to the secondary coil of the transformer, a current will flow in the primary coil. This current consists of:

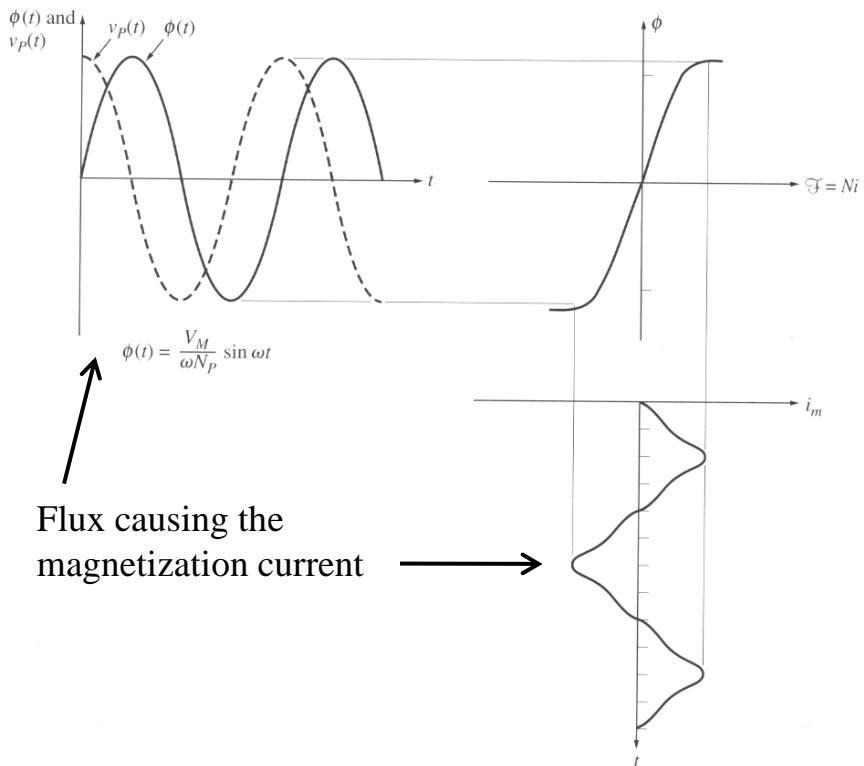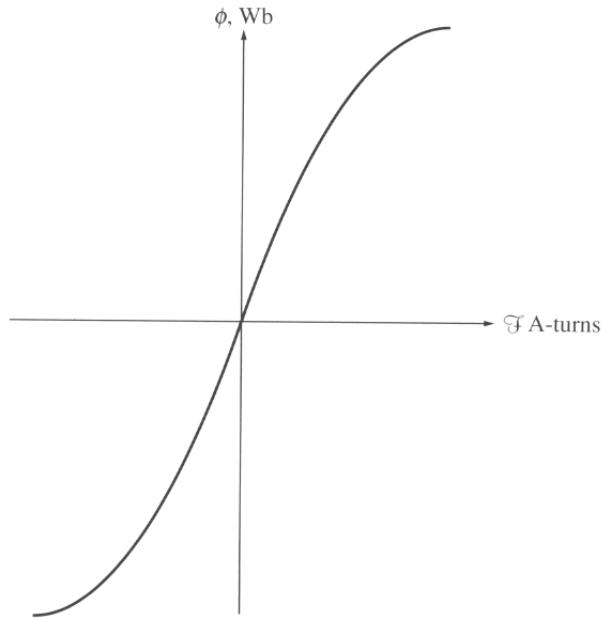1. The magnetization current i_m needed to produce the flux in the core;
2. The core-loss current i_{h+e} hysteresis and eddy current losses.




Typical magnetization curve

Analysis of Transformer

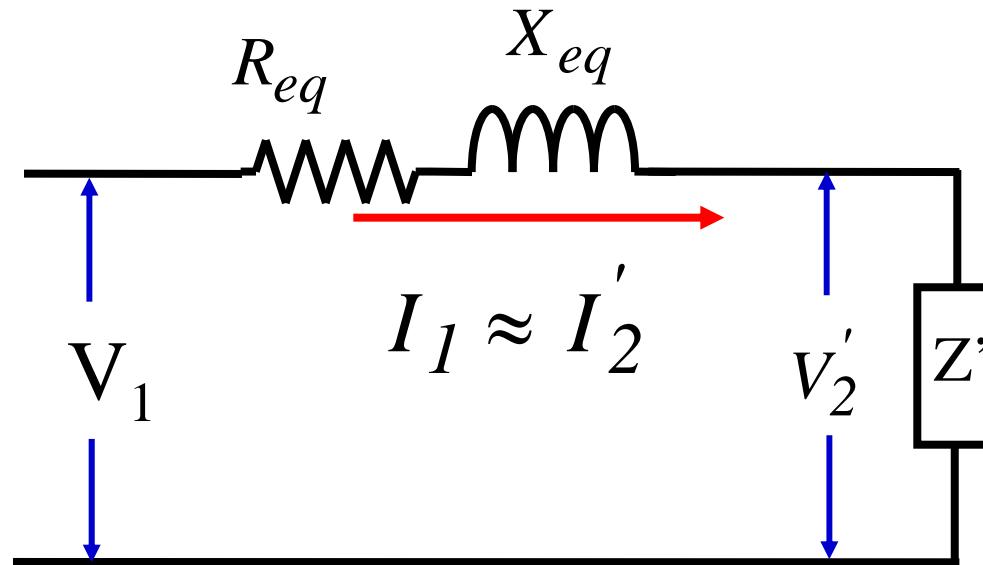


$$\bar{V}_1 = \bar{V}_2' + \bar{I}_2' (R_{eq} + jX_{eq})$$


Analysis of Transformer

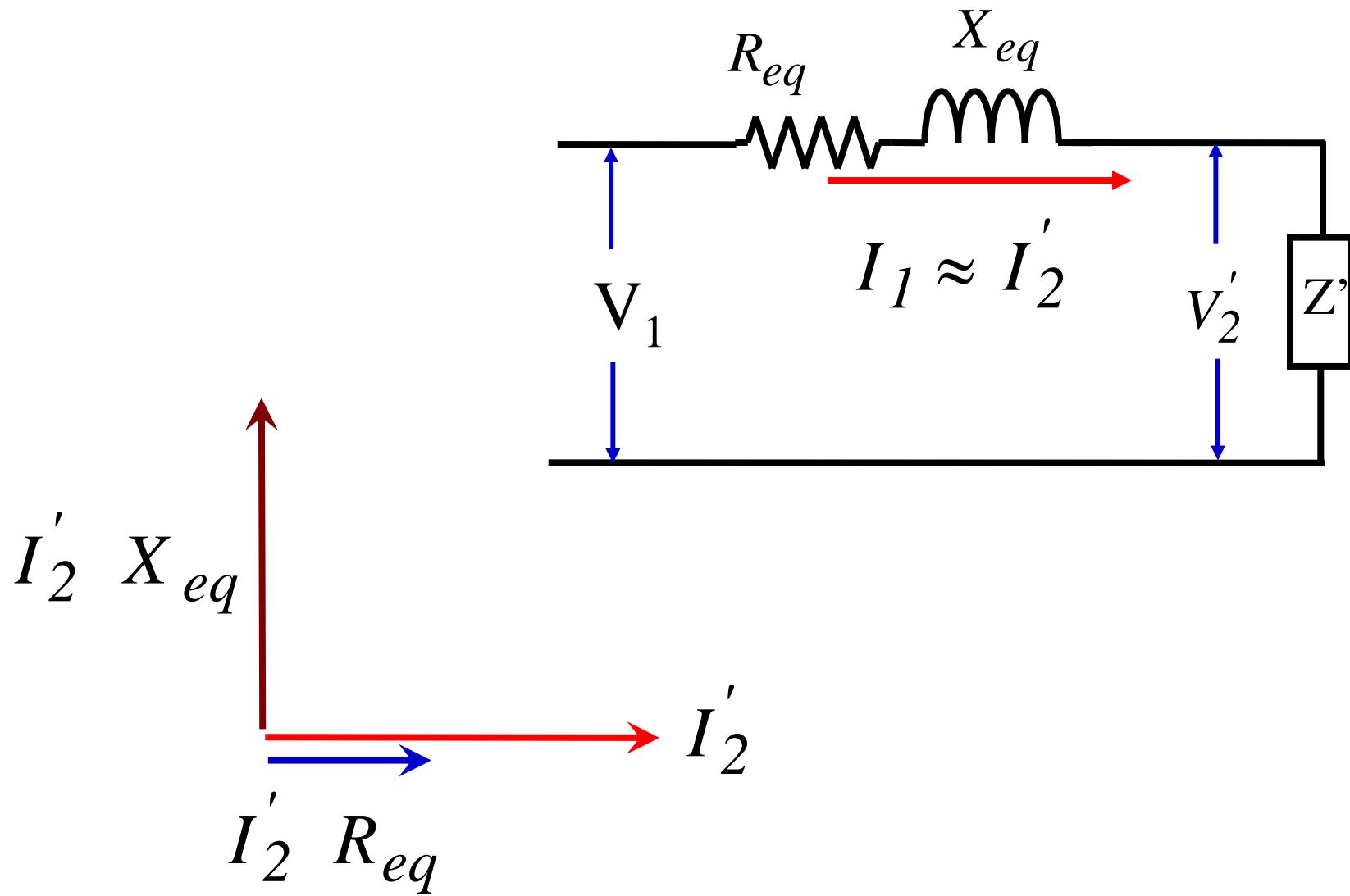

Analysis of Transformer

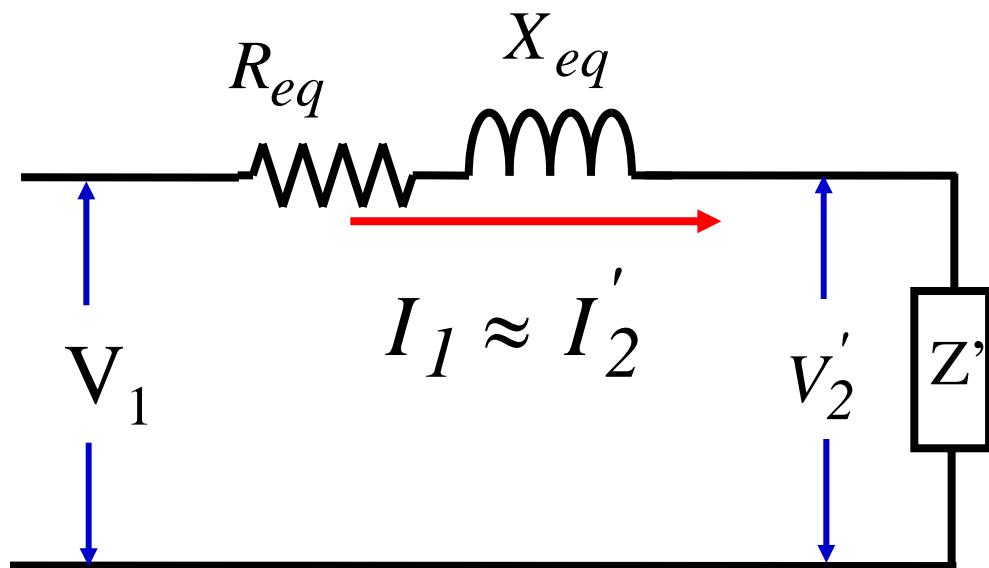

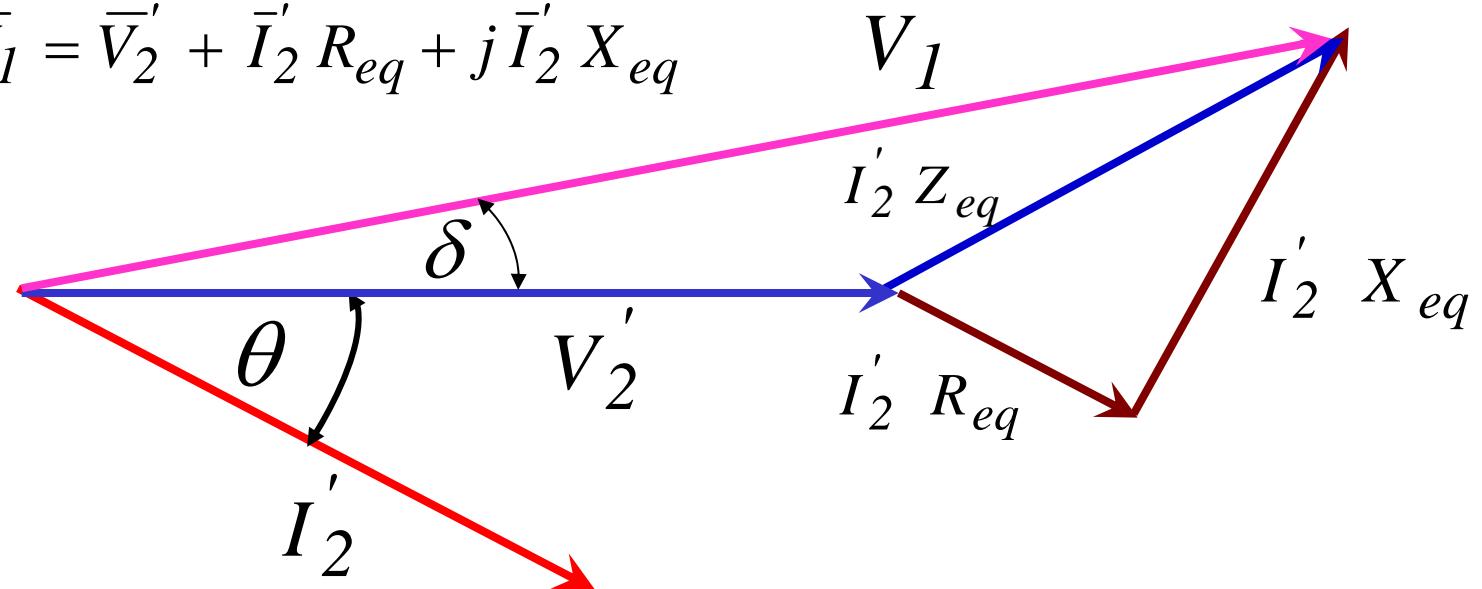
$$\bar{V}_1 = \bar{V}_2' + \bar{I}_2' R_{eq} + j \bar{I}_2' X_{eq}$$



- ***Rated voltage:*** The device can continuously operate at the rated voltage without being damaged due to insulation failure
- ***Rated current:*** The device can continuously operate at the rated current without being damaged due to thermal destruction


Transformer Rating and Name Plate

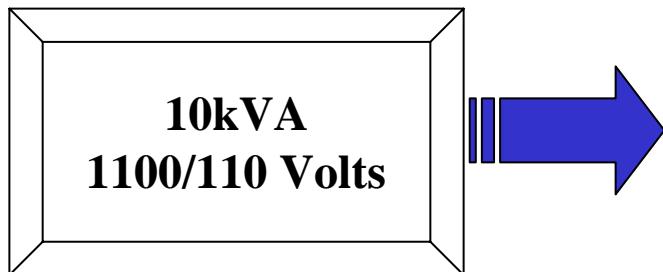

- The transformer has two windings one rated for 1100V and the other one for 110V
 $a = 1100/110 = 10 = \text{turns ratio}$
- Each winding is designed for 10 kVA.
- The current rating for high-voltage winding is $10000/1100 = 9.09 \text{ A}$
- The current rating for lower-voltage winding is $10000/110 = 90.9 \text{ A}$

Equivalent Circuit Parameters

No-Load test (Open-Circuit Test)

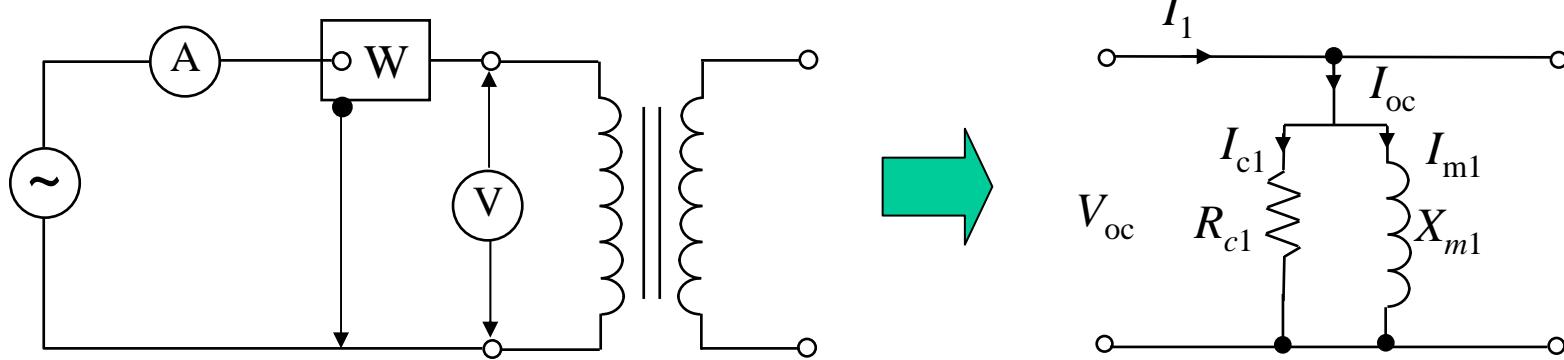

$$R_{c1} = \frac{V_{oc}^2}{P_{oc}}$$

$$I_{c1} = \frac{V_{oc}}{R_{c1}}, \quad I_{m1} = \sqrt{I_{oc}^2 - I_{c1}^2}$$

$$X_{m1} = \frac{V_{oc}}{I_{m1}}$$

$$P_{oc} = I_{oc} V_{oc} \cos(\Phi_o)$$



$$\cos(\Phi_o) = \frac{P_{oc}}{I_{oc} V_{oc}}$$

$$I_{c1} = I_{oc} \cos(\Phi_o) \quad \& \quad I_{m1} = I_{oc} \sin(\Phi_o)$$

$$R_{c1} = \frac{V_{oc}}{I_{c1}}, \quad X_{m1} = \frac{V_{oc}}{I_{m1}}$$

Equivalent Circuit Parameters

Short-Circuit Test

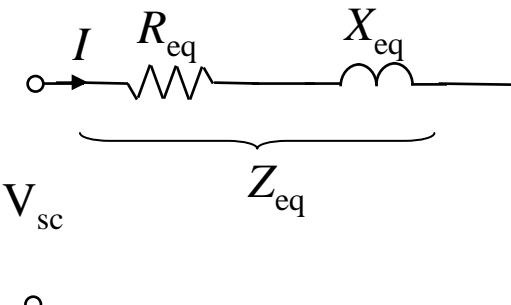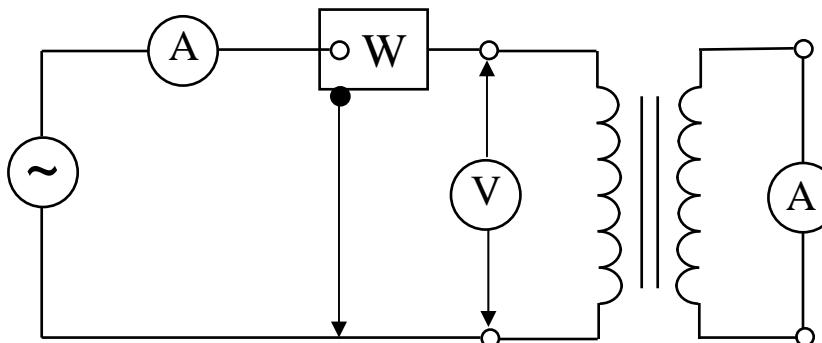

$$R_{eq} = \frac{P_{sc}}{I_{sc}^2}$$

$$Z_{eq} = \frac{V_{sc}}{I_{sc}}$$

$$X_{eq} = \sqrt{Z_{eq}^2 - R_{eq}^2}$$

$$\cos(\Phi_{sc}) = \frac{P_{sc}}{I_{sc} V_{sc}}$$

$$Z_{sc} = \frac{V_{sc}}{I_{sc}}$$

$$R_{eq} = Z_{sc} \cos(\Phi_{sc})$$

$$X_{eq} = Z_{sc} \sin(\Phi_{sc})$$

$$R_1 + a^2 R_2 = R_{eq1} \quad \& \quad X_1 + a^2 X_2 = X_{eq}$$

The primary resistance R_1 can be measured directly.

The leakage reactance is assumed to be divided equally, $X_1 = a^2 X_2 = 0.5 X_{eq}$

Determining the values of components

Example:

Example 2: We need to determine the equivalent circuit impedances of a 20 kVA, 8000/240 V, 60 Hz transformer. The open-circuit and short-circuit tests led to the following data:

$V_{OC} = 8000 \text{ V}$	$V_{SC} = 489 \text{ V}$
$I_{OC} = 0.214 \text{ A}$	$I_{SC} = 2.5 \text{ A}$
$P_{OC} = 400 \text{ W}$	$P_{SC} = 240 \text{ W}$

The power factor during the open-circuit test is

$$PF = \cos \theta = \frac{P_{OC}}{V_{OC} I_{OC}} = \frac{400}{8000 \cdot 0.214} = 0.234 \text{ lagging}$$

The excitation admittance is

$$Y_E = \frac{I_{OC}}{V_{OC}} \angle -\cos^{-1} PF = \frac{0.214}{8000} \angle -\cos^{-1} 0.234 = 0.0000063 - j0.0000261 = \frac{1}{R_C} - j \frac{1}{X_M}$$

Determining the values of components

Example:

Therefore:

$$R_C = \frac{1}{0.0000063} = 159 \text{ k}\Omega; \quad X_M = \frac{1}{0.0000261} = 38.3 \text{ k}\Omega$$

The power factor during the short-circuit test is

$$PF = \cos \theta = \frac{P_{SC}}{V_{SC} I_{SC}} = \frac{240}{489 \cdot 2.5} = 0.196 \text{ lagging}$$


The series impedance is given by

$$Z_{SE} = \frac{V_{SC}}{I_{SC}} \angle \cos^{-1} PF = \frac{489}{2.5} \angle 78.7^\circ \\ = 38.4 + j192 \Omega$$


Therefore:

$$R_{eq} = 38.3 \Omega; \quad X_{eq} = 192 \Omega$$


The equivalent circuit

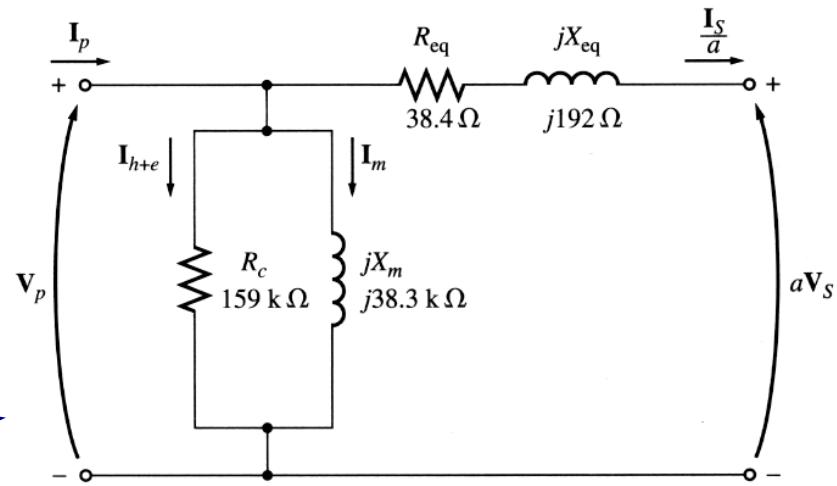

Multi-secondary windings

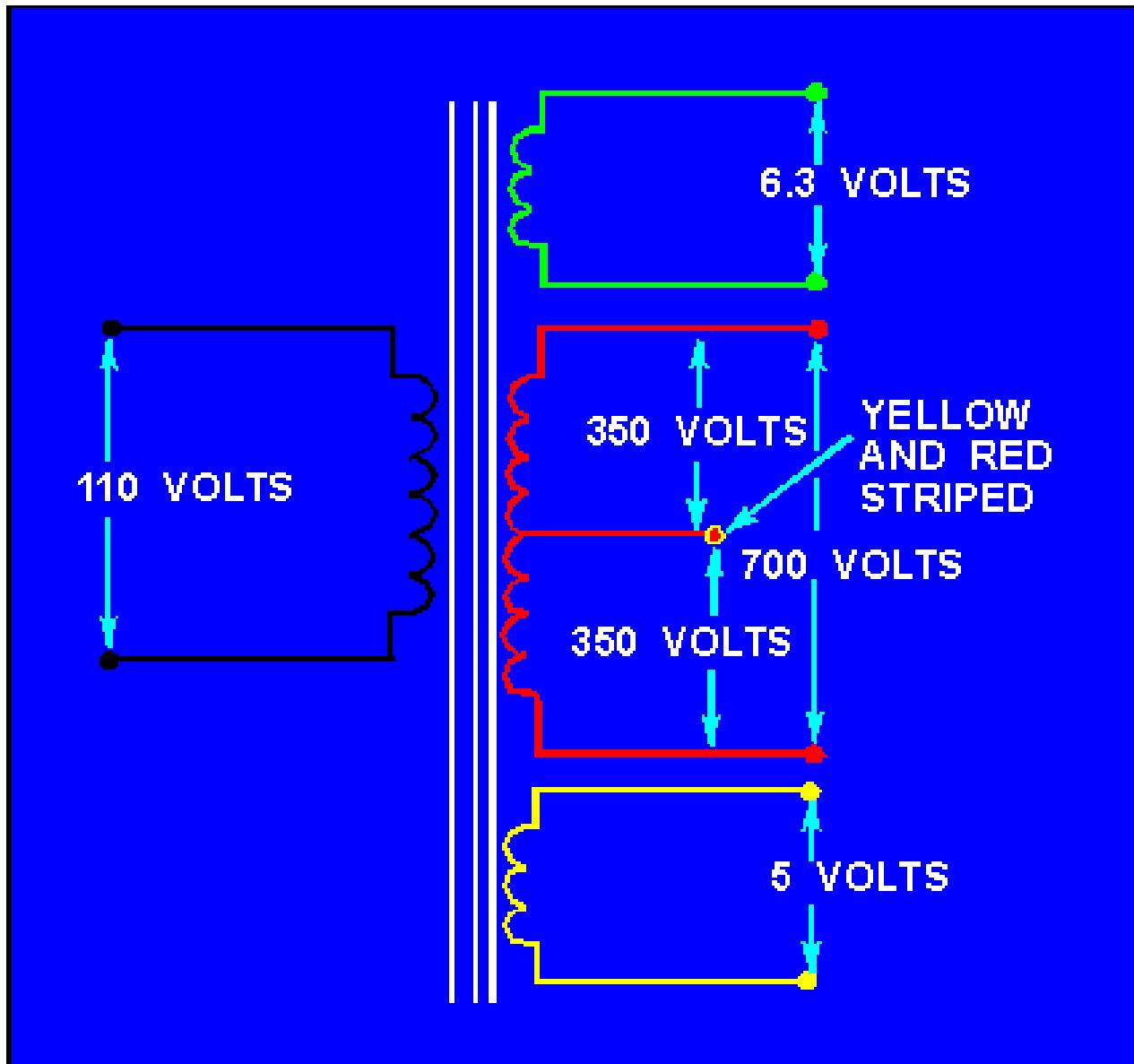


Multi-secondary windings

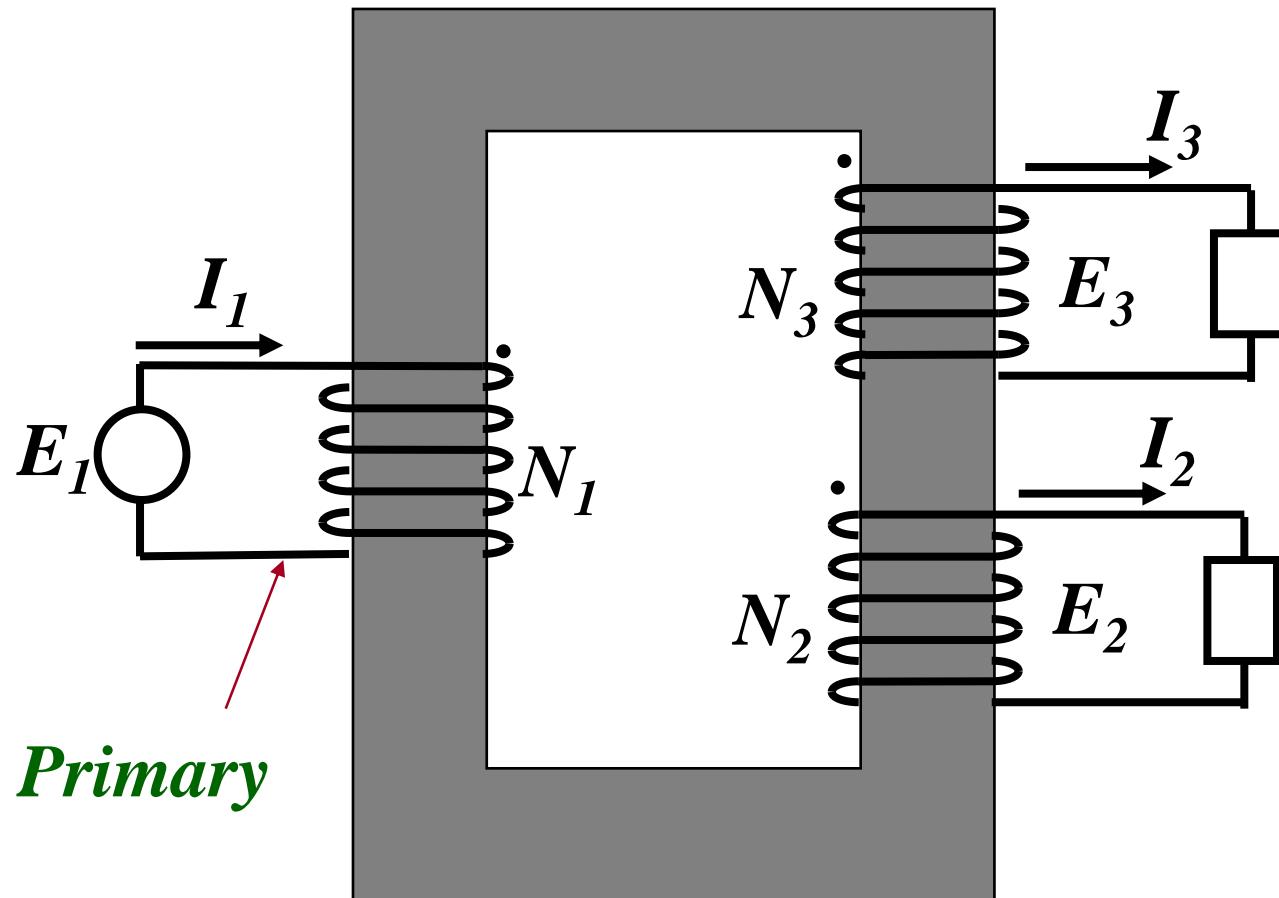


$$\frac{E_1}{E_2} = \frac{N_1}{N_2}$$

$$\frac{E_1}{E_3} = \frac{N_1}{N_3}$$

Autotransformer

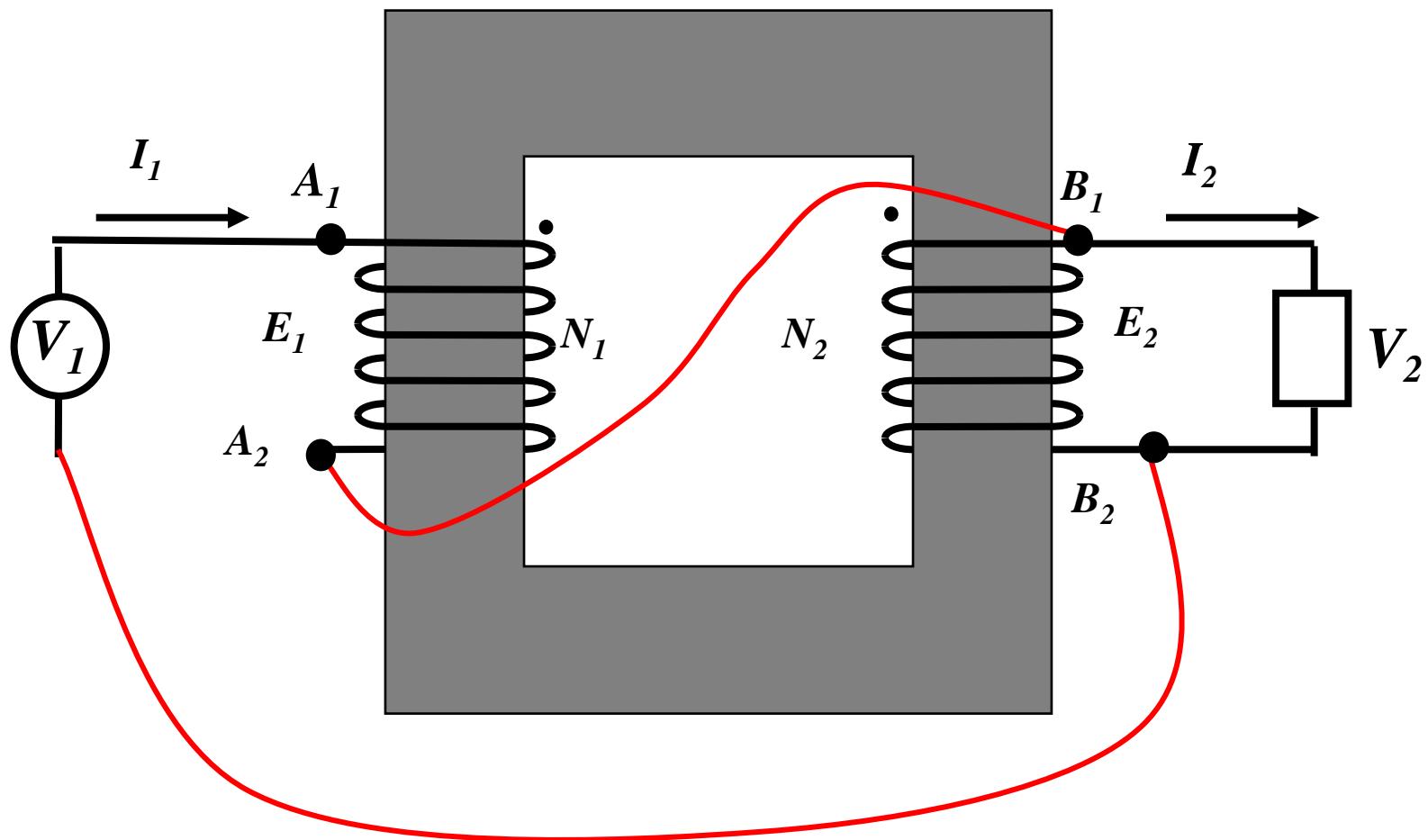

Autotransformer

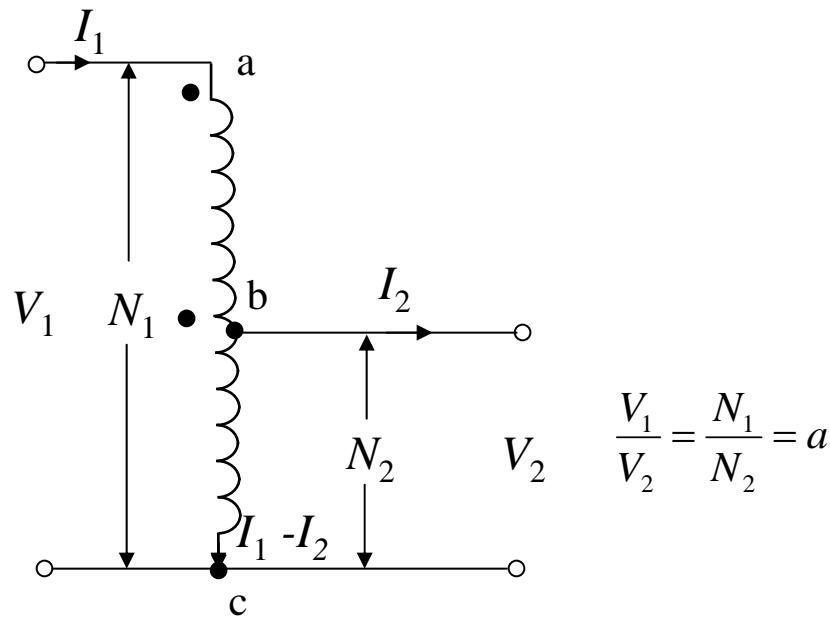

Advantages:

- Lower leakage reactances
- Lower losses
- Lower exciting current
- Increased kVA rating
- Variable voltage output


Disadvantage:

- The direct connection between the primary and secondary sides.


Autotransformer: Voltage and current

$$\bar{I}_{load} = \bar{I}_1 + \bar{I}_2$$


$$\bar{V}_1 = \bar{E}_1 + \bar{E}_2$$

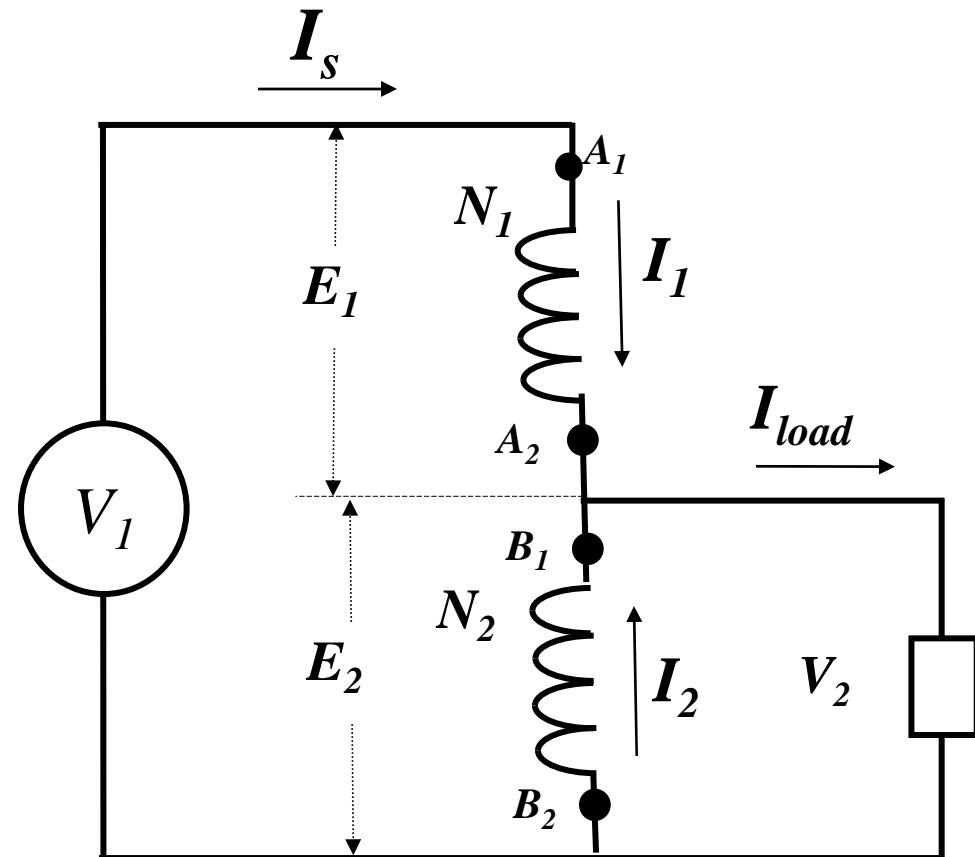

Autotransformer

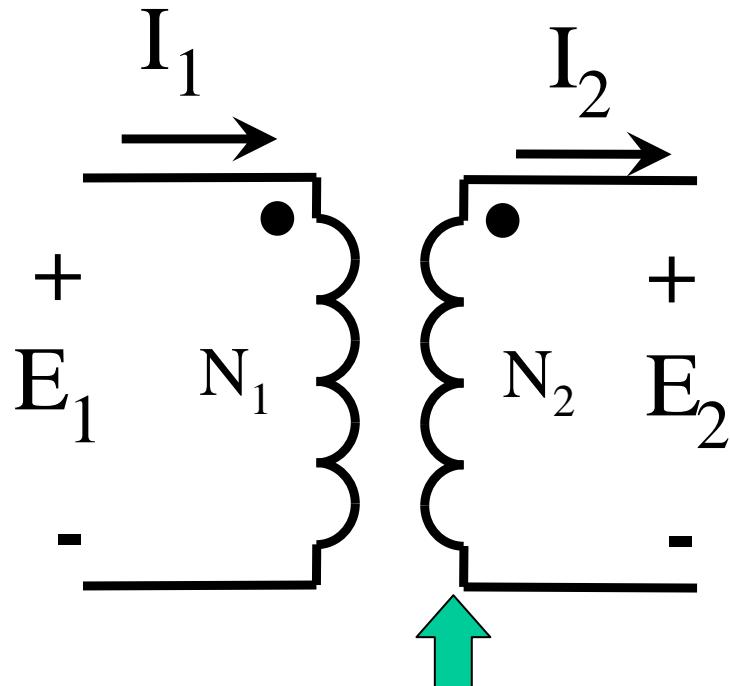

$$|S_A| = E_1 I_1 = E_2 I_2$$

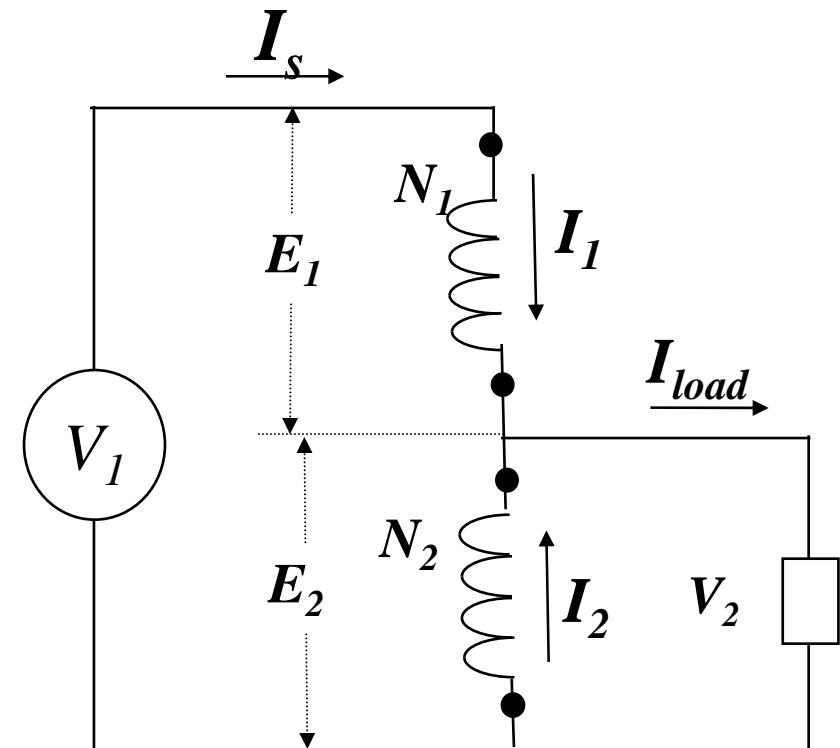

$$|S_B| = V_1 I_s = V_2 I_{load}$$



Autotransformer: Power

$$|S_B| = V_1 I_s = (E_1 + E_2) I_1 = E_1 I_1 + E_2 I_1$$

$$|S_B| = |S_A| + E_2 I_1$$

$$|S_B| > |S_A|$$

VARIC: Variable Auto-Transformer

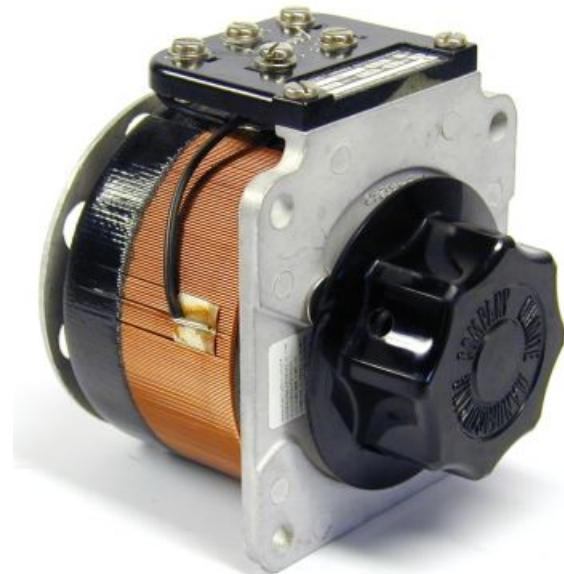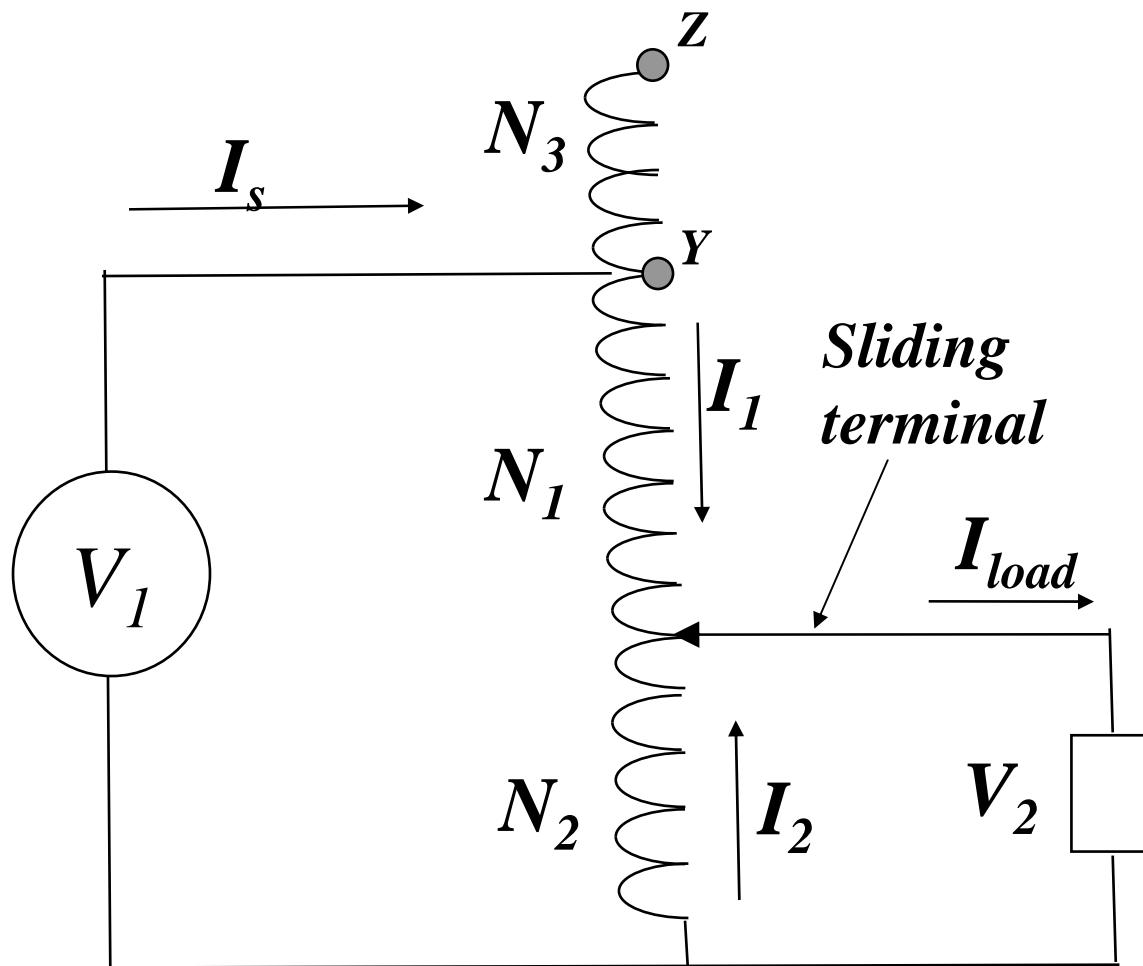

VARIC: Output Voltage


$$V_{load} = V_s \frac{N_2}{N_1 + N_2}$$

At Y

$$V_{load} = V_s \frac{N_1 + N_2}{N_1 + N_2} = V_s$$

At Z

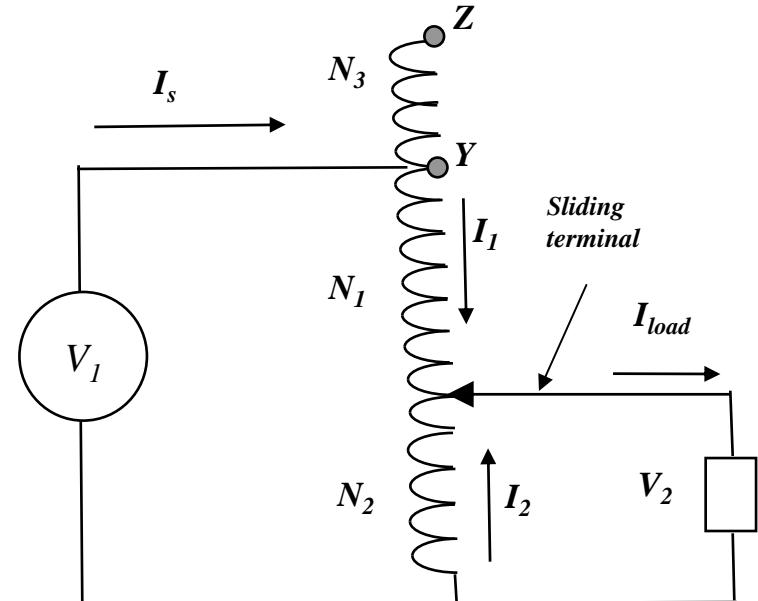
$$V_{load} = V_s \frac{N_1 + N_2 + N_3}{N_1 + N_2}$$



The Variac can adjust the load voltage from zero to greater than the supply voltage.

Voltage Regulation

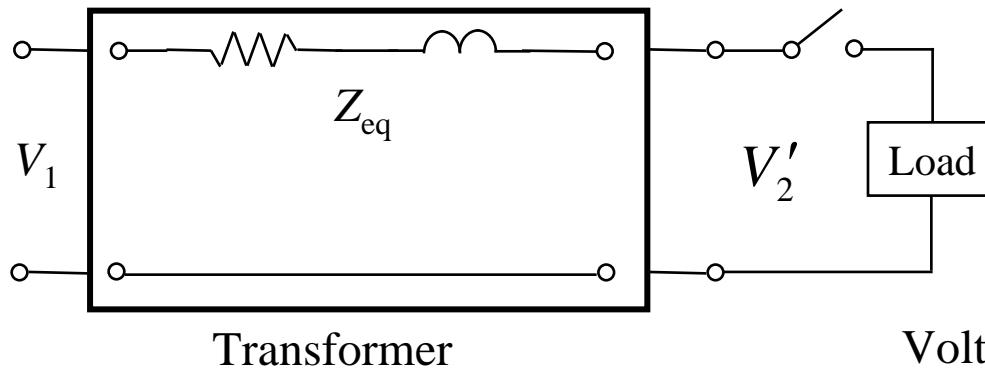voltage regulation is the ability of a system to provide near constant voltage over a wide range of load conditions.




$$\text{Voltage regulation} = \frac{|V|_{NL} - |V|_L}{|V|_L}$$

Referred to Primary

$$\text{Voltage regulation} = \frac{|V'_2|_{NL} - |V'_2|_L}{|V'_2|_L}$$

$|V'_2|_{NL} = |V_1|$

$$\text{Voltage regulation} = \frac{|V_1| - |V'_2|_L}{|V'_2|_L}$$

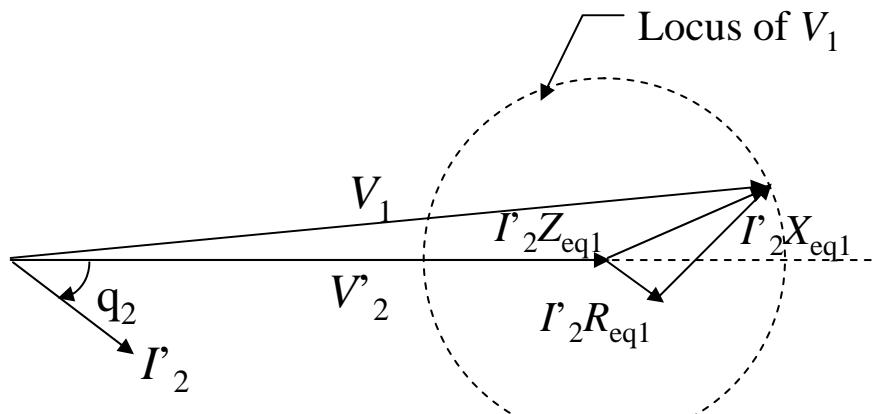

θ_2 is the angle of the load impedance

Efficiency

$$\eta = \frac{P_{out}}{P_{in}} = \frac{P_{out}}{P_{out} + P_{losses}} = \frac{P_{out}}{P_{out} + P_c + P_{cu}}$$

$$P_{out} = V_2 I_2 \cos \theta_2$$

$$P_{cu} = I_1^2 R_1 + I_2^2 R_2 = I_1^2 R_{eq1} = I_2^2 R_{eq2}$$

$$P_c = I_{c1}^2 R_c$$



$$\eta = \frac{V_2 I_2 \cos \theta_2}{V_2 I_2 \cos \theta_2 + I_{c1}^2 R_c + I_2^2 R_{eq2}} = F(I_2, \cos \theta_2)$$

The transformer efficiency:

Example

Example : A 15 kVA, 2300/230 V transformer was tested to by open-circuit and closed-circuit tests. The following data was obtained:

$V_{OC} = 2300 \text{ V}$	$V_{SC} = 47 \text{ V}$
$I_{OC} = 0.21 \text{ A}$	$I_{SC} = 6.0 \text{ A}$
$P_{OC} = 50 \text{ W}$	$P_{SC} = 160 \text{ W}$

- Find the equivalent circuit of this transformer referred to the high-voltage side.
- Find the equivalent circuit of this transformer referred to the low-voltage side.
- Calculate the full-load voltage regulation at 0.8 lagging power factor, at 1.0 power factor, and at 0.8 leading power factor.
- Plot the voltage regulation as load is increased from no load to full load at power factors of 0.8 lagging, 1.0, and 0.8 leading.
- What is the efficiency of the transformer at full load with a power factor of 0.8 lagging?

The transformer efficiency: Example

a. The excitation branch values of the equivalent circuit can be determined as:

$$\theta_{oc} = \cos^{-1} \frac{P_{oc}}{V_{oc} I_{oc}} = \cos^{-1} \frac{50}{2300 \cdot 0.21} = 84^\circ$$

The excitation admittance is:

$$Y_E = \frac{I_{oc}}{V_{oc}} \angle -84^\circ = \frac{0.21}{2300} \angle -84^\circ = 0.0000\,095 - j0.0000\,908 \text{ S}$$

The elements of the excitation branch referred to the primary side are:

$$R_c = \frac{1}{0.0000095} = 105 \text{ k}\Omega$$

$$X_M = \frac{1}{0.0000908} = 11 \text{ k}\Omega$$

The transformer efficiency:

Example

From the short-circuit test data, the short-circuit impedance angle is

$$\theta_{SC} = \cos^{-1} \frac{P_{SC}}{V_{SC} I_{SC}} = \cos^{-1} \frac{160}{47 \cdot 6} = 55.4^\circ$$


The equivalent series impedance is thus

$$Z_{SE} = \frac{V_{SC}}{I_{SC}} \angle \theta_{SC} = \frac{47}{6} \angle 55.4^\circ = 4.45 + j6.45 \Omega$$

The series elements referred to the primary winding are:

$$R_{eq} = 4.45 \Omega; \quad X_{eq} = 6.45 \Omega$$

The equivalent circuit

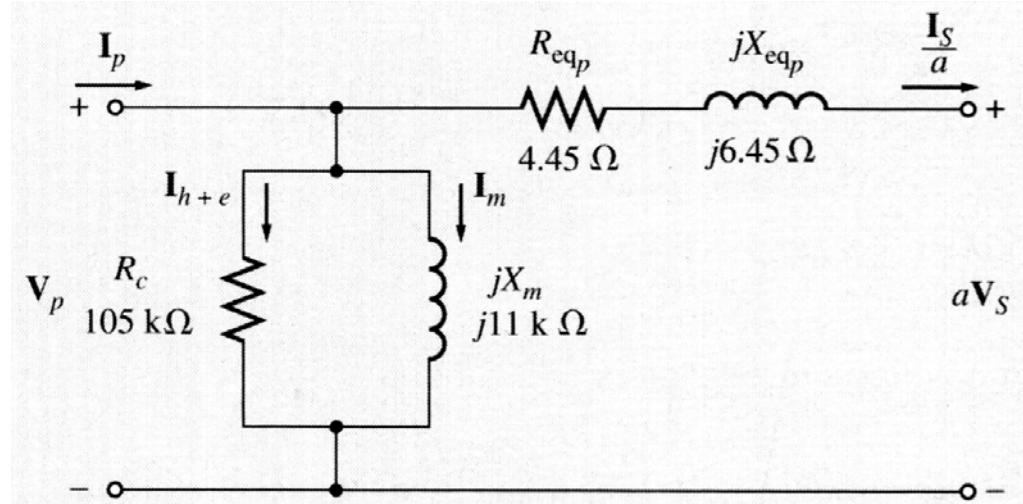


The transformer efficiency:

Example

b. To find the equivalent circuit referred to the low-voltage side, we need to divide the impedance by a^2 . Since $a = 10$, the values will be:

$$R_C = 1050 \Omega \quad X_M = 110 \Omega \quad R_{eq} = 0.0445 \Omega \quad X_{eq} = 0.0645 \Omega$$

The equivalent circuit will be

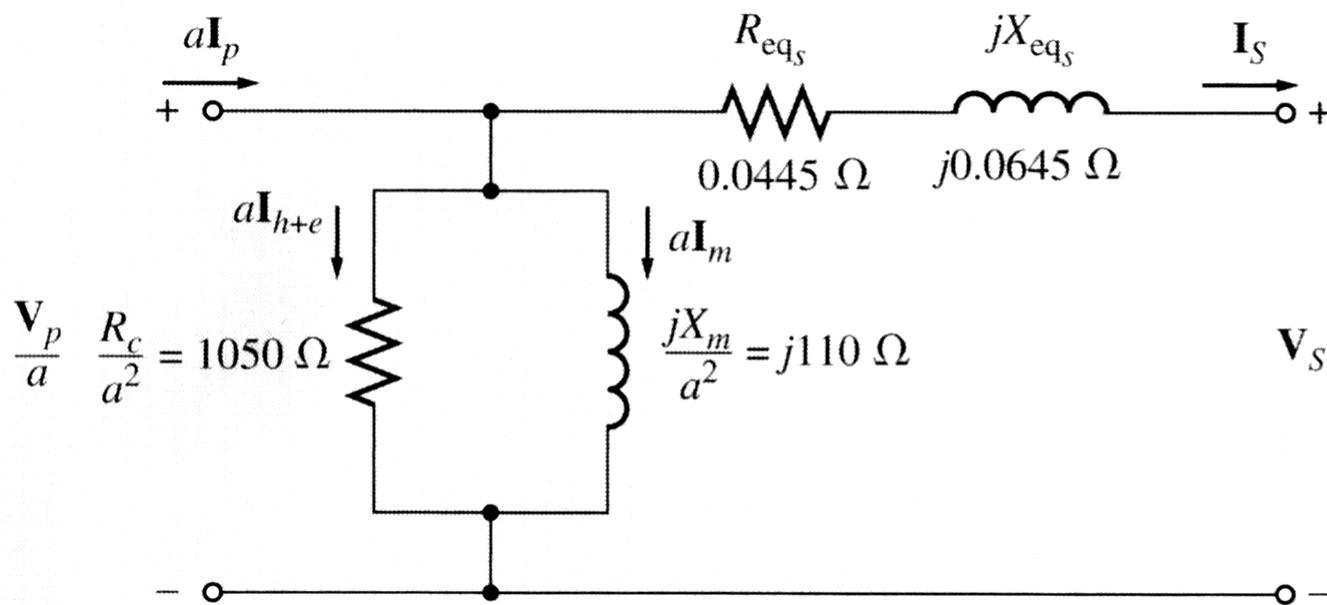

The transformer efficiency:

Example

c. The full-load current on the secondary side of the transformer is

$$I_{S, \text{rated}} = \frac{S_{\text{rated}}}{V_{S, \text{rated}}} = \frac{15\,000}{230} = 65.2 \text{ A}$$

Since:

$$\frac{V_p}{a} = V_S + R_{eq} I_S + jX_{eq} I_S$$


At PF = 0.8 lagging, current

$$I_s = 65.2 \angle -\cos^{-1}(0.8) = 65.2 \angle -36.9^\circ \text{ A}$$

and $\frac{V_p}{a} = 230 \angle 0^\circ + 0.0445 \cdot (65.2 \angle -36.9^\circ) + j0.0645 \cdot (65.2 \angle -36.9^\circ) = 234.85 \angle 0.40^\circ \text{ V}$

The resulting voltage regulation is, therefore:

$$\begin{aligned} VR &= \frac{|V_p/a| - V_{S, \text{fl}}}{V_{S, \text{fl}}} \cdot 100\% \\ &= \frac{234.85 - 230}{230} \cdot 100\% \\ &= 2.1\% \end{aligned}$$

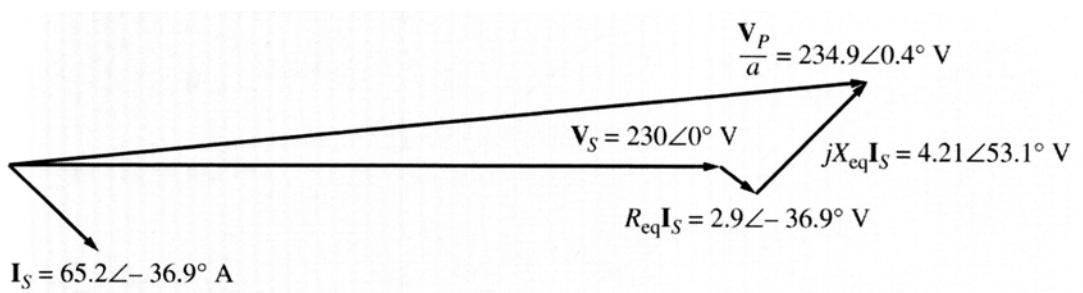

The transformer efficiency:

Example

At PF = 1.0, current

$$I_s = 65.2 \angle \cos^{-1}(1.0) = 65.2 \angle 0^\circ \text{ A}$$

and

$$\frac{V_p}{a} = 230 \angle 0^\circ + 0.0445 \cdot (65.2 \angle 0^\circ) + j0.0645 \cdot (65.2 \angle 0^\circ) = 232.94 \angle 1.04^\circ \text{ V}$$

The resulting voltage regulation is, therefore:

$$VR = \frac{|V_p/a| - V_{s,fl}}{V_{s,fl}} \cdot 100\% = \frac{232.94 - 230}{230} \cdot 100\% = 1.28\%$$



The transformer efficiency:

Example

At PF = 0.8 leading, current

$$I_s = 65.2 \angle \cos^{-1}(0.8) = 65.2 \angle 36.9^\circ \text{ A}$$

and


$$\frac{V_p}{a} = 230 \angle 0^\circ + 0.0445 \cdot (65.2 \angle 36.9^\circ) + j0.0645 \cdot (65.2 \angle 36.9^\circ) = 229.85 \angle 1.27^\circ \text{ V}$$

The resulting voltage regulation is, therefore:

$$VR = \frac{|V_p/a| - V_{s,fl}}{V_{s,fl}} \cdot 100\% = \frac{229.85 - 230}{230} \cdot 100\% = -0.062\%$$

$$I_s = 65.2 \angle 36.9^\circ \text{ A}$$

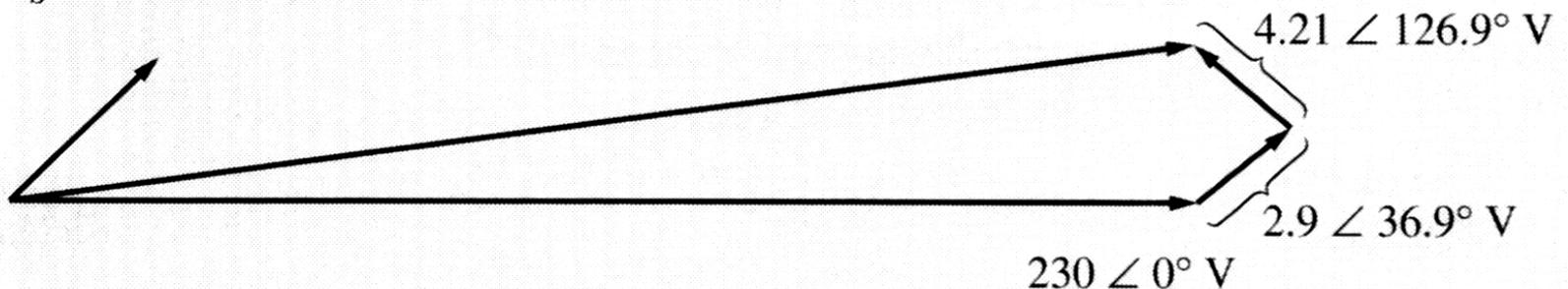
$$\frac{V_p}{a} = 229.8 \angle 1.27^\circ \text{ V}$$



The transformer efficiency:

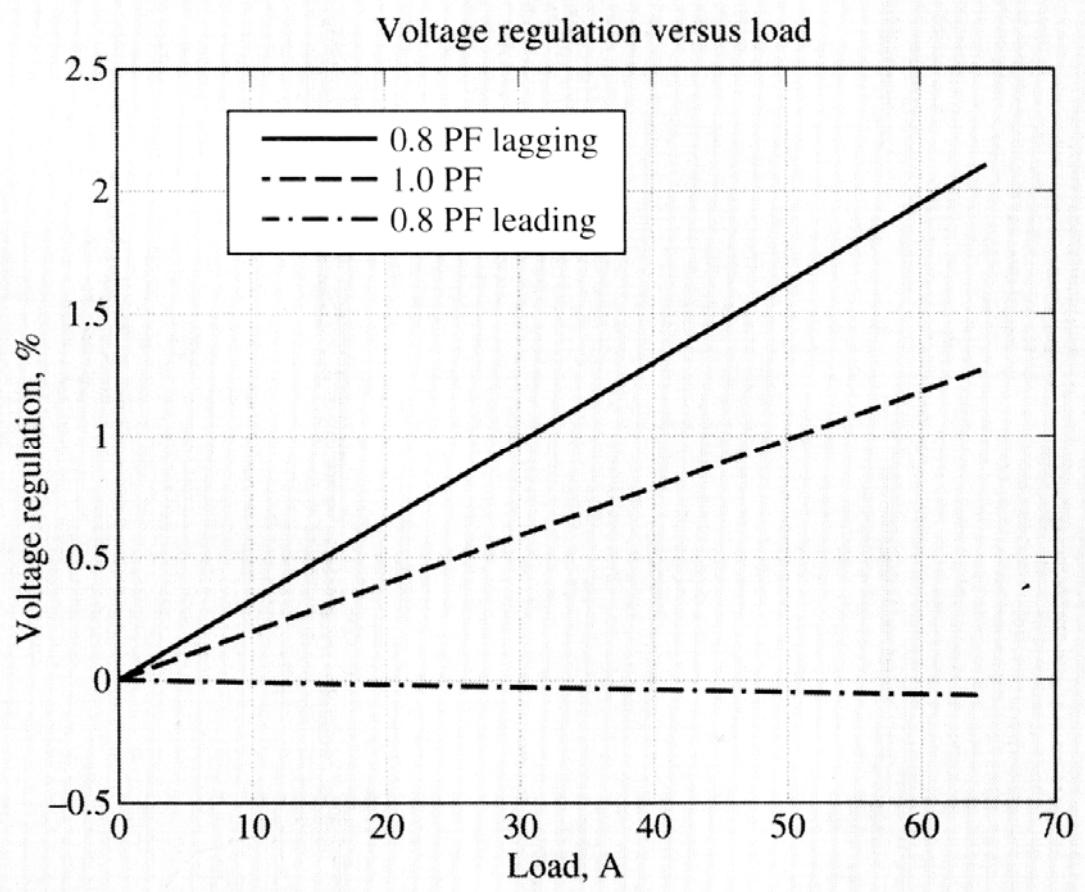Example

Similar computations can be repeated for different values of load current. As a result, we can plot the voltage regulation as a function of load current for the three Power Factors.



The transformer efficiency: Example

e. To find the efficiency of the transformer, first calculate its losses.

The copper losses are:

$$P_{Cu} = I_s^2 R_{eq} = 65.2^2 \cdot 0.0445 = 189 \text{ W}$$

The core losses are:

$$P_{core} = \frac{(V_p/a)^2}{R_C} = \frac{234.85^2}{1050} = 52.5 \text{ W}$$

The output power of the transformer at the given Power Factor is:

$$P_{out} = V_s I_s \cos \theta = 230 \cdot 65.2 \cdot \cos 36.9^\circ = 12000 \text{ W}$$

Therefore, the efficiency of the transformer is

$$\eta = \frac{P_{out}}{P_{Cu} + P_{core} + P_{out}} \cdot 100\% = 98.03\%$$

Transformer taps and voltage regulation




We assumed before that the transformer turns ratio is a fixed (constant) for the given transformer. Frequently, distribution transformers have a series of taps in the windings to permit small changes in their turns ratio. Typically, transformers may have 4 taps in addition to the nominal setting with spacing of 2.5 % of full-load voltage. Therefore, adjustments up to 5 % above or below the nominal voltage rating of the transformer are possible.

Example : A 500 kVA, 13 200/480 V transformer has four 2.5 % taps on its primary winding. What are the transformer's voltage ratios at each tap setting?

+ 5.0% tap	13 860/480 V
+ 2.5% tap	13 530/480 V
Nominal rating	13 200/480 V
- 2.5% tap	12 870/480 V
- 5.0% tap	12 540/480 V

3-phase transformers

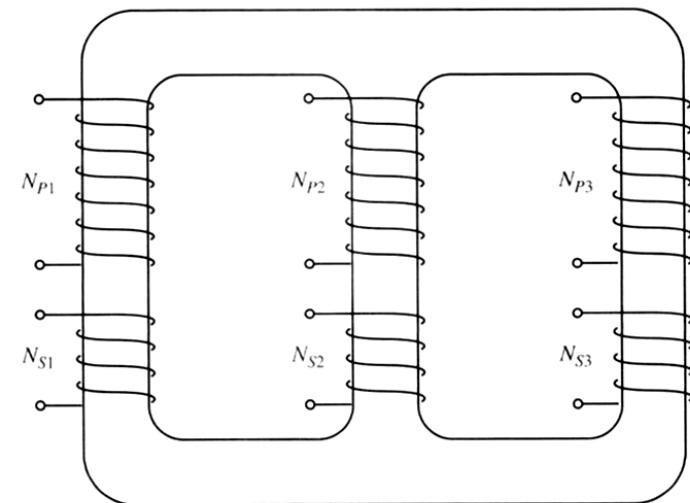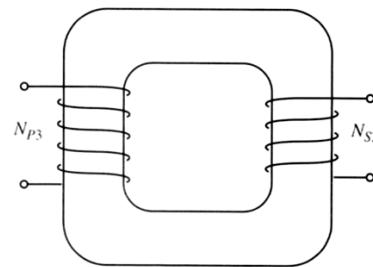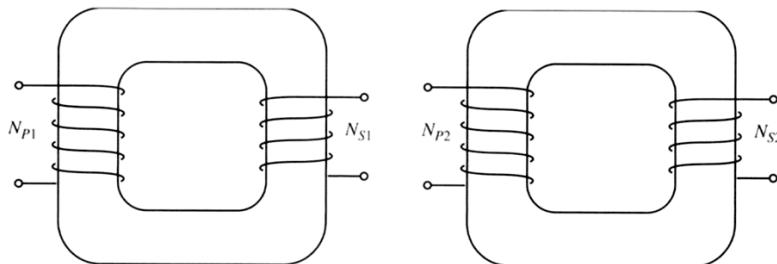The majority of the power generation/distribution systems in the world are 3-phase systems. The transformers for such circuits can be constructed either as a 3-phase bank of independent identical transformers (can be replaced independently) or as a single transformer wound on a single 3-legged core (lighter, cheaper, more efficient).



3-phase transformers


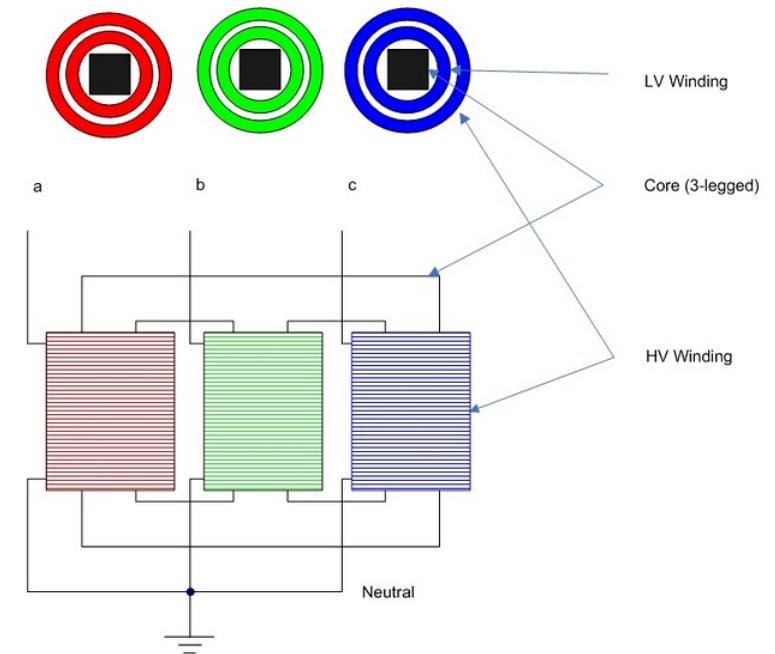
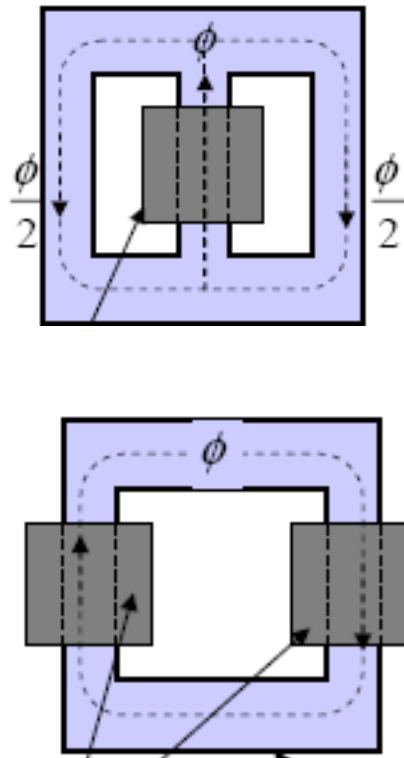


Fig – B: Three Phase Transformer with Top View

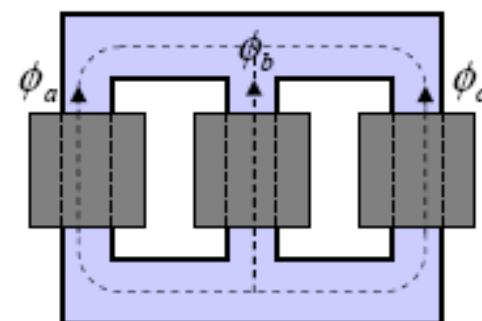

3-phase transformer Connection

We assume that any single transformer in a 3-phase transformer (bank) behaves exactly as a single-phase transformer. The impedance, voltage regulation, efficiency, and other calculations for 3-phase transformers are done on a per-phase basis, using the techniques studied previously for single-phase transformers.

Four possible connections for a 3-phase **transformer bank** are:

- 1.Y-Y
- 2.Y- Δ
3. Δ - Δ
4. Δ -Y





3-phase transformer Connection

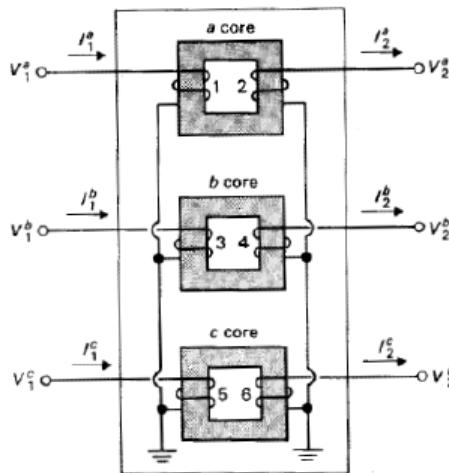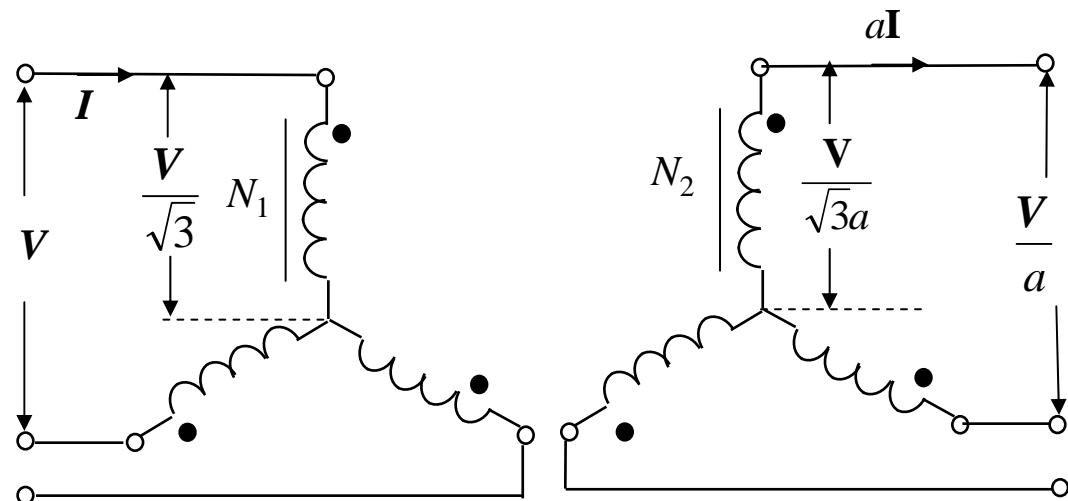1. Y-Y connection:

$$\frac{V_{ph1}}{V_{ph2}} = \frac{N_1}{N_2} = a$$

$$\frac{V_{L1}}{V_{L2}} = \frac{\sqrt{3} V_{ph1}}{\sqrt{3} V_{ph2}} = a$$






Y-Y

3-phase transformer Connection

2. Y- Δ connection:

- **Wye-Delta Connection Y- Δ**

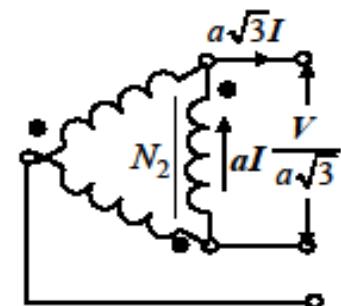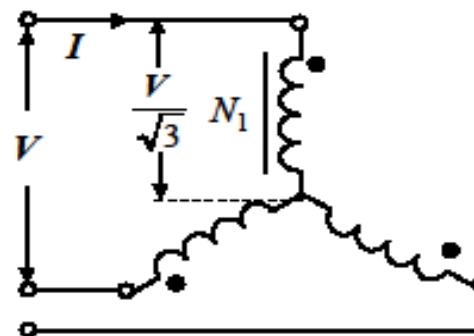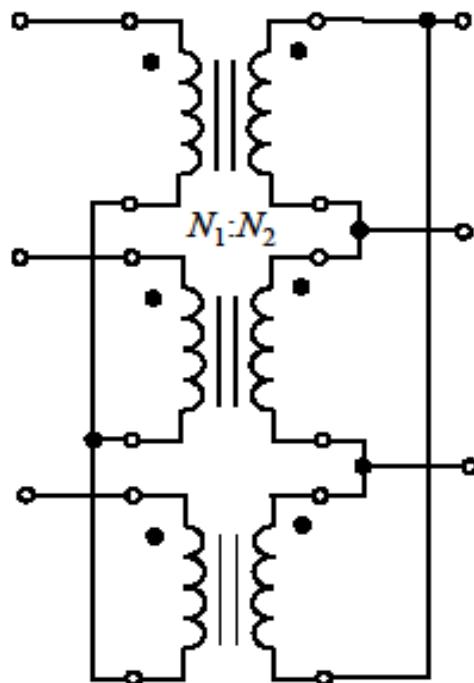


Y - Δ

$$a = \frac{N_1}{N_2} = \text{turns ratio}$$

3-phase transformer Connection

3. Δ - Y connection:

Delta – Way Connection Δ - Y

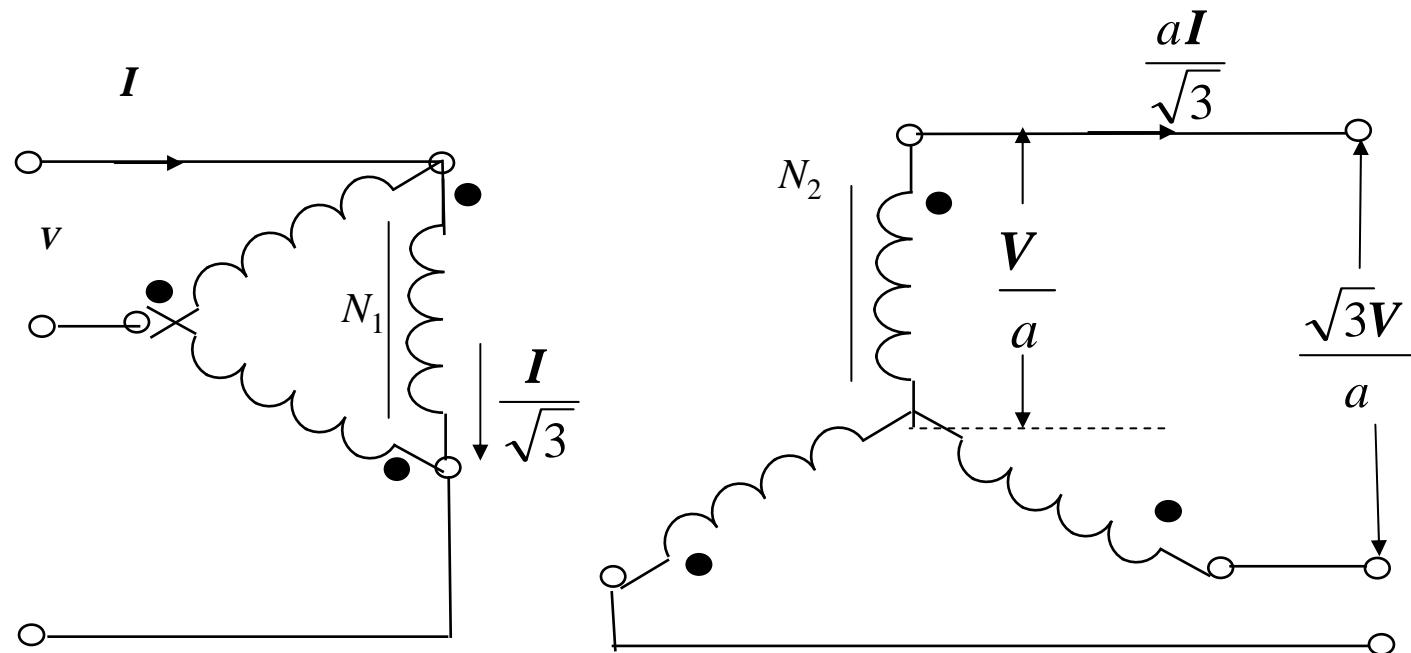


Δ - Y

3-phase transformer Connection

4. $\Delta - \Delta$ connection:

The primary voltage on each phase of the transformer is

$$V_{\phi P} = V_{LP}$$

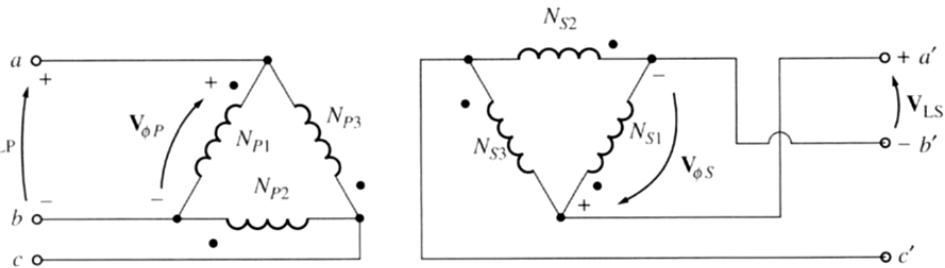


The secondary phase voltage is

$$V_{LS} = V_{\phi S}$$

The overall voltage ratio is

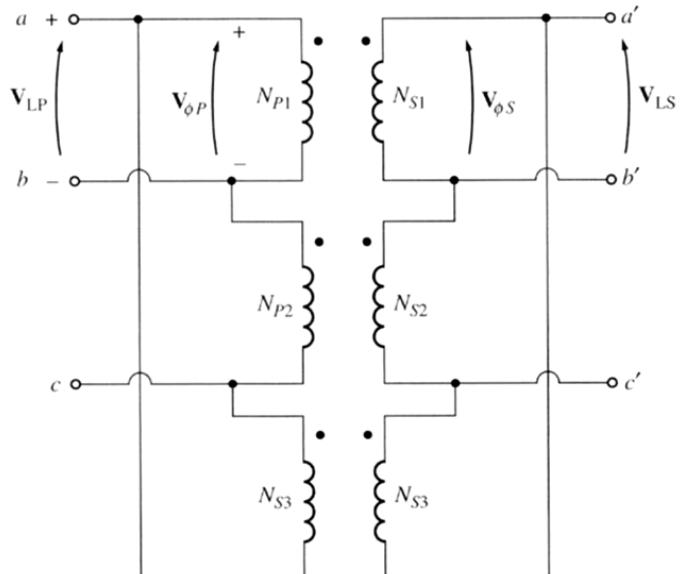
$$\frac{V_{LP}}{V_{LS}} = \frac{V_{\phi P}}{V_{\phi S}} = a$$



No phase shift, no problems with unbalanced loads or harmonics.

3-phase transformer

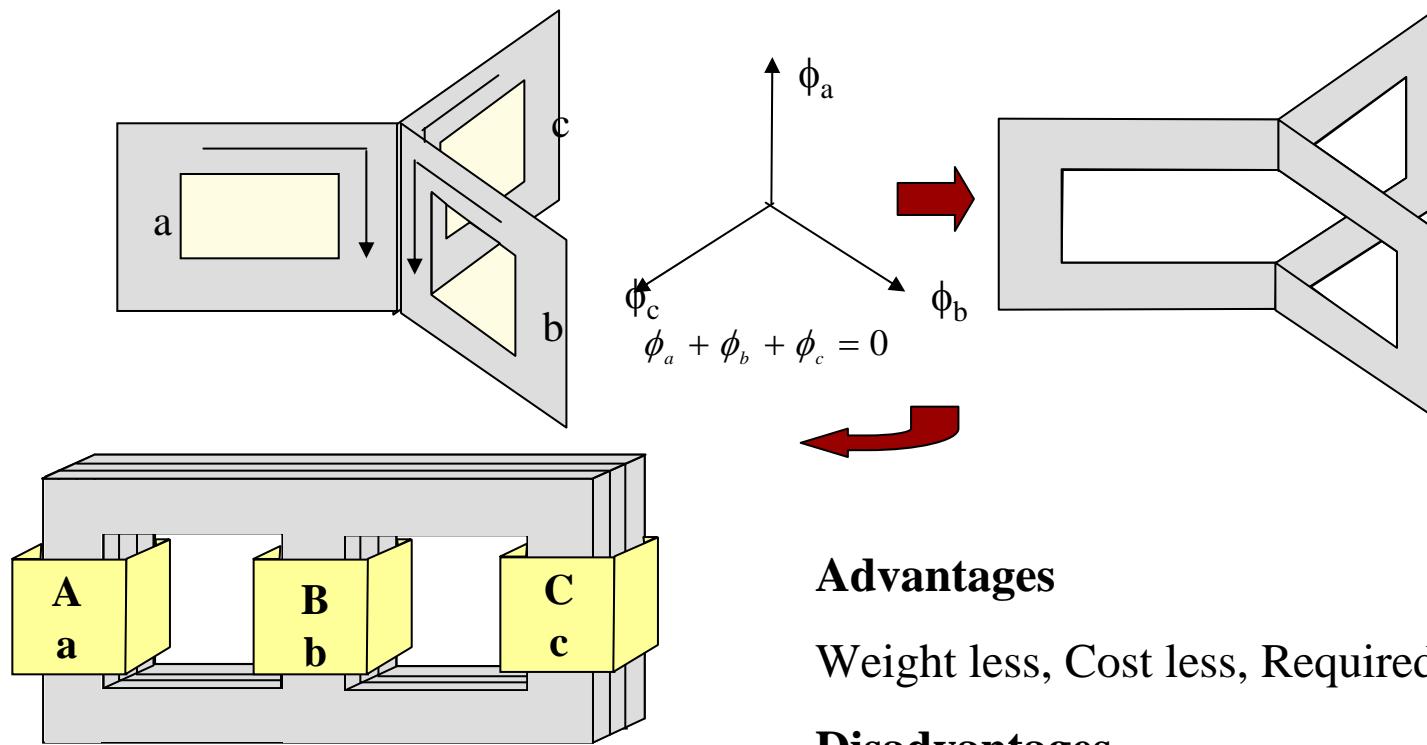- A three phase transformer can be constructed by having three primary and three secondary windings on a common magnetic core as shown in the following Figure.



Advantages



Weight less, Cost less, Required less space

Disadvantages

Magnetic current imbalance

3-phase transformer

- Phase Shift

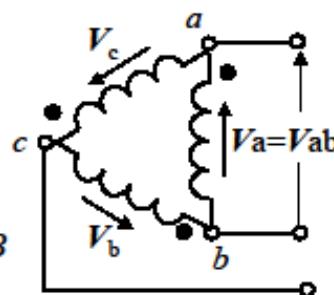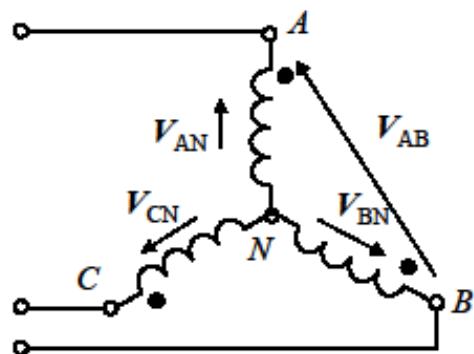

$Y - \Delta \Rightarrow V_{AB}$ leads V_{ab} by 30°

$\Delta - Y \Rightarrow V_{AB}$ lags V_{ab} by 30°

$\Delta - \Delta \Rightarrow$ No phase shift

$Y - Y \Rightarrow$ No phase shift

